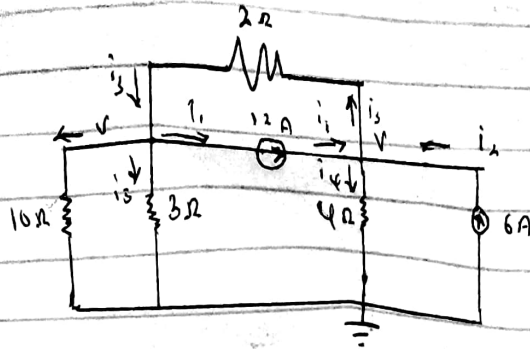


EMEROLE CHINAEME IKENNA
MECHATRONICS ENG

17/ENG05/012



at node V_1

$$i_3 = i_1 + i_5 + i_6 = 12 + i_5 + i_6$$

$$12 = 12 - i_5 - i_6$$

$$12 = \frac{V_2 - V_1}{2} + \left[\frac{V_1 - 0}{5} \right] - \left[\frac{V_1 - 0}{10} \right]$$

$$12 = \frac{V_2 - V_1}{2} - \frac{V_1}{5} - \frac{V_1}{10}$$

$$12 = \frac{V_2 - V_1}{2} - \frac{V_1}{5} - \frac{V_1}{10}$$

$$12 = \frac{5(V_2 - V_1) - 2(V_1) - V_1}{10}$$

$$120 = 5V_2 - 5V_1 - 2V_1 - V_1$$

$$120 = 5V_2 - 8V_1 \quad \dots (1)$$

from node V_2

$$i_1 + i_2 + i_3 + i_4$$

$$12 + 6 = \frac{V_2 - V_1}{2} + \left[\frac{V_2}{4} \right]$$

$$18 = \frac{V_2 - V_1}{2} + \frac{V_2}{4}$$

$$18 = \frac{2(V_2 - V_1) + V_2}{4}$$

$$72 = 3V_2 - 2V_1 \quad \dots (2)$$

Using Simultaneous Equ

$$120 = 5V_2 - 8V_1 \quad \text{--- (2)}$$

$$72 = 3V_2 - 2V_1 \quad \text{--- (1)}$$

$$240 = 10V_2 - 16V_1$$

$$576 = 24V_2 - 16V_1$$

$$\frac{-336}{-14} = \frac{-144V_2}{-14}$$

$$V_2 = 24V$$

From Equ (1)

$$120 = 5(24) - 8V_1$$

$$120 = 120 - 8V_1$$

$$8V_1 = 120 - 120$$

$$V_1 = 0$$

Current flowing through the 2Ω resistor


$$= \frac{V_2 - V_1}{2} = \frac{24 - 0}{2} = 12A$$

while the current flowing through the 4Ω resistor

$$= \frac{V_1}{4} = \frac{0}{4} = 0A$$

Since both V_1 being 0 then current through the 10Ω & 5Ω resistor both equal to zero (0)

~~At node~~

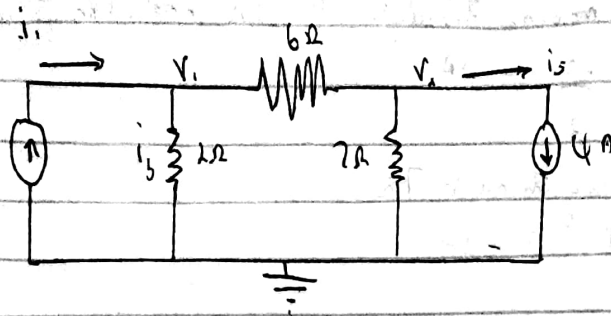

At node 1

$$i_1 = i_2 + i_3$$

$$1 = \left[\frac{V_1 - V_2}{6} \right] + \left[\frac{V_1 - V_2}{2} \right]$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$1 = \frac{V_1 - V_2 + 3V_1}{6}$$

$$6 = 4V_1 - V_2 \quad \dots (1)$$

At node 2

$$i_3 = i_4 + i_5$$

$$\left[\frac{V_1 - V_2}{6} \right] = \left[\frac{V_2}{7} \right] + 4$$

$$\frac{V_1 - V_2}{6} = \frac{V_2}{7} + 4$$

$$7(V_1 - V_2) - 6V_2 = 4$$

or

$$108 = 7V_1 - 13V_2 \quad \dots (2)$$

Solving Simultaneously

$$V_1 = 2V \text{ \& } V_2 = 14V$$

from this current moving through the 6Ω

$$= V_1 - V_2$$


$$= \frac{-2 - 14}{6} = \frac{-16}{6}$$

$$= -2.67A$$

from this current moving through the 2Ω resistor
 $= \frac{V_1}{2} = \frac{2}{2} = 1A$

Current moving through 7Ω
 $\frac{V_2}{7} = \frac{-14}{7} = -2A$

Q2

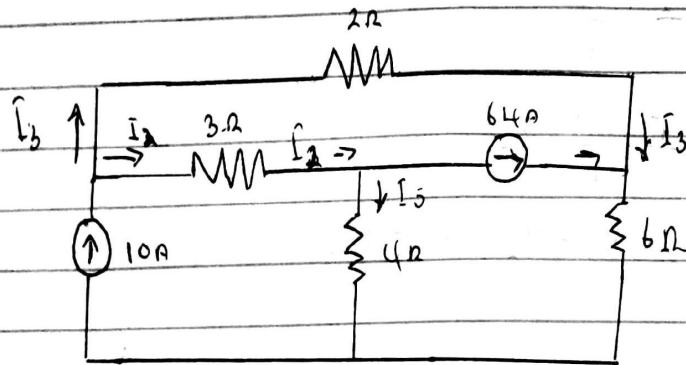

$$I_1 = I_2 + I_5$$

$$10 = \frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{2}$$

$$10 = (V_1 - V_2) \frac{2}{3} + (V_1 - V_3) \frac{1}{2}$$

$$60 = -2V_2 + 2V_1 + 3V_1 - 3V_3$$

$$60 = 5V_1 - 2V_2 - 3V_3 \quad \dots (1)$$

from node 2

$$I_2 = I_3 + I_4$$

$$\frac{V_1 - V_2}{3} = \frac{V_2}{6} + 6V$$

$$\frac{V_1 - V_2}{3} = \frac{V_2}{4} = 64$$

$$\frac{4V_1 - 4V_2 - 3V_2}{12} = 64$$

$$\frac{4V_1 - 7V_2}{12} = 64$$

$$4V_1 - 7V_2 = 768$$

from node b

$$I_4 + I_5 = I_6$$

$$64 + \frac{V_2 - V_3}{2} = \frac{V_3}{6}$$

$$64 = \frac{V_3}{6} - \frac{(V_1 - V_3)}{2}$$

$$64 = \frac{V_3 - 3V_1 + 3V_3}{6}$$

$$384 = 4V_3 - 3V_1 \dots (3)$$

$$60 = 5V_1 - 2V_2 - 3V_3$$

$$268 = 4V_1 - 7V_2 + 0V_3$$

$$384 = -3V_1 + 0V_2 + 4V_3$$

Solve Simultaneously

$$V_1 = 80V \quad V_2 = -64V \quad V_3 = 156V$$