


# Circuit theory

Oloegun Chioke Fortune

17123021062

Computer Engineering

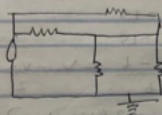- ① Find the voltage of node 1, 2 and 3 in the circuit below



Node 1 KCL

$$10 = i_1 + i_2 \Rightarrow 10 = \frac{V_1 - V_3}{3} + \frac{V_1 - V_2}{2}$$

multiply through by 6

$$60 = 3(V_1 - V_3) + 2(V_1 - V_2)$$

$$60 = 3V_1 = 3V_3 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 3V_3 - 2V_2 = 0$$

At node 2 KCL

$$i_2 = i_3 + 6A$$

$$6A = i_2 - i_3$$

$$6A = \frac{V_1 - V_2}{3} - \frac{V_2 - 0}{4}$$

multiply through by 7

$$2680 = 4(V_1 - V_2) - 3(V_2 - 0)$$

$$768 = 4V_1 - 7V_2 \quad \text{--- (2)}$$

Node 3 kcl

$$64 + i_1 = 13$$

$$64 = 15 - 14$$

$$64 = \frac{V_3 - 6}{6} - \frac{V_1 - V_3}{2}$$

$$384 = V_3 - 3(V_1 - V_3)$$

$$384 = -3V_1 + 4V_3 \quad \text{--- (3)}$$

$$5V_1 - 2V_2 - 3V_3 = 60 \quad \text{--- (1)}$$

$$4V_1 - 7V_2 + 6V_3 = 768 \quad \text{--- (2)}$$

$$-3V_1 + 0V_2 + 4V_3 = 384$$

matrix eq

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta} \quad V_2 = \frac{\Delta_2}{\Delta} \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -2 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$$= 5(-2 \times 0 - 0) + 2(16 + 0) - 3(0 - 21)$$

$$= -140 + 32 + 63$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$= 60(-28 - 0) - 768(-8 - 0) - 384(0 - 21)$$

$$= -1680 + 6144 + 8064$$

$$= 13524$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45} = 80V$$

$$V_2, \Delta_2 = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$$

$$= 5((768 \times 4) - 0) - 4((60 \times 4) - (384 \times 3))$$

$$- 3(0 - (768 \times 3)) = 2880$$


$$V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64V$$

$$V_3 = \begin{vmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ -3 & 0 & 384 \end{vmatrix}$$

$$= 5((-7 \times 384) - 0) - 4((-2 \times 384) - 0) - 3((-2 \times 768) - (-7 \times 60)) = -7020$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{-45} = 156V$$
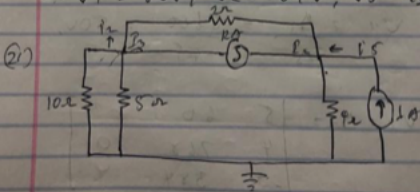
$$\therefore V_1 = 80V, V_2 = -64V, V_3 = 156V$$





Node 1 KCL

$$i_1 = i_2 + i_3 + i_4$$

$$\frac{V_0 - V_1}{10} = \frac{V_1 - V_2}{2} + 12 + \frac{V_1 - V_2}{5}$$

$$0 - V_1 = 5(V_1 - V_2) + 120 + 2(V_1 - 0)$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 2V_1$$

$$+20 = -8V_1 + 5V_2 \quad \text{--- (i)}$$

Node 2

$$i_5 + i_2 + i_3 = 16$$

$$\frac{12 + V_1 - V_2}{2} + 6 = \frac{V_2 - 0}{4}$$

$$96 + 4(V_1 - V_2) + 48 = 2(V_2)$$

$$144 + 4V_1 - 4V_2 + 48 = 2V_2$$

$$144 = -4V_1 + 6V_2 \quad \text{--- (ii)}$$

Using Elimination method

$$120 = -8V_1 + 5V_2 \quad \text{--- (i)} \times 4$$

$$244 = -4V_1 + 6V_2 \quad \text{--- (ii)} \times 8$$

$$-480 = 32V_1 + 20V_2 \quad \text{--- (iii)}$$

$$-1152 = 32V_1 - 48V_2 \quad \text{--- (iv)}$$

Subtract eqn (3) from (4)

$$-672 = 0 = 28V_2$$

$$-6i_2 = -28V_2$$

$$V_2 = \frac{-6i_2}{-28}$$

$$V_2 = 24V$$

Sub  $V_2$  into eq (1)


$$14i_1 - 4V_1 + 6V_2 = 0$$

$$V_1 = \frac{14i_1 - 6(-24)}{-4}$$

$$V_1 = \frac{-14i_1 - 144}{-4} = 0V$$

$$V_1 = 0V, V_2 = 24V$$

$$i_1 = 0A, i_2 = 0A, i_3 = 6A, i_4 = -2A$$

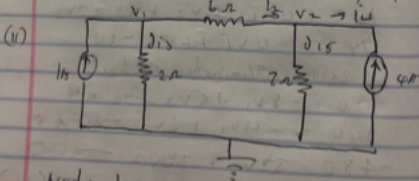

Node 1

$$i_1 = i_2 + i_3$$

$$i_1 = \frac{V_1 - V_2}{2} + \frac{V_1}{2}$$

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \quad \text{--- (1)}$$

Node 2

$$I_2 = 14 + I_3$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

$$7(V_1 - V_2) = 6(4 + V_2)$$

$$7V_1 - 7V_2 = 24 + 6V_2$$

$$\therefore 168 = 7V_1 - 13V_2 \quad \text{--- (2)}$$

from equation (1)

$$V_2 = 4V_1 - 6$$

$$546 = 7V_1 - 13(4V_1 - 6) \quad \text{--- eqn (2)}$$

$$168 = 7V_1 - 52V_1 + 78$$

$$168 = 7V_1 - 52V_1 + 78$$

$$90 = 45V_1$$

$$V_1 = 90 / 45$$

$$V_1 = 2V$$

$$\text{Subs } V_1 = 2 \text{ into eqn (1)}$$

$$6 = 4(-2) - V_2$$

$$6 = -8 - V_2$$

$$V_2 = -8 - 6$$

$$V_2 = -14V$$

$$V_1 = -2V_3, V_2 = -14V$$


Current through the resistors

$$i_2 = \frac{V_1 - V_2}{6} = \frac{-2 - (-14)}{6} = 2A$$

$$i_3 = \frac{V_1}{2} = \frac{-2}{2} = -1A$$

$$i_3 = \frac{V_2}{7} = \frac{-14}{7} = -2A$$

(3)

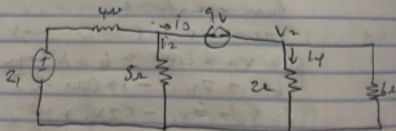


find the current through the  $3\Omega$  and  $2\Omega$  resistors.

Use KCL at node 1

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\frac{V_1 - 2}{4} + \frac{V_1}{3} + \frac{V_2}{6} + \frac{V_2}{2}$$
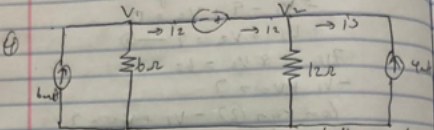
$$i_u = \frac{V_2}{4} = \frac{0.4}{4} = 0.1 \text{ A} \text{ at } 2\Omega$$



Find the nodes of the voltage and the current through the  $6\Omega$  and  $12\Omega$  resistors.

$$\text{For } V_1 - V_2 = 6V \rightarrow i_2$$

at node 1 using KCL

$$6mA = i_1 + i_2$$

$$6mA = \frac{V_1 - 0}{6} + (V_1 - V_2)$$

$$36 = V_1 + 6(V_1 - V_2)$$

$$36 = V_1 + 6V_1 - 6V_2$$

$$36 = 7V_1 - 6V_2 \quad \text{--- (1)}$$

At node 3

$$i_2 = i_3 + i_4$$

$$V_1 - V_2 = 4mA + \frac{V_2 - 0}{12}$$

$$12(V_1 - V_2) = 48 + V_2$$

$$48 = 12V_1 - 12V_2 - V_2$$

$$48 = 12V_1 - 13V_2 \quad \text{--- (2)}$$

Solving  $V_1$  and  $V_2$  simultaneously we have

$$V_1 = 9.5V$$

$$V_2 = 5.1V$$

Current through the  $6\Omega$  resistor

$$i_1 = \frac{V_1}{6} = \frac{9.5}{6} = 1.58A$$

$$i_2 = V_1 - V_2 = 9.5 - 5.1 \\ = 4.4mA$$

Current through  $12\Omega$

$$i_4 = \frac{V_2}{12} = \frac{5.1}{12} = 0.43A$$

$$V_1 = 9.5V$$

$$V_2 = 5.1V$$

$$i_1 = 1.58A$$

$$i_4 = 0.43A$$