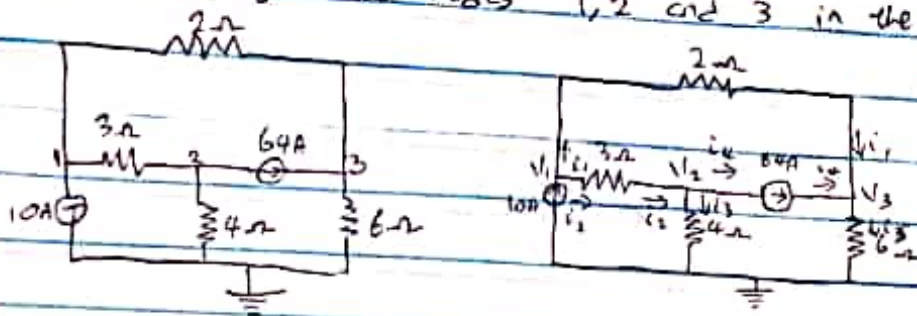


UDE II DANIEL CHAZAM  
 17/Engcot068  
 Electrical/Electronics

1) Find the voltages at nodes 1, 2 and 3 in the circuit below



At node 1, kcl:

$$10 = i_1 + i_2 \Rightarrow 10 = \frac{v_1 - v_2}{2} + \frac{v_1 - v_2}{3}$$

$$60 = 3(v_1 - v_2) + 2(v_1 - v_2)$$

$$60 = 3v_1 - 3v_2 + 2v_1 - 2v_2$$

$$60 = 5v_1 - 5v_2 \quad \dots (i)$$

At node 2, kcl:

$$i_2 = i_3 + 64$$

$$64 = i_2 - i_3$$

$$64 = \frac{v_1 - v_2}{3} - \frac{v_2 - 0}{4}$$

$$768 = 4(v_1 - v_2) - 3(v_2 - 0)$$

$$768 = 4v_1 - 4v_2 - 3v_2$$

$$768 = 4v_1 - 7v_2 \quad \dots (ii)$$

At node 3, kcl

$$64 + i_1 = i_5$$

$$64 = i_5 - i_1$$

$$64 = \frac{v_2 - 0}{6} - \frac{v_1 - v_2}{2}$$

$$384 = v_2 - 3(v_1 - v_2)$$

$$384 = -3v_1 + 4v_2 \quad \dots (iii)$$

$$= 5[(768 \times 4) - 0] - 4[(60 \times 4) - (384 - 3)] - 3[0 - (768 - 3)]$$

$$= 2880$$

$$\therefore V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64V$$

$$\text{For } V_3, \begin{bmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ -3 & 0 & 384 \end{bmatrix}$$


$$= 5[(-7 \times 384) - 0] - 4[(-2 \times 384) - 0] - 3[(-2 \times 768) - (-7 \times 60)]$$

$$= -7020$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{-45} = 156V$$

$$\text{Hence } V_1 = 80V, V_2 = -64V, V_3 = 156V$$

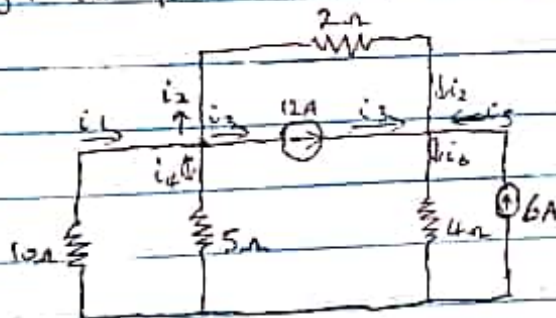2) i) Find the voltages at nodes 1 and 2 and determine the currents flowing through the four resistors in the circuit below.



At node 1, KCL

$$i_1 = i_2 + i_3 + i_4$$

$$\frac{V_0 - V_1}{10} = \frac{V_1 - V_2}{5} + 12 + \frac{V_1 - V_2}{2}$$

$$0 - V_1 = 5(V_1 - V_2) + 120 + 2(V_1 - V_2)$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 2V_1$$

$$120 = -8V_1 + 5V_2 \quad \dots (i)$$

$$6 = -8 - v_2$$

$$v_2 = -8 - 6$$

$$v_2 = -14V$$

$$\therefore v_1 = -2V, v_2 = -14V$$


Current through the resistors

$$i_2 = \frac{v_1 - v_2}{6} = \frac{-2 + 14}{6} = 2A$$

$$i_3 = \frac{v_1}{2} = \frac{-2}{2} = -1A$$

$$i_5 = \frac{v_2}{1} = \frac{-14}{1} = -14A$$

3)

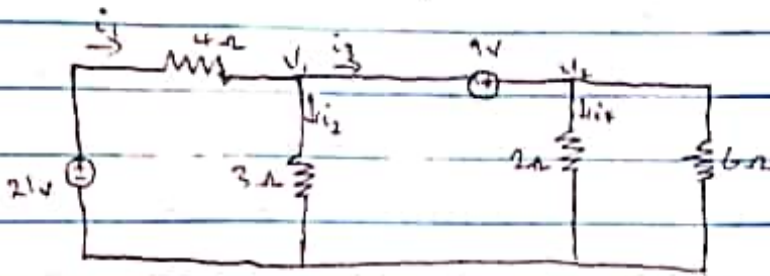

Find the current through the 3Ω and 2Ω resistors

Using KCL at node 1

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\frac{v_1 - 2}{4} + \frac{v_1}{3} + \frac{v_2}{6} + \frac{v_2}{2} = 0$$

$$7v_1 + 8v_2 - 63 = 0 \quad \dots (i)$$

Using KVL for loop 1

$$-v_1 - 9 + v_2 = 0$$

$$-v_1 + v_2 = 9 \quad \dots (ii)$$

$$7v_1 + 8v_2 = 63 \quad \dots (i)$$

$$-v_1 + v_2 = 9 \quad \dots (ii)$$

$$\therefore \text{Let } v_2 = 9 + v_1$$

$$\text{Substitute } v_2 = 9 + v_1 \text{ in eqn (i)}$$



At node 2

$$i_2 = i_3 + i_4$$

$$v_1 - v_2 = 4 \text{ mA} + \frac{v_2 - 0}{12}$$

$$12(v_1 - v_2) = 48 + v_2$$

$$48 = 12v_1 - 12v_2 - v_2$$

$$48 = 12v_1 - 13v_2 \quad \dots (1)$$

Solving  $v_1$  and  $v_2$  simultaneously, we have

$$v_1 = 9.5 \text{ V} \text{ and } v_2 = 5.1 \text{ V}$$

Current through the 6- $\Omega$  resistor

$$i_1 = \frac{v_1}{6} = \frac{9.5}{6} = 1.58 \text{ A}, \quad i_2 = v_1 - v_2 = 9.5 - 5.1 \Rightarrow 4.4 \text{ A}$$

Current through the 12- $\Omega$  resistor

$$i_4 = \frac{v_2}{12} = \frac{5.1}{12} = 0.43 \text{ A}$$

$$\therefore v_1 = 9.5 \text{ V}, \quad v_2 = 5.1 \text{ V}$$

$$i_1 = 1.58 \text{ A}, \quad i_4 = 0.43 \text{ A}$$

$$7V_1 + 8(9 + V_1) = 63$$

$$7V_1 + 72 + 8V_1 = 63$$

$$15V_1 = -9$$

$$V_1 = -0.6V$$

Substitute  $V_1 = -0.6$  in eqn (1)

$$-(-0.6) + V_2 = 9$$

$$0.6 + V_2 = 9$$

$$V_2 = 8.4V$$

$$V_1 = -0.6V \text{ and } V_2 = 8.4V$$

Current through the  $3\Omega$  resistor

$$i_2 = \frac{V_1}{3} = \frac{-0.6}{3} = -0.2A$$

Current through the  $2\Omega$  resistor

$$i_4 = \frac{V_2}{4} = \frac{8.4}{4} = 2.1A$$



Find the node voltages and the currents through the  $6\Omega$  and  $2\Omega$  resistors.

Let assume that  $V_1 = V_2 = 6V \Rightarrow i_2$

At node 1, using Kcl

$$6mA = i_1 + i_2$$


$$6mA = \frac{V_1 - 0}{6} + (V_1 - V_2)$$

$$36 = V_1 + 6(V_1 - V_2)$$

$$36 = V_1 + 6V_1 - 6V_2$$

$$36 = 7V_1 - 6V_2 \quad \dots (1)$$

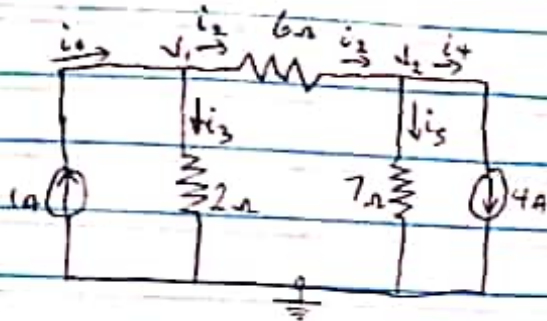ii) Obtain  $V_1$  and  $V_2$  and the currents through the resistors for the circuit in example 11) if the 2A current source was replaced by a 1A current source.



At node 1

$$i_1 = i_2 + i_3$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \quad \text{--- (i)}$$

At node 2

$$i_2 = i_4 + i_5$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

$$7(V_1 - V_2) = 168 + 6V_2$$

$$168 = 7V_1 - 13V_2 \quad \text{--- (ii)}$$

from eqn (i)  $V_2 = 4V_1 - 6$

Substitute  $V_2 = 4V_1 - 6$  in eqn (ii)

$$168 = 7V_1 - 13(4V_1 - 6)$$

$$168 = 7V_1 - 52V_1 + 78$$

$$90 = -45V_1$$

$$V_1 = \frac{90}{-45}$$

$$V_1 = -2V$$

Substitute  $V_1 = -2$  in eqn (i)

$$6 = 4(-2) - V_2$$



Using Cramer's rule

$$5v_1 - 2v_2 - 3v_3 = 60 \quad \text{--- (i)}$$

$$4v_1 - 7v_2 = 768 \quad \text{--- (ii)}$$

$$-2v_1 + 4v_3 = 384 \quad \text{--- (iii)}$$

In matrix representation

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -2 & 0 & 4 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$v_1 = \frac{\Delta_1}{\Delta}, \quad v_2 = \frac{\Delta_2}{\Delta}, \quad v_3 = \frac{\Delta_3}{\Delta}$$

$$\text{where } \Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -2 & 0 & 4 \end{vmatrix}$$

$$\begin{aligned} &= 5(-28-0) + 2(16+0) - 3(0-21) \\ &= -140 + 32 + 63 \\ &= -45 \end{aligned}$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$\begin{aligned} &= 60(-28-0) - 768(-8-0) - 384(0-21) \\ &= -1680 + 6144 - 8064 \\ &= -3600 \end{aligned}$$

$$v_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45} = \underline{\underline{80}}$$

$$\text{For } v_2 \quad \Delta_2 = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -2 & 384 & 4 \end{vmatrix}$$