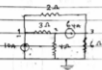


Question 1

Find the Voltages at nodes 1, 2 and 3 in the circuit below.



At node 1, KCL

$$10 = i_1 + i_2 \rightarrow 10 = \frac{V_1 - V_2}{2} + \frac{V_1 - V_2}{3}$$

$$60 = 3(V_1 - V_2) + 2(V_1 - V_2)$$

$$60 = 3V_1 - 3V_2 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 2V_2 + 2V_2 \quad \text{--- (i)}$$

At node 2, KCL

$$i_2 = i_3 + 6$$

$$6 = i_3 - i_2$$

$$6 = \frac{V_1 - V_2}{3} - \frac{V_2 - 0}{6}$$

$$768 = 4(V_1 - V_2) - 3(V_2 - 0)$$

$$768 = 4V_1 - 4V_2 - 3V_2 - 0$$

$$768 = 4V_1 - 7V_2 \quad \text{--- (ii)}$$

At Node 3, KCL

$$64 = i_1 + i_2$$

$$64 = i_2 - i_1$$

$$V \quad 64 = \frac{V_2 - 0}{6} - \frac{V_1 - V_2}{2}$$

$$384 = V_2 - 3(V_1 - V_2)$$

$$384 = -3V_1 + 4V_2 \quad \text{--- (iii)}$$

Using Cramer's Rule.


$$5V_1 - 2V_2 - 3V_2 = 60 \quad \text{--- (i)}$$

$$4V_1 - 7V_2 = 768 \quad \text{--- (ii)}$$

$$-2V_1 - 2V_2 = 204 \quad \text{--- (iii)}$$

Question 4

4)

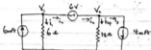

Find the node voltages and the currents through the 6Ω and 12Ω resistors.

Solution

Let say  $V_1 - V_2 = 6V \rightarrow i_1$   
at node 2, using KCL:

$$6A = i_1 + i_2$$

$$6A = \frac{V_1 - 0}{6} + (V_1 - V_2)$$

$$0.036 = V_1 + 6(V_1 - V_2)$$

$$0.036 = V_1 + 6V_1 - 6V_2$$

$$0.036 = 7V_1 - 6V_2 \quad \text{--- (i)}$$

At Node 2:

$$i_3 = i_1 + i_2$$

$$V_1 - V_2 = 4A + \frac{V_2 - 0}{12}$$

$$12(V_1 - V_2) = 0.048 + V_2$$

$$0.048 = 12V_1 - 12V_2 - V_2$$

$$0.048 = 12V_1 - 13V_2 \quad \text{--- (ii)}$$

$$7V_1 - 6V_2 = 0.036 \times 12 \quad \text{--- (i)}$$

$$12V_1 - 13V_2 = 0.048 \times 7 \quad \text{--- (ii)}$$

$$84V_1 - 72V_2 = 0.432 \quad \text{--- (iii)}$$

$$84V_1 - 91V_2 = 0.336 \quad \text{--- (iv)}$$

$$0 + 19V_2 = 0.096$$

$$V_2 = 5.053 \times 10^{-3} V$$

Sub  $V_2$  in eqn (iii)

$$84V_1 - 0.4578 = 0.432$$

$$84V_1 = 0.336 + 0.4578$$

$$V_1 = \frac{0.7938}{84} = 9.44 \times 10^{-3} V$$

$\therefore$  Current through the 6Ω resistor:

$$\frac{V_1 - 21}{4} + \frac{V_1}{3} + \frac{V_1}{6} + \frac{V_1}{2}$$

$$7V_1 + 8V_1 - 63 = 0 \quad \text{--- (i)}$$

Using KVL for loop 2

$$-V_1 - 9 + V_2 = 0$$

$$-V_1 + V_2 = 9 \quad \text{--- (ii)}$$

$$7V_1 + 8V_2 = 63 \quad \text{--- } \times 1$$

$$-V_1 + V_2 = 9 \quad \text{--- } \times 7$$

$$+ 7V_1 + 8V_2 = 63 \quad \text{--- (iii)}$$

$$+ -7V_1 + 7V_2 = 63 \quad \text{--- (iv)}$$

$$0 + 15V_2 = 126$$

$$V_2 = \frac{126}{15} = 8.4V$$

Sub  $V_2$  in eqn (ii)

$$-V_1 + 7(8.4) = 63$$

$$-V_1 + 63 = 63 - 58.8$$

$$-V_1 = 4.2$$

$$V_1 = -0.6V$$


Current through the  $2\Omega$  resistor.

$$i_1 = \frac{V_1}{2} = \frac{-0.6}{2} = -0.3A$$

Current through the  $4\Omega$  resistor.

$$i_2 = \frac{V_2}{4} = \frac{8.4}{4} = 2.1A$$

Question 4

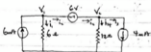

Find the node voltages and the currents through the  $6\Omega$  and  $12\Omega$  resistors.

Sol.  $V_1 = -2$  in eqn (i)

$6 = 4V_1$

$$6 = 4(-2) - V_2$$

$$6 = -8 - V_2$$

$$V_2 = -8 - 6$$

$$= -14V$$

$$\therefore V_1 = -2V, V_2 = -14V$$

Current through the resistor:


$$i_1 = \frac{V_1 - V_2}{6} = \frac{-2 + 14}{6} = 2A$$

$$i_2 = \frac{V_1}{2} = \frac{-2}{2} = -1A$$

$$i_3 = \frac{V_2}{2} = \frac{-14}{2} = -7A$$

Question 2

3)

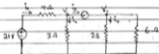

Find the current through the 3 ohm and 2V resistors.

Solution

Using KCL at Node 1

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\frac{V_1 - 2}{4} + \frac{V_1}{3} + \frac{V_2}{6} + \frac{V_2}{2}$$

$$7V_1 + 8V_2 - 63 = 0 \quad \text{--- (1)}$$

Using KVL for loop 2

$$394 = V_2 - 3(V_1 - V_2)$$

$$394 = -3V_1 + 4V_2 \quad \text{--- (5)}$$

Using Cramer's Rule.

$$5V_1 - 2V_2 - 3V_3 = 60 \quad \text{--- (1)}$$

$$4V_1 - 7V_2 = 749 \quad \text{--- (2)}$$

$$-3V_1 + 4V_2 = 394 \quad \text{--- (3)}$$

In Matrix Representation.

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 749 \\ 394 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta}, \quad V_2 = \frac{\Delta_2}{\Delta}, \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\text{where } \Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 0 \end{vmatrix}$$

$$= 5(-17-0) + 2(16+0) - 3(0-21) \\ = -140 + 32 + 63 \\ = -75$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 749 & -7 & 0 \\ 394 & 0 & 0 \end{vmatrix}$$

$$= 60(-21-0) - 769(-9-0) - 394(0) \\ = -1260 + 6921 - 0 \\ = -360$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-360}{-75} = 4.8V$$

Scanned with CamScanner

$$V_2 = \frac{\Delta_2}{\Delta} = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 749 & 0 \\ -3 & 394 & 0 \end{vmatrix}$$

$$= 5(749 \cdot 0) - 4(2+0 + 1152) - 3(0 + 294)$$

At Node 1, KCL:  $\dots$

$$i_1 = i_2 + i_3 + i_4$$

$$\frac{V_1 - V_2}{10} = \frac{V_1 - V_2}{2} + 12 + \frac{V_1 - V_2}{5}$$

$$0 - V_1 = 5(V_1 - V_2) + 120 + 2(V_1 - 0)$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 2V_1$$

$$120 = -8V_1 + 5V_2 \quad \text{--- (i)}$$

At Node 2:

$$i_1 + i_2 + i_3 = i_4$$

$$12 + \frac{V_1 - V_2}{2} + 6 = \frac{V_2 - 0}{4}$$

$$96 + 4(V_1 - V_2) + 48 = 2(V_2)$$

$$144 + 4V_1 - 4V_2 = 2V_2$$

$$144 = -4V_1 + 6V_2 \quad \text{--- (ii)}$$

Using Elimination Method:

$$120 = -8V_1 + 5V_2 \quad \times 2$$

$$144 = -4V_1 + 6V_2 \quad \times 4$$

$$240 = -16V_1 + 10V_2 \quad \text{--- (iii)}$$

$$576 = -16V_1 + 24V_2 \quad \text{--- (iv)}$$

$$\frac{336}{816} = 0 + 14V_2$$

$$V_2 = 24V$$

Sub  $V_2$  in eqn (i)

$$120 = -16V_1 + 240$$

$$V_1 = 0V$$

$$\therefore V_1 = 0V, V_2 = 24V$$

$$i_1 = 0A, i_2 = 0A, i_3 = 6A, i_4 = -12A$$

- 21: Obtain  $V_1$  and  $V_2$  and the currents through the resistors for the circuit in example (i) if the 2A current source was replaced by a 2A current 2A.



$$12V_1 - 13V_2 = 0.048 \times 7$$

$$84V_1 - 72V_2 = 0.432 \quad \text{--- (1)}$$

$$84V_1 - 91V_2 = 0.336 \quad \text{--- (2)}$$

$$0 + 19V_2 = 0.096$$

$$V_2 = 5.053 \times 10^{-3} \text{ V}$$

Scanned with CamScanner

Sub  $V_2$  in eqn (1)

$$84V_1 - 0.4378 = 0.336$$

$$84V_1 = 0.336 + 0.4378$$

$$V_1 = \frac{0.7738}{84} = 9.214 \times 10^{-3} \text{ V}$$

$\therefore$  Current through the  $6\Omega$  resistor:

$$i_1 = \frac{V_1}{6} = \frac{9.214 \times 10^{-3}}{6} = 1.539 \times 10^{-3} \text{ A}$$

Current through the  $12\Omega$  resistor:

$$i_2 = \frac{V_2}{12} = \frac{5.053 \times 10^{-3}}{12} = 4.212 \times 10^{-4} \text{ A}$$

$$V_1 = 9.214 \times 10^{-3} \text{ V}$$

$$V_2 = 5.053 \times 10^{-3} \text{ V}$$

$$i_1 = 1.539 \times 10^{-3} \text{ A}$$

$$i_2 = 4.212 \times 10^{-4} \text{ A}$$

Scanned with CamScanner

$$V_1 = \Delta_1 = \begin{vmatrix} 5 & 60 & -3 \\ -4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$$

$$= 5(768 - 0) - 4(240 + 1152) - 3(0 + 3072)$$

$$= 2880$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{2880}{-45} = -64V$$

$$V_2 = \Delta_2 = \begin{vmatrix} 5 & -2 & 60 \\ -4 & -7 & 768 \\ -3 & 0 & 384 \end{vmatrix}$$

$$= 5((-7 \times 384) - 0) - 4((-3 \times 384) - 0) - 3((-3 \times 768) - (-7 \times 60))$$

$$= -7020$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{-7020}{-45} = 156V$$

$$\therefore V_1 = 90V, V_2 = -64V, V_3 = 156V$$

### Question 2

2. Find the voltages at nodes 1 and 2 and determine the current flowing through the 10A resistor in the circuit below.



At Node 1, KCL:  $i_1 = i_2 + i_3 + i_4$


$$i_1 = i_2 + i_3 + i_4$$

$$\frac{V_1 - V_2}{10} = \frac{V_2 - V_3}{5} + 10 + \frac{V_1 - V_3}{2}$$

$$0 - V_1 = 5(V_2 - V_3) + 120 + 2(V_1 - V_3)$$



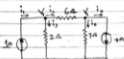210 Obtain  $V_1$  and  $V_2$  and the currents through the resistors for the circuit in example (5) if the  $2A$  current source was replaced by a  $2A$  current  $2A$ .



Solution

At Node 1

$$i = i_1 + i_2$$

$$2 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$6 = 8(V_1 - V_2) + 3V_1$$

$$6 = 4V_1 - V_2 \quad \dots \text{--- (i)}$$

At Node 2

$$i_3 = i_4 + i_5$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

$$7(V_1 - V_2) = 168 + 6V_2$$

$$168 = 7V_1 - 13V_2 \quad \dots \text{--- (ii)}$$

From eqn (i),  $V_2 = 4V_1 - 6$

Sub  $V_2$  in eqn (ii)

$$168 = 7V_1 - 13(4V_1 - 6)$$

$$168 = 7V_1 - 52V_1 + 78$$

$$168 - 78 = 7V_1 - 52V_1$$

$$90 = -45V_1$$

$$V_1 = -2V$$

Sub  $V_1 = -2$  in eqn (i)

$$6 = 4V_1 - V_2$$

$$6 = 4(-2) - V_2$$

$$6 = -8 - V_2$$

$$V_2 = -8 - 6$$

$$= -14V$$