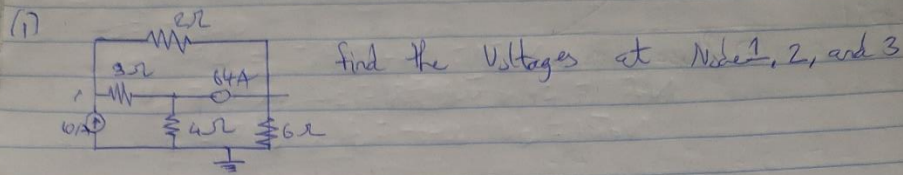


Ide Alexius Azibane
 Computer Engineering
 17 (EN6027032)
 EEE 322 Assignment



from Node 1, Applying KCL
 $10 = I_1 + I_2 = 10 = \left(\frac{V_1 - V_2}{2}\right) + \left(\frac{V_1 - V_2}{3}\right)$

~~$60 = 3(V_1 - V_2) + 2(V_1 - V_2)$~~

~~$10 = \frac{3(V_1 - V_2) + 2(V_1 - V_2)}{6}$~~

$60 = 3(V_1 - V_2) + 2(V_1 - V_2)$

$60 = 3V_1 - 3V_2 + 2V_1 - 2V_2$

$60 = 5V_1 - 2V_2 - 3V_3$ ——— eqn ①

Then from Node 2, (KCL)

$I_2 = I_3 + 64A$

$64 = I_2 - I_3$ (since $I_2 = \frac{V_1 - V_2}{3}$ & $I_3 = \frac{V_2 - 0}{4}$)

$64 = \left(\frac{V_1 - V_2}{3}\right) - \left(\frac{V_2 - 0}{4}\right)$

$64 = \frac{4(V_1 - V_2) - 3(V_2 - 0)}{12}$

$768 = 4V_1 - 4V_2 - 3V_2$

$768 = 4V_1 - 7V_2$ ——— eqn ②

Node 3

$64 + I_1 = I_5$

$$64 = I_5 - I_1$$

$$64 = \frac{V_3 - 0}{6} - \frac{V_1 - V_3}{2}$$

$$64 = \frac{V_3 - 0 - 3(V_1 - V_3)}{6}$$

$$384 = V_3 - 3V_1 + 3V_3$$

$$384 = -3V_1 + 4V_3 \quad \text{--- (3)}$$

1, 2, and 3

Applying Cramer's Rule

$$5V_1 - 2V_2 - 3V_3 = 60 \quad \text{--- (1)}$$

$$4V_1 - 7V_2 + 0 = 768 \quad \text{--- (2)}$$

$$-3V_1 + 0 + 4V_3 = 384 \quad \text{--- (3)}$$

Matrix form

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \Delta_1/\Delta, \quad V_2 = \Delta_2/\Delta, \quad V_3 = \Delta_3/\Delta$$

$$\Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$$= 5(-28) + 2(16) - 3(-21)$$

$$\Delta = -140 + 32 + 63$$

$$\Delta = -45$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ -768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$\Delta_1 = 60(-28) + 768(-8) + 384(-21)$$

$$\Delta_1 = -1680 + 6144 - 8064$$

$$= -3600$$

$$\therefore V_1 = \Delta_1/\Delta = -3600/-45 = 80V$$

$$V_2 \Delta_2 = \begin{vmatrix} 5 & 60 & -3 \\ -4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$$

$$= 5(3072) - 4(240 + 1152) - 3(2304)$$

$$= 15360 - 4320 - 7056$$

$$= 3984$$

$$V_2 = \Delta_2/\Delta = 3984/-45 = -88.53V$$

$$\text{for } V_3, \begin{array}{c|ccc} + & 5 & -2 & 60 \\ - & 4 & -7 & 708 \\ + & -3 & 0 & 384 \end{array}$$

$$= 5(-2688) - 4(-768) - 3(-1536 + 420)$$


$$\Delta_3 = -7020$$

$$V_3 = \Delta_3 / \Delta = -7020 / -45 = 156V$$

$$\therefore V_1 = 80V, V_2 = -64V, V_3 = 156V$$

$$V_1 = 80V, V_2 = -64V, V_3 = 156V$$

20.1)

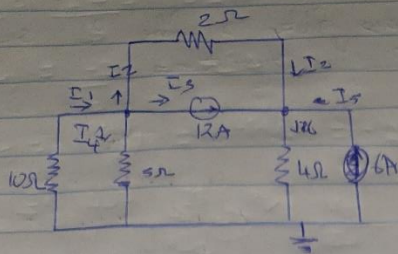

$$(1) I_1 = I_2 + I_3 + I_4$$

$$\frac{V_2 - V_1}{10} = \frac{V_1 - V_2}{2} + 12 + \frac{V_1 - V_2}{5}$$

$$0 - V_1 = 5(V_1 - V_2) + 120 + 2(V_1 - 0)$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 2V_1$$

$$120 = -8V_1 + 5V_2 \quad \text{--- (i)}$$

$$\text{Node 2 } (I_3 + I_2 + I_5 = I_6)$$

$$12 + \frac{V_1 - V_2}{2} + 6 = \frac{V_2 - 0}{4}$$

$$24 + V_1 + V_2 + 12 = \frac{V_2 - 0}{2}$$

$$36 + V_1 + V_2 = \frac{V_2 - 0}{2}$$

$$72 + 2V_1 + 2V_2 = V_2 \quad \text{--- (ii)}$$

$$72 + 2V_1 = V_2 - 2V_2$$

$$72 = 2V_1 - V_2$$

$$2V_1 - 2V_2 - V_2 = -72$$

$$2V_1 - 3V_2 = -72 \quad \text{--- (iii)}$$

$$18 + \frac{V_1 - V_2}{2} = \frac{V_2 - 0}{4}$$

$$\frac{V_1 - V_2}{2} = \frac{V_2}{4} - 18$$

$$\frac{V_1 - V_2}{2} - \frac{V_2}{4} = -18$$

$$\frac{2(V_1 - V_2) - V_2}{4} = -18$$

Using elimination method

$$120 = -8V_1 + 5V_2 \quad \text{--- (i)}$$

$$-72 = 2V_1 - 3V_2 \quad \text{--- (ii) } \times 4$$

$$120 = -8V_1 + 3V_2$$

$$-288 =$$

$$288 = -8V_1 + 12V_2$$

$$120 = -8V_1 + 3V_2$$

$$168 = 0 + 7V_2$$

$$V_2 = 24V$$

put V_2 into eqn (1)

$$120 = -8V_1 + 3(24)$$


$$120 = -8V_1 + 72$$

$$V_1 = 0$$

$$V_1 = 0, V_2 = 24V$$

$$I_1 = 0A, I_2 = 0A, I_3 = 6A, I_4 = 12A$$

(ii)

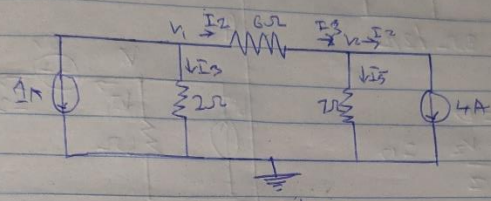

Node 1

$$I_1 = I_2 + I_3$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$1 = \frac{V_1 - V_2 + 3V_1}{6}$$

$$6 = 4V_1 - V_2 \quad \text{--- (i)}$$

Node 2

$$I_2 = I_4 + I_3$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7} = \frac{V_1 - V_2 - 28}{7}$$

$$7(V_1 - V_2) - 6V_2 = 42$$

$$168 = 7V_1 - 13V_2 \quad \text{--- (ii)}$$

× eqn by 13 = $78 = 52V_1 - 13V_2$ --- (iii)

∴ subtract eqn (iii) from (ii)

$$78 = 52V_1 - 13V_2$$

$$168 = 7V_1 - 13V_2$$

$$-90 = 45V_1 + 0$$

$$V_1 = -2V$$

Put $V_1 = -2V$ into eqn (ii)

$$\rightarrow 168 = 7(-2) - 13V_2$$

$$168 = -14 - 13V_2$$

$$182 = -13V_2$$


$$V_2 = -14V$$

Current through resistors

$$I_2 = \frac{-2+14}{6} = 2A$$

$$I_3 = \frac{-2}{2} = -1A$$

$$I_5 = \frac{14}{7} = 2A$$

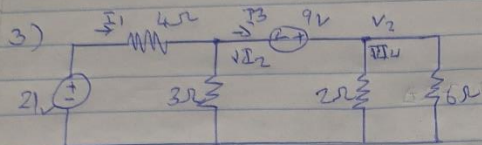

Find Current through $3\Omega/2\Omega$

Applying KCL

$$I_1 + I_2 + I_3 + I_4 = 0$$

$$\frac{V_1 - 2}{4} + \frac{V_1}{3} + \frac{V_2}{6} + \frac{V_2}{2} = 0$$

$$7V_1 + 8V_2 = 63 \quad \text{--- (i)}$$

KVL for Loop 1

$$-V_1 - 9 + V_2 = 0$$

$$-V_1 + V_2 = 9 \quad \text{--- (ii)}$$

Simultaneously

$$\therefore 7V_1 + 8V_2 = 63 \quad \text{--- (i)}$$

$$-V_1 + V_2 = 9 \quad \text{--- (ii)}$$

From eqn 2

$$V_2 = 9 + V_1 \quad \text{--- (*)}$$

put eqn (*) in (i)

$$7V_1 + 8(9 + V_1) = 63$$

$$7V_1 + 72 + 8V_1 = 63$$

$$15V_1 = -9$$

$$V_1 = -0.6V$$

put $V_1 = -0.6V$ in eqn (*)

$$V_2 = 9 - 0.6V$$

$$V_2 = 8.4V$$

$$V_1 = -0.6V$$

$$V_2 = 8.4V$$


Current through 3Ω resistor

$$I_2 = \frac{V_1}{3} = \frac{-0.6}{3} = -0.2A$$

Current through the 2Ω resistor

$$I_4 = \frac{V_2}{2} = \frac{8.4}{2} = 4.2A$$

(A)

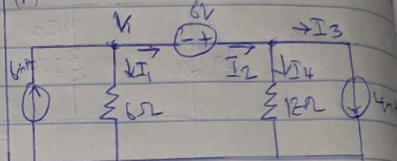

Find Voltage and Current through

the 12Ω and 6Ω resistor

Soln

At Node 1: KCL

$$6mA = I_1 + I_2$$

$$6 = \frac{V_1}{6} + \frac{V_1 - V_2}{6}$$

$$36 = V_1 + 6(V_1 - V_2)$$

$$36 = 7V_1 - 6V_2 \quad \text{--- (i)}$$

Node 2

$$I_2 = I_3 + I_4$$

$$V_1 - V_2 = 4mA + \frac{V_2}{12}$$

$$12(V_1 - V_2) = 48 + V_2$$

$$12V_1 - 12V_2 = 48 + V_2$$

$$12V_1 - 13V_2 = 48 \quad \text{--- (ii)}$$

4) Solving V_1 and V_2
 $V_1 = 9.5$, $V_2 = 5.1V$

resistor
0.2A

Current through 6Ω resistor
$$I_1 = \frac{V_1}{6} = \frac{9.5}{6} = 1.58A$$

$$I_2 = V_1 - V_2 = 9.5 - 5.1 = 4.4A$$

2 resistor
2.1V

Current through 12 resistor
$$I_4 = \frac{V_2}{12} = \frac{5.1}{12} = 0.43A$$

$$\therefore V_1 = 9.5V, V_2 = 5.1V,$$

$$I_1 = 1.58A, I_4 = 0.43A$$

ES

4mA

through