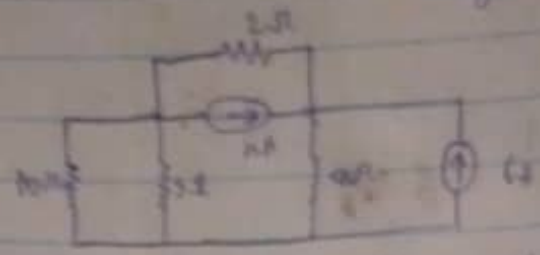




Circuit Theory

1)



- i. Find the voltage at node 1 w.r.t 2
- ii. Find the current flowing through the 10Ω resistor

Solution

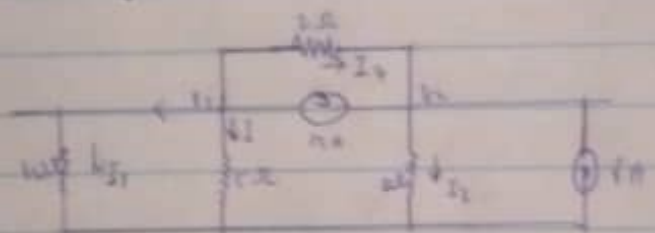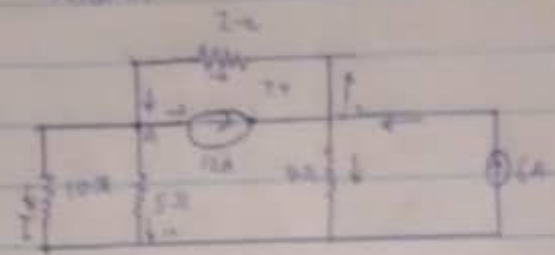

From node 1, using Kcl

$$I_1 + I_2 + I_3 = -12A$$

$$I_1 = \frac{V_1 - 0}{10} = \frac{V_1}{10}$$

$$I_2 = \frac{V_1 - 0}{2} = \frac{V_1}{2}$$

$$I_3 = \frac{V_1 - V_2}{5}$$

$$\frac{V_1}{10} + \frac{V_1}{2} + \frac{V_1 - V_2}{5} = -12$$

$$V_1 \left(\frac{1}{10} + \frac{2}{10} + \frac{2(V_1 - V_2)}{10} \right) = -12$$

$$\frac{V_1 (2V_1 + 3V_1 - 2V_2)}{10} = -12$$

$$\frac{5V_1 - 2V_2}{10} = -12$$

$$\Rightarrow 5V_1 - 2V_2 = -120$$

Applying KCL in node 2.

$$I_4 + I_6 + I_2 = 0$$

$$I_4 + I_2 = -I_6$$

$$I_4 = \frac{V_1 - V_2}{2} \quad \text{and} \quad I_2 = \frac{V_2 - 0}{4} = \frac{V_2}{4}$$

$$\Rightarrow \frac{V_1 - V_2}{2} + \frac{V_2}{4} = -14$$

$$\frac{2(V_1 - V_2) + V_2}{4} = -14$$

$$\frac{2V_1 - 2V_2 + V_2}{4} = -14$$

$$\frac{2V_1 - V_2}{4} = -14$$

$$2V_1 - V_2 = -72 \quad \dots \text{(n7)}$$

$$8V_1 - 5V_2 = -120$$

$$2V_1 - 3V_2 = -72$$

Using calculator to solve simultaneously

$$V_1 = 0 \text{ V} \quad \& \quad V_2 = 24 \text{ V}$$


$$I_4 = \frac{V_1}{10} = \frac{0}{10} = 0 \text{ A}$$

$$I_6 = \frac{V_2}{5} = \frac{24}{5} = 4.8 \text{ A}$$


$$I_2 = \frac{V_2}{4} = \frac{24}{4} = 6 \text{ A}$$

$$I_3 = \frac{V_2 - V_1}{2} = \frac{24 - 0}{2} = \frac{24}{2} = 12 \text{ A}$$

2.)

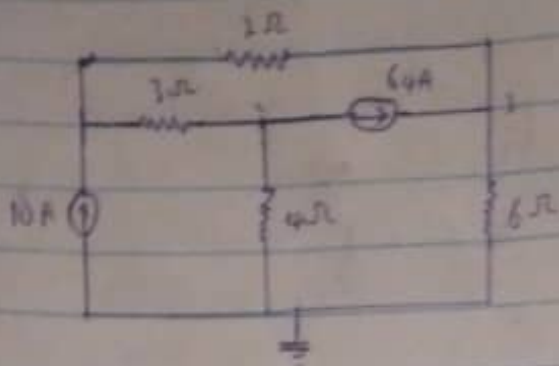

Find the voltage at node 1 & 2
solution

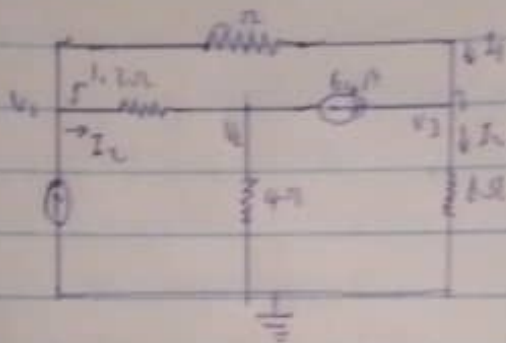

at node 1. using KCL $10 = I_1 + I_2$
 $10 = \frac{v_1 - v_2}{3} + \frac{v_1 - v_2}{2}$

at node 2; using KCL: $I_2 = I_3 + I_4$
 $\frac{v_1 - v_2}{2} = 6 + \frac{v_2 - v_3}{6}$

at node 3 using KCL: $I_4 = I_5 + I_6$
 $\frac{v_2 - v_3}{6} = 6 + \frac{v_3 - 0}{6}$

$$10 = \frac{2}{3}v_1 - \frac{1}{3}v_2 - \frac{1}{2}v_2$$

$$10 = \frac{1}{3}v_1 - \frac{1}{2}v_2 + 6$$

$$4 = \frac{1}{3}v_1 - \frac{1}{2}v_2$$

using matrix method

$$\begin{bmatrix} 10 \\ 6 \\ 6 \end{bmatrix} = \begin{bmatrix} \frac{1}{3} & -\frac{1}{2} & 0 \\ \frac{1}{3} & -\frac{1}{2} & 0 \\ 0 & 0 & \frac{1}{6} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

$v_1 = 15V$

$$B^{-1}P = \begin{bmatrix} 3.73 & -2.13 & 2.4 \\ 2.13 & -2.93 & 1.6 \\ 2.4 & -1.6 & 3.6 \end{bmatrix} \begin{bmatrix} 16 \\ 64 \\ 64 \end{bmatrix}$$

$$C = \begin{bmatrix} 80 \\ -64 \\ 156 \end{bmatrix}$$

1. $V_1 = 80V, V_2 = -64V, V_3 = 156V$