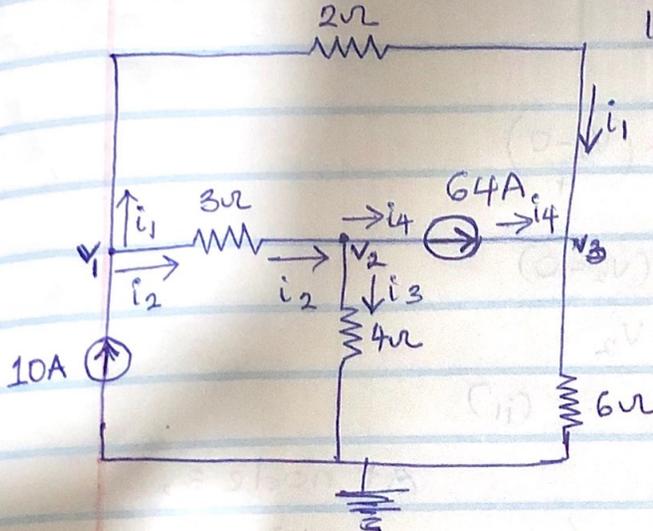


NODAL ANALYSIS EEE 322
 ASSIGNMENT

ADEROJU OLUWARIKEMI ADEBOSOLA COMPUTER ENG

18LENG021102 - N = 40



At node 1,

$$10 = i_1 + i_2$$

$$10 = \frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{3}$$

$$\frac{3(V_1 - V_2) + 2(V_1 - V_3)}{6}$$

$$10 = 3(V_1 - V_3) + 2(V_1 - V_2)$$

$$10 = 3V_1 - 3V_3 + 2V_1 - 2V_2$$

~~$$10 = 5V_1 - 5V_2$$~~

$$10 = 3V_1 - 3V_3 + 2V_1 - 2V_2$$

$$10 = 5V_1 - 2V_2 - 3V_3 \dots (1)$$

At node 2, ~~$i_2 = i_3 + i_4$~~

$$i_2 = i_3 + 64 ; 64 = i_2 - i_3$$

$$64 = \frac{V_1 - V_2}{3} + \frac{V_2 - 0}{4}$$

$$64 \times 12 = 12 \frac{(V_1 - V_2)}{3} + 12 \left(\frac{V_2 - 0}{4} \right)$$

$$768 = 4(V_1 - V_2) + 3(V_2 - 0)$$

$$768 = 4V_1 - 4V_2 + 3V_2$$

$$768 = 4V_1 - V_2 \dots (i)$$

At node 3,

~~$$i_1 + i_4 = i_3$$~~

~~$$\frac{V_1 - V_3}{2} + 64 = \frac{V_2 - 0}{4}$$~~

~~$$\frac{V_1 - V_3}{2} - \frac{V_2 - 0}{4} = -64$$~~

~~divide through by 2~~

~~$$\frac{V_1 - V_3}{1} - \frac{V_2 - 0}{2} = -32$$~~

At node 3,

$$i_1 + i_4 = i_3$$

$$\frac{V_1 - V_2}{2} + 64 = \frac{V_3 - 0}{6}$$

$$\frac{V_1 - V_2}{2} - \frac{V_3 - 0}{6} = -64$$

$$\frac{V_1 - V_2}{2} - \frac{V_3}{6} = -64$$

multiply through by 6

$$\left(\frac{V_1 - V_2}{2} \right) 3 - \left(\frac{V_3}{6} \right) 6 = -64 \times 6$$

$$(V_1 - V_2) 3 - V_3 = -384$$

$$3V_1 - 3V_2 + 384 = V_3$$

$$3V_1 - 4V_3 = 384$$

$$3V_1 - 4V_3 = 384; 4V_3 - 3V_1 = 384 \dots (ii)$$

Using matrix rule

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$= 60(-28) + 2(3072) - 3(2688)$$

$$\Delta_1 = -3600$$

therefore, $V_1 = 80V$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{+45} = 80V$$

$$V_2 = -64V$$

$$V_3 = 156V$$

$$\Delta_{22} = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ 3 & 384 & 4 \end{vmatrix}$$

$$= 5(3072) - 60(16) - 3(3840)$$


$$\Delta_{22} = 2880$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64V$$

$$\Delta_3 = \begin{vmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ 3 & 0 & 384 \end{vmatrix} = 5(-2688) + 2(3840) - 60(-21)$$
$$\Delta_3 = -7020$$
$$V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{-45} = 156$$



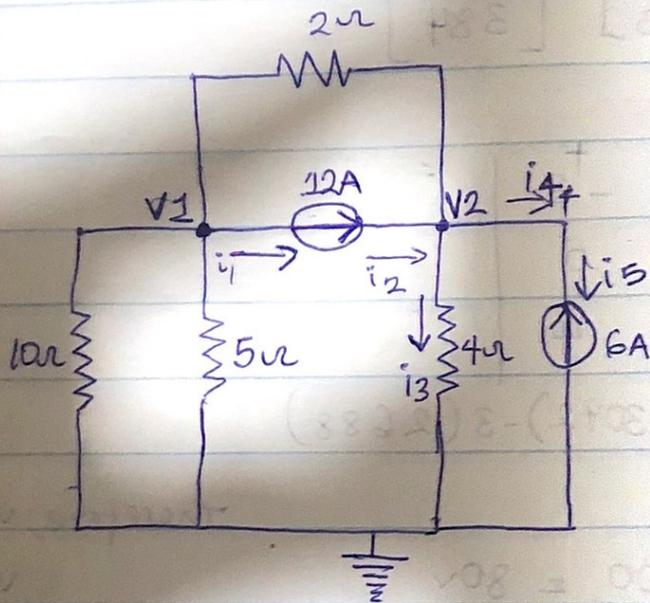i) Find the voltages at nodes 1 and 2 and determine the currents flowing through the four resistors in the circuit below.



At node 1

$$\frac{-V_1 - V_1}{10} = 12A + \frac{V_1 - V_2}{2}$$
$$\frac{-V_1 + 2V_1}{10} = 12A + \frac{V_1 - V_2}{2}$$

$$\cancel{10} \left(\frac{-V_1 + 2V_1}{\cancel{10}} \right) = \cancel{12A} + \cancel{10} \left(\frac{V_1 - V_2}{2} \right)$$

$$\cancel{10} V_1 + 2V_1 - 5V_1 + 5V_2 = 120A$$
$$-6V_1 + 7V_2 = 120$$

$$i_1 = i_2 + i_3 + i_4$$

$$10 \left(\frac{V_0 - V_1}{10} \right) = \left(\frac{V_1 - V_2}{2} \right) + 120 + \left(\frac{V_1 - V_2}{5} \right)$$

$$V_0 - V_1 = 5V_1 - 5V_2 + 120 + 2V_1 - 2V_2$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 2V_1$$

$$120 = -8V_1 + 5V_2 \quad (i)$$

Node 2,

$$i_3 + i_2 + i_5 = i_3$$

$$12 + \frac{V_1}{2} - \frac{V_2}{4} + 6 = \frac{V_2}{4} - 0$$

$$12 + \frac{V_1}{2} - \frac{V_2}{4} + 6 = \frac{V_2}{4} - 0$$

Multiply through by 8

$$(12 \times 8) + (V_1 \times 8) + (6 \times 8) = (V_2 \times 8) - 0$$

$$96 + 8V_1 + 48 = 8V_2 - 0$$

$$144 + 8V_1 - 8V_2 = 0 \quad (ii)$$

$$144 + 8V_1 - 8V_2 = 0 \quad (ii)$$

$$144 + 8V_1 - 8V_2 = 0 \quad (ii)$$

$$144 + 8V_1 - 8V_2 = 0 \quad (ii)$$

$$144 + 8V_1 - 8V_2 = 0 \quad (ii)$$

$$144 + 8V_1 - 8V_2 = 0 \quad (ii)$$

$$144 + 8V_1 - 8V_2 = 0 \quad (ii)$$

$$144 + 8V_1 - 8V_2 = 0 \quad (ii)$$

Class-work

Node 1

$$i_1 = i_2 + i_3$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \quad \dots (1)$$

Node 2

$$i_2 = i_4 + i_5$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

$$7(V_1 - V_2) = 168 + 6V_2$$

$$168 = 7V_1 - 13V_2 \quad \dots (2)$$

$$V_2 = 4V_1 - 6 \quad \dots (3)$$

Substitute V_2 into eqn(2)

$$168 = 7V_1 - 13(4V_1 - 6)$$


$$168 = 7V_1 - 52V_1 + 78$$

$$168 - 78 = -45V_1$$

$$90 = -45V_1$$

$$V_1 = -2V$$

$$V_2 = 4(-2) - 6 = -14V$$

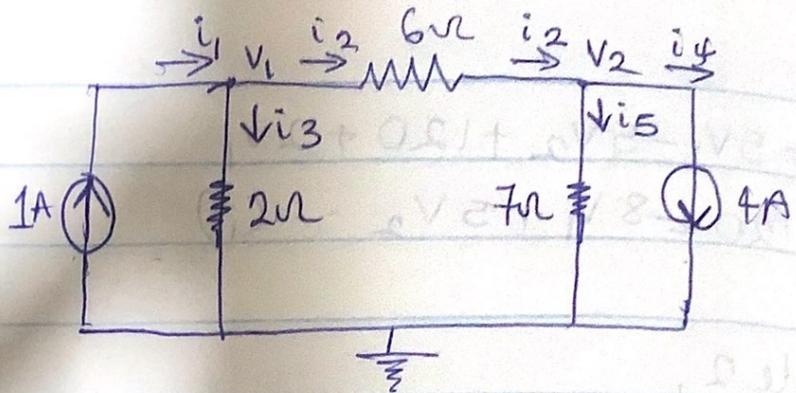

Therefore, the current across the resistor

$$i_2 = \frac{V_1 - V_2}{6} = \frac{-2 - (-14)}{6} = \frac{12}{6} = 2A$$

$$i_3 = \frac{V_1}{2} = \frac{-2}{2} = -1A$$

$$i_5 = \frac{V_2}{7} = \frac{-14}{7} = -2A$$