
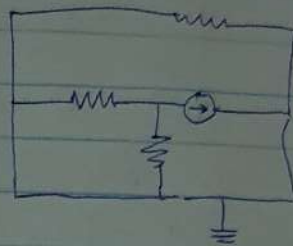


Emmanuel Elegbe

17/ENG021020

COMPUTER ENGINEERING

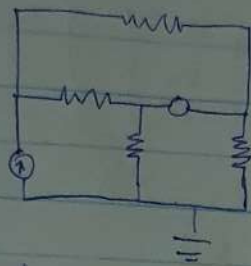1) Find the voltages at nodes 1, 2 and 3 in the circuit below



At node 1 kcl:

$$10 = i_1 + i_2 \Rightarrow 10 = \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{3}$$

$$\Rightarrow 60 = 3(V_1 - V_3) + 2(V_1 - V_2)$$

$$60 = 3V_1 - 3V_3 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 2V_2 - 3V_3 \dots (i)$$

At node 2 kcl:

$$i_2 = i_3 + 64$$

$$64 = i_2 - i_3$$

$$64 = \frac{V_1 - V_2}{4} - \frac{V_2 - 0}{3}$$

$$768 = 4(V_1 - V_2) - 3(V_2 - 0)$$

$$768 = 4V_1 - 4V_2 - 3V_2$$

$$768 = 4V_1 - 7V_2 \dots (ii)$$

At node 3, kcl

$$64 + i = i_c$$

$$64 = i_5 - i$$

$$64 = \frac{V_3 - 0}{6} - \frac{V_1 - V_3}{2}$$

$$384 = V_3 - 3(V_1 - V_3)$$

$$384 = -3V_1 + 4V_3 \dots (iii)$$

using Cramer's Rule

$$5V_1 - 2V_2 - 3V_3 = 60 \dots (i)$$

$$4V_1 - 7V_2 = 768 \dots (ii)$$

$$-3V_1 + 4V_3 = 384 \dots (iii)$$

in matrix representation

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \Delta_1/\Delta, V_2 = \Delta_2/\Delta, V_3 = \Delta_3/\Delta$$

$$\text{where } \Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$$= 5(-280) + 2(16+0) - 3(0-21)$$

$$= -140 + 32 + 63$$

$$= -45$$

$$\Delta = \begin{vmatrix} + & 60 & -2 & -3 \\ - & 768 & -7 & 0 \\ + & 384 & 0 & 4 \end{vmatrix} = 60(-28-0) - 768(-8-0) - 384(-21)$$

$$= -1680 + 6144 - 8064$$

$$= -3600$$

$$V_1 = \Delta_1/\Delta = -3600/-45 = 80V$$

$$\text{for } V_2: \Delta_2 = \begin{vmatrix} + & 5 & 60 & -3 \\ - & 4 & 768 & 0 \\ + & -3 & 384 & 4 \end{vmatrix}$$

$$= 5((768 \times 4) - 0) - 4(60 \times 4) - (384 \times 3)$$

$$- 3(0 - (768 \times 3))$$

$$= 2880$$

$$\therefore V_2 = \Delta_2/\Delta = 2880/-45 = -64V$$

$$\text{for } V_3: \Delta_3 = \begin{vmatrix} + & 5 & -2 & 60 \\ - & 4 & -7 & 768 \\ + & -3 & 0 & 384 \end{vmatrix}$$


$$= 5((-7 \times 384) - 0) - 4((-2 \times 384) - 0) - 3((-2 \times 768) - (-7 \times 60))$$

$$= -7020$$

$$\therefore V_3 = \Delta_3 / \Delta = -7020 / -45 = 156V$$

Hence  $V_1 = 20V$ ,  $V_2 = -64V$ ,  $V_3 = 156V$

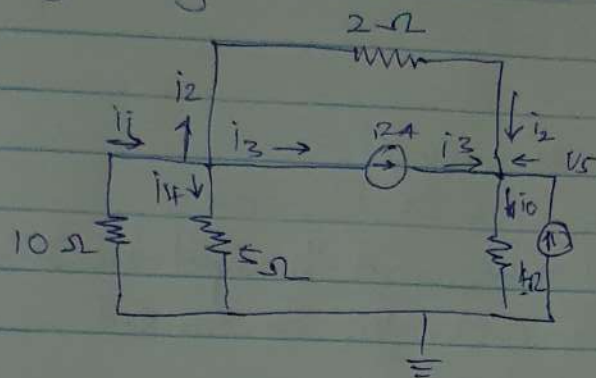2) i) find the voltages at nodes 1 and the currents flowing through the four resistors in the circuit below



at node 1; KCL

$$i_1 = i_2 + i_3 + i_4$$

$$V_0 - V_1 / 10 = V_1 - V_2 / 2 + 12 + V_1 - V_1 / 4$$

$$0 - V_1 = 5(V_1 - V_2) + 120 + 2(V_1 - 0)$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 2V_1$$

$$120 = -8V_1 + 5V_2 \quad \dots (i)$$

At Node 2

$$i_2 + i_2 + i_5 = i$$

$$12 + V_1 - V_2 / 2 + 0 = V_2 - 0 / 4$$

$$46 + 4(V_1 - V_2) + 40 = 2(V_2)$$

$$144 + 4V_1 - 4V_2 = 2V_2$$

$$144 = -4V_1 + 6V_2 \quad \dots (ii)$$

using Elimination method

$$120 = -8V_1 + 5V_2 \quad \dots (i) \times -4$$

$$-480 = 32V_1 - 20V_2 \quad \dots (ii) \times -8$$

$$-480 = 32V_1 - 20V_2 \quad \dots (iii)$$

$$-1152 = 32V_1 - 48V_2 \quad \dots (iv)$$

subtract eqn (iii) from (iv)

$$-672 = 8 - 28V_2$$

$$V_2 = -672 / -28$$

$$V_2 = 24V$$

Subs  $V_2 = 24$  in eqn (ii)

$$144 = 4V_1 + 0V_2$$

$$V_1 = 144 - 0V_2 / 4$$


$$V_1 = 144 - 0V_2 / 4$$

$$V_1 = 0$$

$$\therefore V_1 = 0V, V_2 = 24V$$

$$i_1 = 0A, i_2 = 0A, i_3 = 6A, i_4 = -12A$$

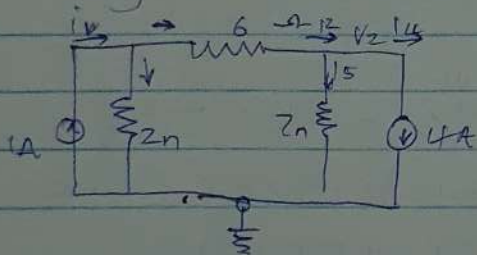ii) obtain  $V_1$  and  $V_2$  and the current through the resistor in the circuit in example (i) if the 2A current source is replaced by a 1A current source



At node 1

$$i = i_2 + i_3$$

$$1 = V_1 - V_2 / 6 + V_2 / 2$$

$$6 = V_1 - V_2 + 3V_2$$

$$6 = 4V_1 - V_2 \dots (i)$$

At node 2

$$i_2 = i_4 + i_5$$

$$V_1 - V_2 / 6 = 4 + V_2 / 2$$

$$7(V_1 - V_2) = 108 + 0V_2$$

$$168 = 7V_1 - 13V_2 \dots (ii)$$

from eqn (i);  $V_2 = 4V_1 - 6$

Subs  $V_2 = 4V_1 - 6$  in eqn

$$168 = 7V_1 - 13(4V_1 - 6)$$

$$168 = 7V_1 - 52V_1 + 78$$

$$90 = -45V_1$$

$$V_1 = 90 / -45$$

$$V_1 = -2V$$

Subs  $\cdot V_1 = -2$  in eqn (i)

$$6 = 4(-2) - V_2$$

$$6 = -8 - V_2$$

$$V_2 = -8 - 6$$

$$V_2 = -14V$$

$$\therefore V_1 = -2V, V_2 = -14V$$


Current through the resistors

$$i_2 = V_1 - V_2 / 6 = -2 + 14 / 6 = 2A$$

$$i_3 = V_1 / 2 = -2 / 2 = -1A$$

$$i_5 = V_2 / 7 = -14 / 7 = -2A$$

3)

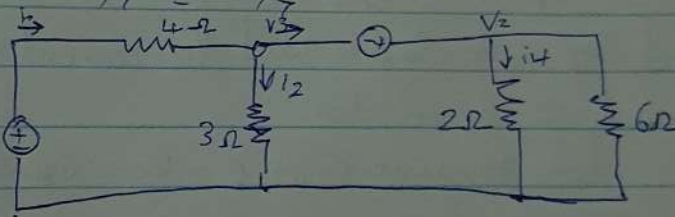

find the current through the  $3\Omega$  and  $2\Omega$  resistors

using KCL at node 1

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$V_1 - 2i_1 / 4 + V_1 / 3 + V_2 / 6 + V_2 / 2$$

$$7V_1 + 8V_2 - 63 = 0 \quad \dots (i)$$

using KVL for loop 1

$$-V_1 - 9 + V_2 = 0$$

$$-V_1 + V_2 = 9 \quad \dots (ii)$$

$$7V_1 + 8V_2 = 63 \quad \dots (i)$$

$$-V_1 + V_2 = 9 \quad \dots (ii)$$

$$\text{let } v_2 = 9 + v_1$$

$$\text{Sub } v_2 = 9 + v_1 \text{ in eqn (i)}$$

$$7v_1 + 8(9 + v_1) = 63$$

$$7v_1 + 72 + 8v_1 = 63$$

$$15v_1 = -9$$

$$v_1 = -0.6 \text{ V}$$

$$\text{Sub } v_1 = -0.6 \text{ in eqn (ii)}$$

$$-(-0.6) + v_2 = 9$$

$$0.6 + v_2 = 9$$

$$v_2 = 8.4 \text{ V}$$

$$\therefore v_1 = -0.6 \text{ V and } v_2 = 8.4 \text{ V}$$

Current through the  $3 \Omega$  resistor;

$$i_2 = v_1 / 3 = -0.6 / 3 = -0.2 \text{ A}$$

Current through the  $2 \Omega$  resistor

$$i_4 = v_2 / 2 = 8.4 / 2 = 4.2 \text{ A}$$

find the node voltages and the currents through the  $6 \Omega$  and  $12 \Omega$  resistors

$$\text{let Assume that } v_1 - v_2 = 6 \text{ V} \Rightarrow i_2$$

At node 1; using KCL

$$6 \text{ mA} = i_1 + i_2$$

$$6 \text{ mA} = v_1 - 0 / 6 + (v_1 - v_2)$$

$$36 = v_1 + 6(v_1 - v_2)$$

$$36 = v_1 + 6v_1 - 6v_2$$

$$36 = 7v_1 - 6v_2 \quad \dots (i)$$

At Node 2

$$i_2 = i_3 + i_4$$

$$v_1 - v_2 = 4 \text{ mA} + v_2 - 0 / 12$$

$$12(v_1 - v_2) = 48 + v_2$$

$$48 = 12v_1 - 12v_2 - v_2$$

$$48 = 12v_1 - 13v_2 \quad \dots (ii)$$

Solving  $V_1$  and  $V_2$  simultaneously

$$V_1 = 9.5V \text{ and } V_2 = 5.1V$$

$\therefore$  Current through the  $12\Omega$  resistor

$$i_2 = V_2 / 12 = 5.1 / 12 = 0.425A$$

$$\therefore V_1 = 9.5V, V_2 = 5.1V$$

$$i_1 = 1.58A, i_2 = 0.425A$$

1  
2  
0.2A

through the

$i_2$

(17)