


RAJESH SANKAR JOSEPH

16/ENG05/015

Mechatronics Engineering

EEE 322 - Electric Circuit Theory

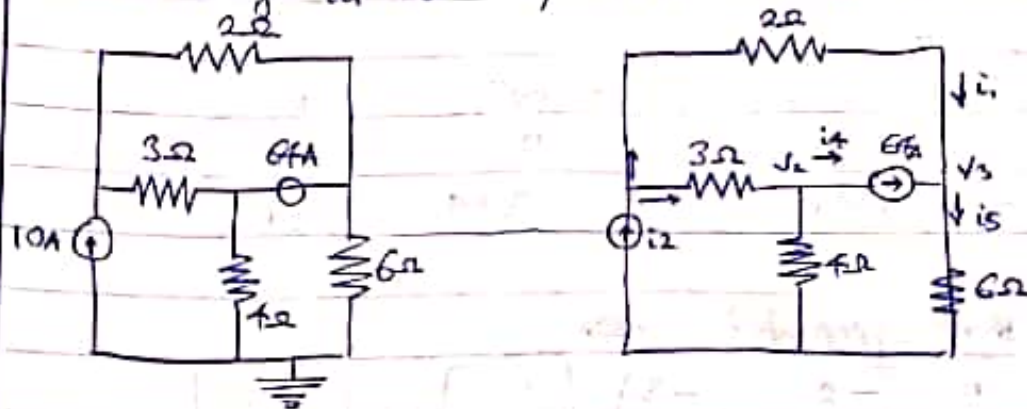① Find the voltages at nodes 1, 2 and 3 in the circuit below



Solution

At node 1, KCL:

$$10 = i_1 + i_2 \Rightarrow 10 = \frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{5}$$

$$60 = 3(V_1 - V_3) + 2(V_1 - V_2)$$

$$60 = 3V_1 - 3V_3 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 2V_2 - 3V_3 \quad \text{--- (i)}$$

At node 2, KCL:

$$i_2 = i_3 + 6A$$

$$6A = i_2 - i_3$$

$$6A = \frac{V_1 - V_2}{3} - \frac{V_2 - 0}{4}$$

$$768 = 4(V_1 - V_2) - 3(V_2 - 0)$$

$$768 = 4V_1 - 4V_2 - 3V_2$$

$$768 = 4V_1 - 7V_2 \quad \text{--- (ii)}$$

At node 3, KCL:

$$6A + i_1 = i_5$$

$$6A = i_5 - i_1$$

$$64 = \frac{V_3 - 0}{6} - \frac{V_1 - V_3}{2}$$

$$384 = V_3 - 3(V_1 - V_3)$$

$$384 = -3V_1 + 4V_3$$

(ii)

Using Cramer's Rule

$$5V_1 - 2V_2 - 3V_3 = 60 \quad \text{--- (i)}$$

$$4V_1 - 7V_2 = 768 \quad \text{--- (ii)}$$

$$-3V_1 + 4V_3 = 384 \quad \text{--- (iii)}$$

In Matrix representation \Rightarrow

$$\begin{pmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{pmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta}, \quad V_2 = \frac{\Delta_2}{\Delta}, \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\text{where } \Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix} = 5(-28-0) + 2(16+0) - 3(0-21) \\ = -140 + 32 + 63 \\ = -85$$

$$\Delta_1 = + \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix} = 60(-28-0) - 7(8-0) + 3(0-21) \\ = -1680 - 56 - 63 \\ = -1800$$

$$\therefore V_1 = \frac{\Delta_1}{\Delta} = \frac{-1800}{-85} \\ = 80V$$

$$\Delta_2 = + \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix} = 5(3072-0) - 4(240+152) - 3(0+2304) \\ = 15360 - 1600 - 7152 \\ = 6608$$

$$= 15360 - 5558 - 6912$$

$$= \underline{2890}$$

$$\therefore V_2 = \frac{\Delta_2}{\Delta} = \frac{2890}{-45} = -64.2222222222 \text{ V}$$

$$V_3 = \begin{vmatrix} + & 5 & -2 & 60 \\ - & 4 & -7 & 788 \\ + & -3 & 0 & 384 \end{vmatrix}$$

$$= 5(-2088 - 0) - 4(-788 - 0) - 3(0 - 1536 + 420)$$

$$= -10440 + 3152 + 3348$$

$$= -7020$$


$$\therefore V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{-45} = \underline{156 \text{ V}}$$

Hence $V_1 = 80 \text{ V}$

$$V_2 = -64 \text{ V}$$

$$V_3 = 156 \text{ V}$$

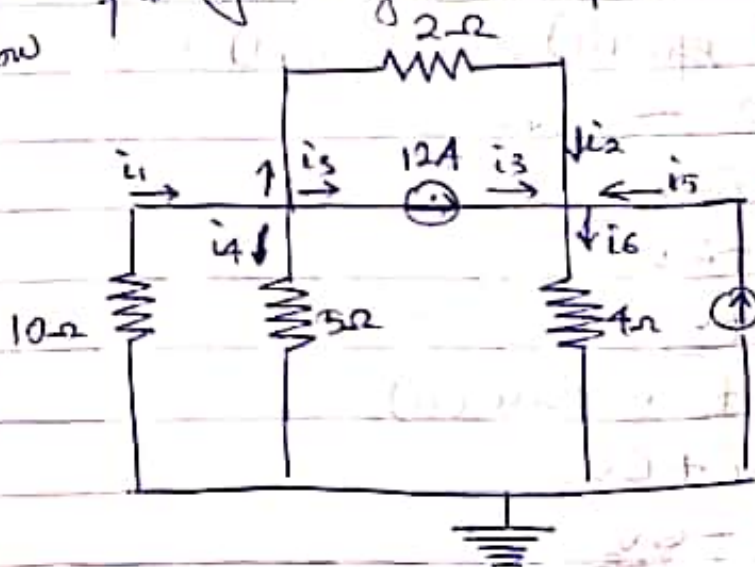(3) Find the voltages at nodes 1 and 2 and determine the currents flowing through the ^{four} resistors in the circuit below



At Node 1, KCL

$$i_1 = i_2 + i_3 + i_4$$

$$i_1 = i_2 + i_3 + i_4$$

$$\frac{V_0 - V_1}{10} = \frac{V_1 - V_2}{2} + 12 + \frac{V_1 - V_0}{5}$$

$$0 - V_1 = 5(V_1 - V_2) + 120 + 2(V_1 - 0)$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 2V_1$$

$$-V_1 = 7V_1 - 5V_2 + 120$$

$$-V_1 - 7V_1 + 5V_2 = 120$$

$$-8V_1 + 5V_2 = 120 \quad \text{--- (i)}$$

At node 2

$$+i_3 + i_2 + i_5 = i_6$$

$$12 + \frac{V_1 - V_2}{2} + 6 = \frac{V_2 - 0}{4}$$

$$96 + 4(V_1 - V_2) + 48 = 2(V_2)$$

$$144 + 4V_1 - 4V_2 = 2V_2$$

$$144 = -4V_1 + 6V_2 \quad \text{--- (ii)}$$

Using Elimination Method

$$120 = -8V_1 + 5V_2 \quad \text{--- (i)} \times (-4)$$

$$144 = -4V_1 + 6V_2 \quad \text{--- (ii)} \times (-8)$$

$$-480 = 32V_1 - 20V_2 \quad \text{--- (iii)}$$

$$-1152 = 32V_1 - 48V_2 \quad \text{--- (iv)}$$

Subtract eqn (iii) from eqn (iv)

$$-672 = 0 - 28V_2$$

$$V_2 = \frac{-672}{-28}$$

$$\therefore V_2 = 24V$$

Substitute $V_2 = 24$ in eqn (ii)

$$144 = -4V_1 + 6V_2$$

$$V_1 = \frac{144 - 6V_2}{-4}$$

$$V_1 = \frac{144 - 6V_2}{-4} = \frac{144 - 6(24)}{-4}$$


$$V_1 = 0$$

$$V_1 = 0V$$

$$V_2 = 24V$$

$$i_1 = 0A, i_2 = 0A, i_3 = 6A, i_4 = -12A$$

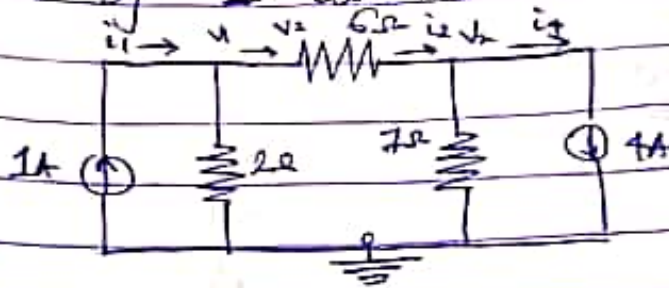2 ii) Obtain V_1 and V_2 and the currents through the resistors for the circuit in example (ii) if the 2A current source was replaced by a 1A current source



At Node 1

$$i_1 = i_2 + i_3$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \quad \text{--- (i)}$$

At Node 2

$$i_3 = i_4 + i_5$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

$$7(V_1 - V_2) = 168 + 6V_2$$

$$168 = 7V_1 - 7V_2 - 6V_2$$

$$168 = 7V_1 - 13V_2 \quad \text{--- (ii)}$$

from eqn (i), $V_2 = 4V_1 - 6$

Substitute $V_2 = 4V_1 - 6$ in eqn (ii)

$$168 = 7V_1 - 7(4V_1 - 6) - 6(4V_1 - 6)$$

$$168 = 7V_1 - 28V_1 + 42 - 24V_1 + 36$$

$$168 = -45V_1 + 78$$

$$45V_1 = -168 + 78$$

$$45V_1 = -90$$

$$V_1 = \frac{-90}{45}$$

$$V_1 = -2V$$

Substitute $V_1 = -2$ in eqn (1)

$$6 = 4(-2) - V_2$$

$$6 = -8 - V_2$$

$$V_2 = -8 - 6$$

$$V_2 = -14V$$

$$\therefore V_1 = -2V$$


$$V_2 = -14V$$

Current through the resistors;

$$i_2 = \frac{V_1 - V_2}{6} = \frac{-2 + 14}{6} = 2A$$

$$i_3 = \frac{V_1}{2} = \frac{-2}{2} = -1A$$
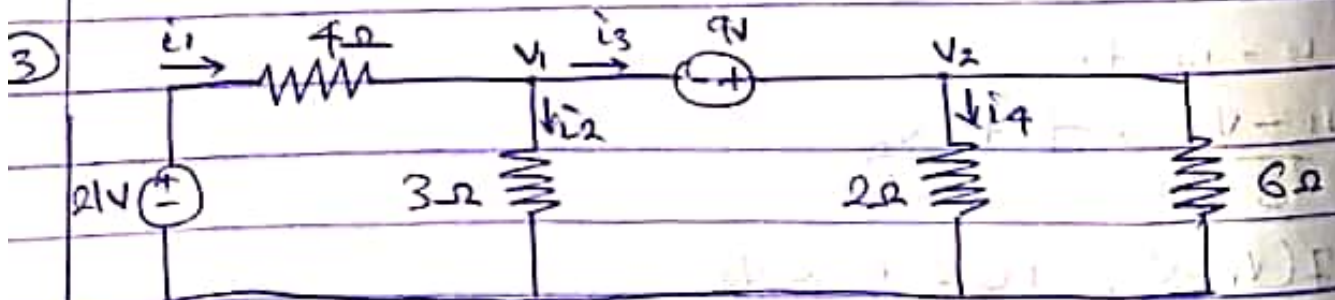
$$i_5 = \frac{V_2}{7} = \frac{-14}{7} = -2A$$



Find the current through the 3Ω and 2Ω resistors using KCL at Node 1

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\frac{V_1 - 21}{4} + \frac{V_1}{3} + \frac{V_2}{6} + \frac{V_2}{2} + \frac{V_2}{2} = 0$$

$$7V_1 + 8V_2 - 63 = 0 \quad \text{--- (i)}$$

using KVL for loop 1

$$-V_1 - 9 + V_2 = 0$$

$$-V_1 + V_2 = 9 \quad \text{--- (i)}$$

$$7V_1 + 8V_2 = 63 \quad \text{--- (ii)}$$

$$-V_1 + V_2 = 9 \quad \text{--- (iii)}$$

from eqn (iii) let $V_2 = 9 + V_1$

Substitute $V_2 = 9 + V_1$ in eqn (ii)

$$7V_1 + 8(9 + V_1) = 63$$

$$7V_1 + 72 + 8V_1 = 63$$

$$15V_1 = 63 - 72$$

$$15V_1 = -9$$

$$V_1 = \frac{-9}{15} = -0.6V$$

$$V_1 = -0.6V$$

Substitute $V_1 = -0.6V$ into eqn (i)

$$+0.6 + V_2 = 9$$

$$V_2 = 9 - 0.6$$

$$V_2 = 8.4V$$

$$\therefore V_1 = -0.6V$$


$$V_2 = 8.4V$$

• Current through the 3Ω resistor;

$$i_2 = \frac{V_1}{3} = \frac{-0.6}{3} = -0.2A$$

• Current through the 2Ω resistor;
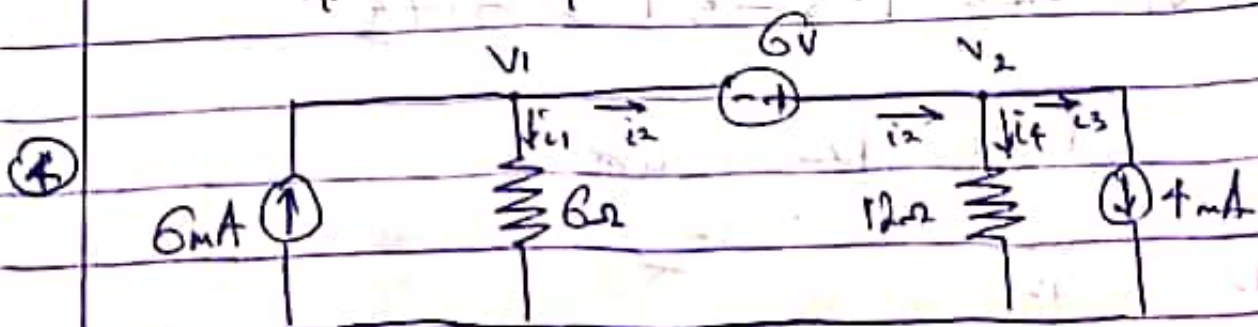
$$i_4 = \frac{V_2}{4} = \frac{8.4}{4} = 2.1A$$



Find the node voltages and the currents through the 6Ω and 12Ω resistor.

$$\text{Let assume that } V_1 - V_2 = 0V \Rightarrow i_2$$

At node 1; using KCL

$$6mA = i_1 + i_2$$

$$6mA = \frac{V_1 - 0}{6} + (V_1 - V_2)$$

$$36 = V_1 + 6(V_1 - V_2)$$

$$36 = V_1 + 6V_1 - 6V_2$$

$$36 = 7V_1 - 6V_2 \quad \text{--- (i)}$$

At node 2,

$$i_2 = i_3 + i_4$$

$$V_1 - V_2 = 4mA + \frac{V_2 - 0}{12}$$

$$12(V_1 - V_2) = 48 + V_2$$

$$12V_1 - 12V_2 = 48 + V_2$$

$$12V_1 - 12V_2 - V_2 = 48$$

$$12V_1 - 13V_2 = 48 \quad \text{--- (ii)}$$

Solving V_1 & V_2 simultaneously

$$V_1 = 9.5V$$

$$V_2 = 5.1V$$

\therefore Current through the 6Ω resistor

$$i_1 = \frac{V_1}{6} = \frac{9.5}{6} = 1.58A$$

$$i_2 = V_1 - V_2 = 9.5 - 5.1 = 4.4A$$

Current through the 12Ω resistor

$$i_4 = \frac{V_2}{12} = \frac{5.1}{12} = 0.43A$$

$$\Delta V_1 = 9.0V$$

$$V_2 = 5.1V$$

$$I_1 = 1.58A$$

$$I_4 = 0.43A$$