
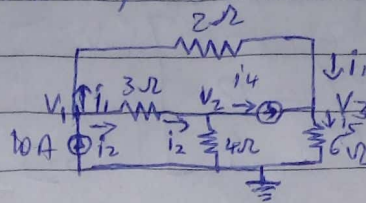


UDOSBN ELEMINI JOHN
17/ENG041070

ELECTRONICS / ELECTRICAL ENGINEERING

CIRCUIT THEORY (ENG 322) Assignment.

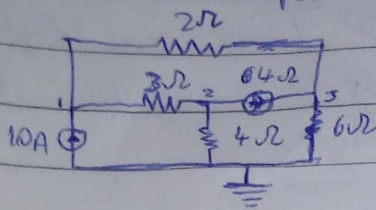1) Find the voltages at nodes 1, 2 and 3 in the circuit below:



At node 1, KCL:

$$10 = i_1 + i_2 \Rightarrow 10 = \frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{3}$$

$$\Rightarrow 60 = 3(V_1 - V_3) + 2(V_1 - V_2)$$

$$60 = 3V_1 - 3V_3 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 2V_2 - 3V_3 \quad \dots \dots \dots (i)$$

At node 2, KCL:

$$i_2 = i_3 + 64$$

$$-64 = i_2 - i_3$$

$$64 = \frac{V_1 - V_2}{3} - \frac{V_2 - 0}{4}$$

$$768 = 4(V_1 - V_2) - 3(V_2 - 0)$$

$$768 = 4V_1 - 4V_2 - 3V_2 - 0$$

$$768 = 4V_1 - 7V_2 \quad \dots \dots \dots (ii)$$

At node 3, KCL:

$$64 + i_1 = i_5$$

$$64 = i_5 - i_1$$

$$64 = \frac{V_3 - 0}{4} - \frac{V_1 - V_3}{2}$$

$$384 = V_3 - 3(V_1 - V_3)$$

$$384 = V_3 - 3V_1 + 3V_3$$

$$384 = -3V_1 + 4V_3 \quad \dots \dots \dots (iii)$$

Using Cramer's Rule

$$5V_1 - 2V_2 - 3V_3 = 60 \quad \dots \dots \dots (i)$$

$$4V_1 - 7V_2 = 768 \quad \dots (ii)$$

$$-3V_1 + 4V_3 = 384 \quad \dots (iii)$$

In matrix representation

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta}, \quad V_2 = \frac{\Delta_2}{\Delta}, \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\text{Where } \Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$$= 5(-2 \times 0) + 2(16 + 0) - 3(0 - 21)$$

$$= -140 + 32 + 63$$

$$= -45$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix} = 60(-28 - 0) - 768(8 - 0) + 384(0 - 21)$$

$$= -1680 + 6144$$

$$= -3600$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45} = 80V$$

$$\text{for } V_2 : \Delta_2 = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$$

$$= 5(768 \times 4 - 0) - 4((60 \times 4) - (384 \times 3)) - 3(0 - (768 \times 3))$$

$$= 2880$$

$$\therefore V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64V$$

$$\text{for } V_3 = \begin{vmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ -3 & 0 & 384 \end{vmatrix}$$


$$= 5((-7 \times 384) - 0) - 4((-2 \times 384) - 0) - 3((-2 \times 768) - (-7 \times 60))$$

$$= -7020$$

$$\therefore V_3 = \frac{D_3}{A} = \frac{-7020}{45} = 156V$$

Therefore, $V_1 = 80V$, $V_2 = -64V$, $V_3 = 156V$

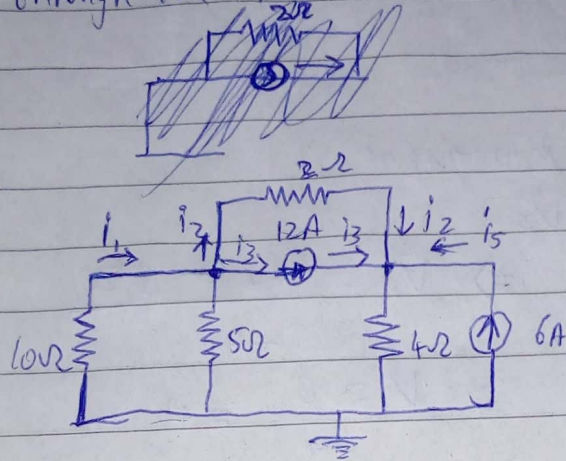2) (i) Find the voltages at nodes 1 and 2 and determine the currents flowing through the four resistors in the circuit below:



At Node 1, KCL

$$i_1 = i_2 + i_3 + i_4$$

$$\frac{V_0 - V_1}{10} = \frac{V_1 - V_2}{5} + i_2 + \frac{V_1 - V_2}{2}$$

$$0 - V_1 = 5(V_1 - V_2) + 12 + 2(V_1 - V_2)$$

$$-V_1 = 5V_1 - 5V_2 + 12 + 2V_1$$

$$120 = -8V_1 + 5V_2 \quad \dots \dots (i)$$

At Node 2

$$i_3 + i_2 + i_5 = i_6$$

$$i_2 + \frac{V_1 - V_2}{2} + 6 = \frac{V_2 - 0}{4}$$

$$96 + 4(V_1 - V_2) + 48 = 2(V_2)$$

$$144 + 4V_1 - 4V_2 = 2V_2$$

$$144 = -4V_1 + 6V_2 \quad \dots \dots (ii)$$

Making use of Elimination method.

$$120 = -8V_1 + 5V_2 \quad \dots \dots (i) \quad \times -4$$

$$144 = -4V_1 + 6V_2 \quad \dots \dots (ii) \quad \times 8$$

$$-480 = 32V_1 - 20V_2 \quad \dots (III)$$

$$-1152 = 32V_1 - 48V_2 \quad \dots (IV)$$

Subtract eqn (III) from (IV)

$$-672 = 0 - 28V_2$$

$$V_2 = \frac{-672}{-28}$$

$$V_2 = 24V$$

Substitute $V_2 = 24$ into eqn (III)

$$144 = -4V_1 + 6V_2$$

$$V_1 = \frac{144 - 6V_2}{-4} \Rightarrow V_1 = \frac{144 - 6(24)}{-4}$$


$$V_1 = \frac{144 - 144}{-4} \Rightarrow V_1 = 0 = 0$$

$$\therefore V_1 = 0$$

$$\therefore V_1 = 0V, V_2 = 24V$$

$$i_1 = 0A, i_2 = 0A, i_3 = 6A, i_4 = -12A$$

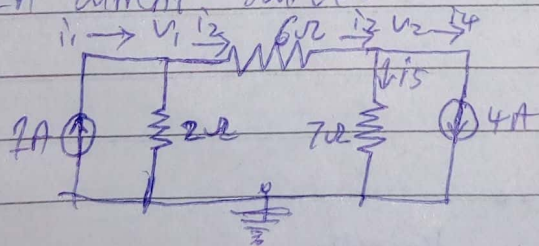(ii) Obtain V_1 and V_2 and the currents through the resistors for the circuit in example (ii) if the 2A current source was replaced by a 1A current source.



At Node 1

$$i_1 = i_2 + i_3$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \quad \dots (1)$$

At Node 2

$$i_2 = i_4 + i_5$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

~~$$7(V_1 - V_2) = 28 + V_2$$~~

$$7(V_1 - V_2) = 168 + 6V_2$$

$$168 = 7V_1 - 13V_2 \quad \dots (1)$$

from eqn (1) ; $V_2 = 4V_1 - 6$

sub. ~~V_2~~ $= 4V_1 - 6$ into eqn (1)

$$168 = 7V_1 - 13(4V_1 - 6)$$

$$168 = 7V_1 - 52V_1 + 78$$

$$90 = -45V_1$$

$$V_1 = \frac{90}{-45}$$

$$V_1 = -2V$$

sub $V_1 = -2$ into eqn(1)

$$6 = 4(-2) - V_2 \Rightarrow 6 = -8 - V_2$$

$$V_2 = -8 - 6$$

$$V_2 = -14V$$


$$\therefore V_1 = -2V, V_2 = -14V$$

Current through the resistor

$$i_2 = \frac{V_1 - V_2}{6} = \frac{-2 + 14}{6} = 2A$$

$$i_3 = \frac{V_1}{2} = \frac{-2}{2} = -1A$$
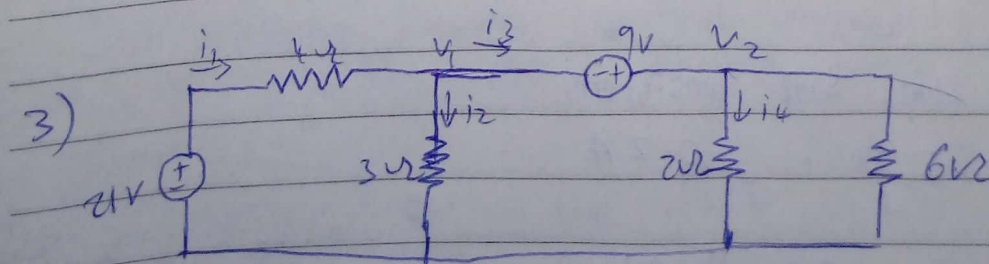
$$i_5 = \frac{V_2}{7} = \frac{-14}{7} = -2A$$



Find the current through the 3Ω and 2Ω resistors.

Using KCL at node 1

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\frac{V_1 - 21}{4} + \frac{V_1}{3} + \frac{V_2}{6} + \frac{V_2}{2}$$

$$7V_1 + 8V_2 - 63 = 0 \quad \dots (1)$$

Using KVL for loop 1

$$-V_1 - 9 + V_2 = 0$$

$$-V_1 + V_2 = 9 \quad \dots (11)$$

$$7V_1 + 8V_2 - 63 = 0 \quad \dots (1)$$

$$-V_1 + V_2 = 9 \quad \dots (11)$$

from (11) let $V_2 = 9 + V_1$

Sub: $V_2 = 9 + V_1$ into eqn (1)

$$7V_1 + 8(9 + V_1) = 63$$

$$7V_1 + 72 + 8V_1 = 63$$

$$15V_1 = -9 \quad \Rightarrow V_1 = \frac{-9}{15}$$

$$V_1 = -0.6V$$

Sub $V_1 = -0.6$ into eqn (11)

$$-(-0.6) + V_2 = 9$$

$$0.6 + V_2 = 9$$

$$V_2 = 9 - 0.6$$

$$V_2 = 8.4V$$


$$\therefore V_1 = -0.6V \quad \& \quad V_2 = 8.4V$$

Current through the 3Ω resistor,

$$i_2 = \frac{V_1}{3} = \frac{-0.6}{3} = -0.2A$$

Current through the 2Ω resistor
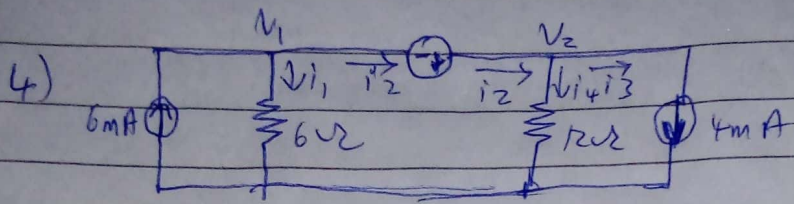
$$i_4 = \frac{V_2}{4} = \frac{8.4}{4} = 2.1 \text{ A}$$



Find the node voltages and the currents through the 6Ω and 12Ω resistor.

Let's assume that $V_1 - V_2 = 6V \Rightarrow i_2$

At node 1, using KCL

$$6\text{mA} = i_1 + i_2$$

$$6\text{mA} = \frac{V_1 - 0}{6} + (V_1 - V_2)$$

$$36 = V_1 + 6(V_1 - V_2)$$

$$36 = V_1 + 6V_1 - 6V_2$$

$$36 = 7V_1 - 6V_2 \quad \dots (1)$$

At Node 2

$$i_2 = i_3 + i_4$$

$$V_1 - V_2 = 4\text{mA} + \frac{V_2 - 0}{12}$$

$$12(V_1 - V_2) = 48 + V_2$$

$$48 = 12V_1 - 12V_2 - V_2$$

$$48 = 12V_1 - 13V_2 \quad \dots (2)$$

Solving V_1 and V_2 simultaneously, we have

$$V_1 = 9.5\text{V} \quad \text{and} \quad V_2 = 5.1\text{V}$$

∴ Current through the 6Ω resistor

$$i_1 = \frac{V_1}{6} = \frac{9.5}{6} = 1.58\text{A}; \quad i_2 = V_1 - V_2 = 9.5 - 5.1 = 4.4\text{A}$$

Current through the 12Ω resistor

$$i_4 = \frac{V_2}{12} = \frac{5.1}{12} = 0.43\text{A}$$

$$\therefore V_1 = 9.5\text{V}, \quad V_2 = 5.1\text{V}$$

$$i_1 = 1.58\text{A}, \quad i_4 = 0.43\text{A}$$