


ADENIYI TOHEB '0.

17/ENG02/006

COMPUTER ENGINEERING

CIRCUIT THEORY ASSIGNMENT

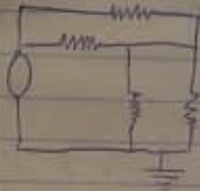1) Find the voltage at node 1, 2, 3 in the circuit below



Node 1 KCL

$$10 = i_1 + i_2 = \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{3}$$

Multiply through by 6

$$60 = 3(V_1 - V_2) + 2(V_1 - V_3)$$

$$60 = 3V_1 = 3V_1 + 2V_1 - 2V_3$$

$$60 = 5V_1 - 3V_3 - 2V_3 \quad \text{--- (1)}$$

At Node 2 KCL

$$I_2 = I_3 + 6$$

$$64 = i_2 - i_1$$

$$64 = \frac{V_1 - V_2}{3} - \frac{V_2 - 0}{4}$$

$$I_2 = -12A$$

Multiply through by 7

$$768 = 4(V_1 - V_2) - 3(V_2 - 0)$$

$$768 = 4V_1 - 7V_2 \quad \text{--- (2)}$$

At Node 3 KCL

$$64 + i_1 = 15$$

$$64 = 15 - 14$$

$$64 = \frac{V_3 - 0}{6} - \frac{V_3 - V_1}{2}$$

$$384 = V_3 - 3(V_3 - V_1)$$

$$384 = -3V_3 + 4V_1 \quad \text{--- (3)}$$

$$5V_1 - 2V_2 - 3V_3 = 60 \quad \text{--- (1)}$$

$$4V_1 - 7V_2 + 0V_3 = 768 \quad \text{--- (2)}$$

$$-3V_1 + 0V_2 + 4V_3 = 384$$

Matrix Eq

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta} \quad V_2 = \frac{\Delta_2}{\Delta} \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$$= 5(-28-0) + 2(16+0) - 3(0-28)$$

$$= -140 + 32 + 84$$

$$= -45$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$= 60(-28-0) - 768(-8-0) - 384(0-28)$$

$$= -1680 + 6144 + 10752$$

$$= 3600$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45} = 80V$$

$$V_2 = \Delta_2 = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$$

$$= 5(2982-0) - 4(2496) - (384-12)$$

$$= 2180$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{2180}{-45} = -48.4V$$


$$V_3 = \begin{vmatrix} 5 & -2 & 60 \\ 4 & -2 & 70 \\ -3 & 0 & 70 \end{vmatrix}$$

$$= 5((-7 \times 384) - 0) - 4((1-2 \times 384) - 0) - 3((1-2 \times 70) - (-7 \times 60))$$

$$= -7020$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{-45} = 156V$$
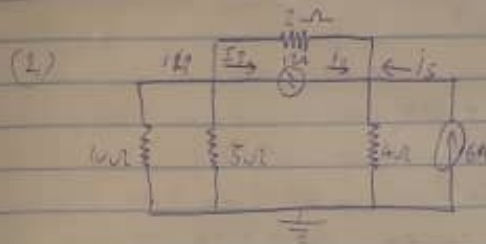
$$\therefore V_1 = 80V, V_2 = -64V, V_3 = 156V$$



Node 1 KCL

$$i_1 = i_2 + i_3 + i_4$$

$$\frac{V_3 - V_1}{10} = \frac{V_1 - V_2}{5} + 12 + \frac{V_1 - V_2}{2}$$

$$0 - V_1 = 5(V_1 - V_2) + 10 + 2(V_1 - V_2)$$

$$-V_1 = 5V_1 - 5V_2 + 10 + 2V_1$$

$$+70 = -8V_1 + 5V_2 \quad \text{--- (1)}$$

Node

$$i_7 + i_8 = i_9 = 1$$

$$12 + \frac{V_1 - V_2}{2} + 6 = V_2 - 0$$

$$90 + 4(V_1 - V_2) + 6V_2 = 0 \quad \text{--- (2)}$$

$$100 + 4V_1 - 4V_2 + 6V_2 = 70$$

$$140 = -4V_1 + 6V_2 \quad \text{--- (3)}$$

Using Equations (1) & (3)

$$170 = -8V_1 + 5V_2 \quad \text{--- (1) } \times 2$$

$$140 = -4V_1 + 6V_2 \quad \text{--- (3) } \times 2$$

$$-40 = 7V_1 + 20V_2 + 20V_2 \quad \text{--- (4)}$$

$$-150 = 7V_1 - 40V_2 \quad \text{--- (5)}$$

Summe $i_1 = 0$ (Knoten 1)

$$-6i_1 = 0 - 3i_2$$

$$-6i_1 = -3i_2$$

$$V_1 = -6i_1$$

$$= -28$$

$$V_2 = 24V$$

Summe V_1 (Knoten 2)

$$16A = -4i_1 + 6i_2$$

$$V_1 = 16A - 6(7A)$$

$$= -4$$

$$V_1 = -10A - 16A = 0V$$

$$V_1 = 0V \quad V_2 = 24V$$

$$i_1 = 0A, \quad i_2 = 0A, \quad i_3 = 6A, \quad i_4 = -12A$$



Node 1

$$i_1 = i_2 + i_3$$

$$i = \frac{V_1 - V_2}{2} + \frac{V_1}{6}$$

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \quad (1)$$

Node 2

$$i_2 = i_4 + i_3$$

$$\frac{V_1 - V_2}{2} = \frac{4 - V_2}{2} + \frac{V_1}{6}$$

$$2(V_1 - V_2) = 4 - V_2 + V_1$$

$$3V_1 - 3V_2 = 4 - V_2 \quad (2)$$

$$16x = 7V_1 - 13V_2 - 30$$

From eqn 4

$$V_2 = 4V_1 - 6$$

Sub $V_2 = 4V_1 - 6$ into eqn 3

$$16x = 7V_1 - 13(4V_1 - 6)$$

$$16x = 7V_1 - 52V_1 + 78$$

$$70 = -45V_1$$

$$V_1 = \frac{70}{-45}$$

$$V_1 = -2V$$

Sub $V_1 = -2$ into eqn 1

$$6 = 4(-2) - V_2$$

$$6 = -8 - V_2$$

$$V_2 = -8 - 6$$

$$V_2 = -14V$$


$$V_1 = -2V, V_2 = -14V$$

Current through the 12Ω resistor

$$i_2 = \frac{V_1 - V_2}{6} = \frac{-2 - (-14)}{6} = 2A$$

$$i_3 = \frac{V_1}{2} = \frac{-2}{2} = -1A$$
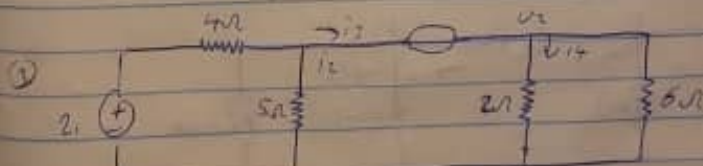
$$i_4 = \frac{V_2}{7} = \frac{-14}{7} = -2A$$



For the current through the 3Ω and 2Ω resistors

i_1 KCL at Node 1

$$i_1 + i_3 + i_4 + i_2 = 0$$

$$\frac{V_1 - 2V}{3} + \frac{V_1}{2} + \frac{V_2}{7} + \frac{V_2}{6} = 0$$