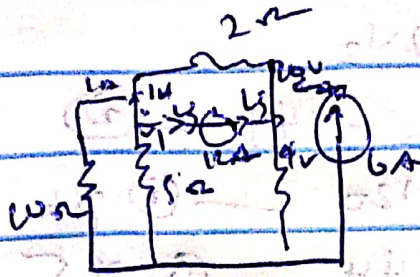


Emmanuel Orborawa

07/MTH01/113



Node 1

$$I_1 + I_2 + I_3 + I_4 = 0$$

$$\frac{V_1}{10} + \frac{V_1}{5} + 12 + \frac{V_1 - V_2}{2} = 0$$

$$\frac{V_1 + 2V_1 + 120 + 5V_1 - 5V_2}{10} = 0$$

$$8V_1 - 5V_2 + 120 = 0$$

$$8V_1 - 5V_2 + 120 = 0$$

$$8V_1 - 5V_2 + 120 = 0$$

$$8V_1 - 5V_2 = -120 \quad \text{--- (1)}$$

Node 2

$$I_3 + I_5 + I_6 = I_7$$

$$\frac{V_1 - V_2}{2} = V_2 + 6 = \frac{V_2}{4}$$

$$\frac{V_1 - V_2 + 24 + 12}{2} = \frac{V_2}{4}$$

$$\frac{V_1 - V_2 + 36}{2} = \frac{V_2}{4}$$

$$4V_1 - 4V_2 + 144 = 2V_2$$

$$4V_1 - 6V_2 = -144 \quad \text{--- (2)}$$

$$8V_1 - 5V_2 = -120 \quad \text{--- (1) } \times 6$$

$$48V_1 - 30V_2 = -720 \quad \text{--- (1) } \times 5$$

$$48V_1 - 30V_2 = -720$$

$$20V_1 - 30V_2 = -720$$

$$48V_1 - 20V_1$$

$$28V_1 = 0$$

$$V_1 = 0$$

Let eq

$$8V_1 - 5V_2 = -120$$

Sub $V_1 = 0$ into eqn (1)

$$8(0) - 5V_2 = -120$$

$$\frac{-120 + 120}{-5} = \frac{-5V_2}{-5} = \frac{-120}{-5}$$

$$V_2 = 24$$

$$V_1 = 0, V_2 = 24V$$


current flowing through resistor.

$$10\Omega: \frac{V_1}{10} = \frac{0}{10} = 0A$$

$$5\Omega: \frac{V_1}{5} = \frac{0}{5} = 0A$$

$$2\Omega: \frac{V_1 - V_2}{2} = \frac{0 - 24}{2} = -12A$$
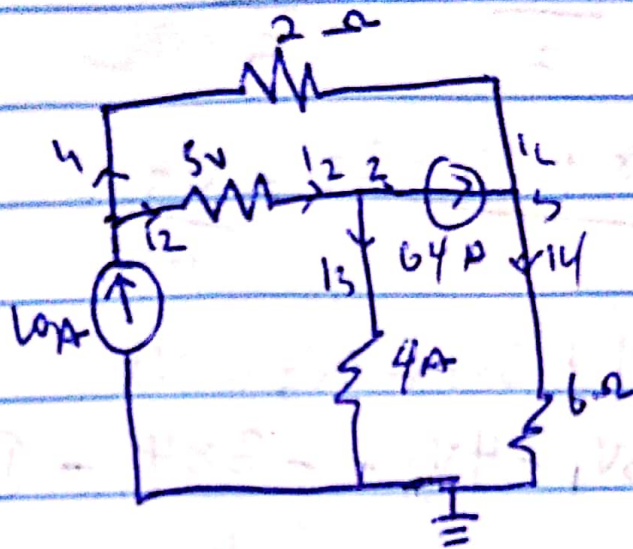
$$4 \Omega : \frac{V_2}{4} = \frac{24}{4} = 6A$$



Node 1 = $I_0 = I_1 + I_2$

$$10 = \frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{3}$$

$$10 = \frac{3V_1 - 3V_3 + 2V_1 - 2V_2}{6}$$

$$60 = 5V_1 - 2V_2 - 3V_3 \quad \text{--- (I)}$$

Node 2

$$64 + I_3 = I_2$$

$$\frac{64}{1} + \frac{V_2}{4} = \frac{V_1 - V_2}{3}$$

$$\frac{256 + V_2}{4} = \frac{V_1 - V_2}{3}$$

$$768 + 3V_2 = 4V_1 - 4V_2$$

$$768 = 4V_1 - 7V_2 \quad \text{--- (II)}$$

Node 3

$$64 + I_1 = 14$$

$$64 + \frac{V_1 - V_3}{2} = \frac{V_3}{6}$$

$$2 \times 128 + \frac{V_1 - V_3}{2} = \frac{V_3}{6}$$

$$384 + 5V_1 - 3V_3 = V_3$$

$$3V_1 - 4V_3 = -384 \quad \text{--- (11)}$$

Using Cramer's rule

$$5V_1 - 2V_2 - 3V_3 = 60$$

$$4V_1 - 7V_2 + 0 = 768$$

$$3V_1 + 0 - 4V_3 = -384$$

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ 3 & 0 & -4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ -384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta}, \quad V_2 = \frac{\Delta_2}{\Delta}, \quad V_3 = \frac{\Delta_3}{\Delta}$$

Δ_2	5	-2	-3	5	-2
	4	-7	0	4	0
	3	0	-4	3	0

$$\frac{V_{12} \Delta_1}{\Delta} \quad \frac{V_{22} \Delta_2}{\Delta} \quad \frac{V_{32} \Delta_3}{\Delta}$$

$$\Delta_2 \left(\begin{array}{ccc|cc} 5 & -2 & -3 & 5 & -2 \\ 4 & -7 & 0 & 4 & -7 \\ 3 & 0 & 4 & 3 & 0 \end{array} \right)$$

$$(+140 + 0 + 0) - (32 + 0 + 63)$$

$$+140 - (+95)$$

$$+140 - 95$$

$$\Delta_2 = 45$$

$$\Delta_{12} \left(\begin{array}{ccc|cc} 60 & -2 & -2 & 60 & -2 \\ 768 & -7 & 0 & 768 & -7 \\ -384 & 0 & -4 & -384 & 0 \end{array} \right)$$

$$(1680 + 0 + 0) - (6144 + 0 - 5064)$$

$$1680 - (-1920)$$

$$\Delta_2 = 3600$$

$$\Delta_2 = (-15360 + 0 + 4608) - (-9600)$$

$$(-6752)$$

$$-10752 - (-7872)$$

$$-10752 + 7872$$

$$\Delta_2 = -2880$$

$$\Delta_3 = \begin{vmatrix} 8 & -2 & 60 \\ 4 & 7 & 768 \\ 3 & 0 & -384 \end{vmatrix} \begin{vmatrix} 8 & -2 \\ 4 & 7 \\ 3 & 0 \end{vmatrix}$$

$$= (13440 - 4608 + 0) - (3072 + 1260)$$

$$8832 - (1812)$$

$$\Delta_3 = 7020$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{3200}{45} = 71.11 \text{ V}$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{-2880}{45} = -64 \text{ V}$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{7020}{45} = 156 \text{ V}$$