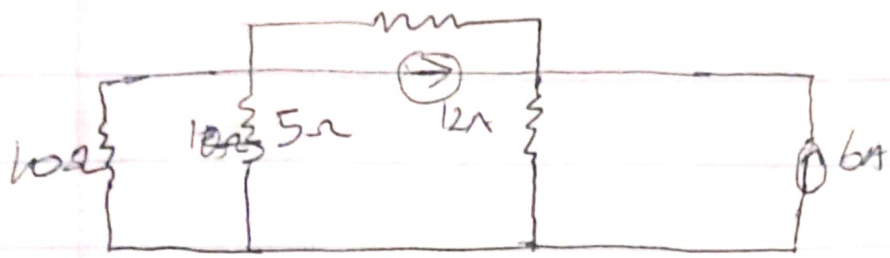




Name: Lawal Mohammad Zahir
 Matric No: 171Eng041039
 Dept: Elects/Elect
 Course: circuit theory

(1)



- (i) Find Voltage of node 1 and 2
- (ii) Find the current flowing through the four resistors

Soln

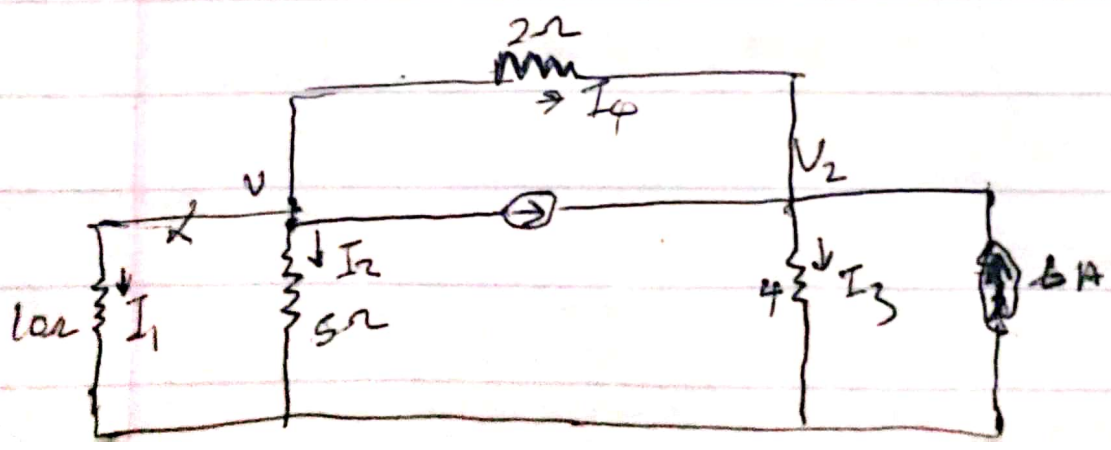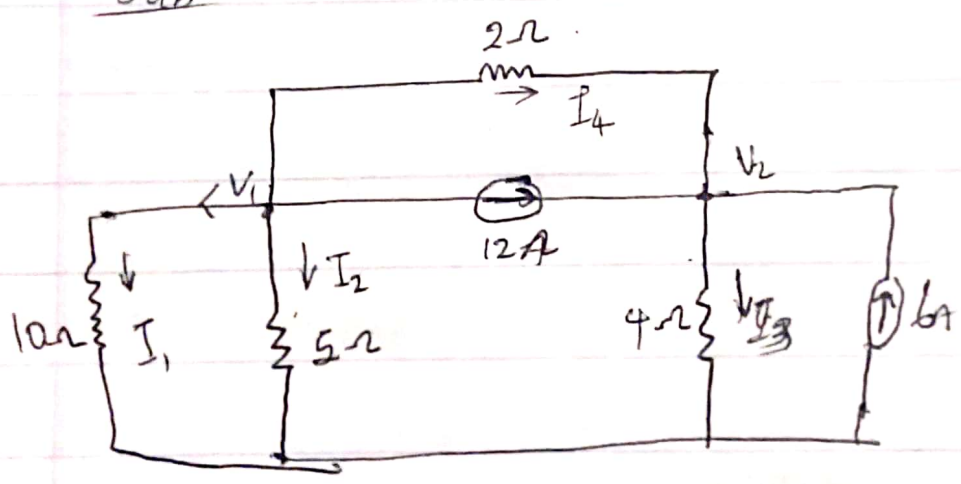

2

from node 1; using KCL

$$i_1 + i_2 + i_4 = -12A$$

$$i_1 = \frac{V_1 - 0}{10} = \frac{V_1}{10}$$

$$i_2 = \frac{V_1 - 0}{5} = \frac{V_1}{5}$$

$$i_4 = \frac{V_1 - V_2}{2}$$

$$\frac{V_1}{10} + \frac{V_1}{5} + \frac{V_1 - V_2}{2} = -12$$

$$\equiv \frac{V_1}{10} + \frac{2V_1}{10} + \frac{5(V_1 - V_2)}{10} = -12$$

$$= \frac{V_1 + 2V_1 + 5V_1 - 5V_2}{10} = -12$$

$$\frac{8V_1 - 5V_2}{10} = -12$$

$$\Rightarrow 8V_1 - 5V_2 = -120$$

Applying KCL in node 2

$$i_4 + 6 + 12 = i_3$$

$$i_4 - i_3 = -18$$

$$i_4 = \frac{V_1 - V_2}{2} \quad \text{and} \quad i_3 = \frac{V_2 - 0}{4} = \frac{V_2}{4}$$

$$\Rightarrow \frac{V_1 - V_2}{2} - \frac{V_2}{4} = -18$$

$$\frac{2(V_1 - V_2)}{4} = \frac{V_2}{4} = -18$$

$$\frac{2V_1 - 2V_2 - V_2}{4} = -18$$

$$\frac{2V_1 - 3V_2}{4} = -18$$

$$2V_1 - 3V_2 = -72 \quad \dots \dots \dots (11)$$

$$8V_1 - 5V_2 = -120$$

$$2V_1 - 3V_2 = -72$$

Using calculator to solve simultaneously

$$V_1 = 0V \quad \& \quad V_2 = 24V$$

$$i_1 = \frac{V_1}{10} = \frac{0}{10} = \underline{\underline{0A}}$$


$$i_2 = \frac{V_1}{5} = \frac{0}{5} = \underline{\underline{0A}}$$

$$i_3 = \frac{V_2}{4} = \frac{24}{4} = \underline{\underline{6A}}$$


$$i_4 = \frac{V_1 - V_2}{2} = \frac{0 - 24}{2} = \frac{-24}{2} = \underline{\underline{-12A}}$$

4

2

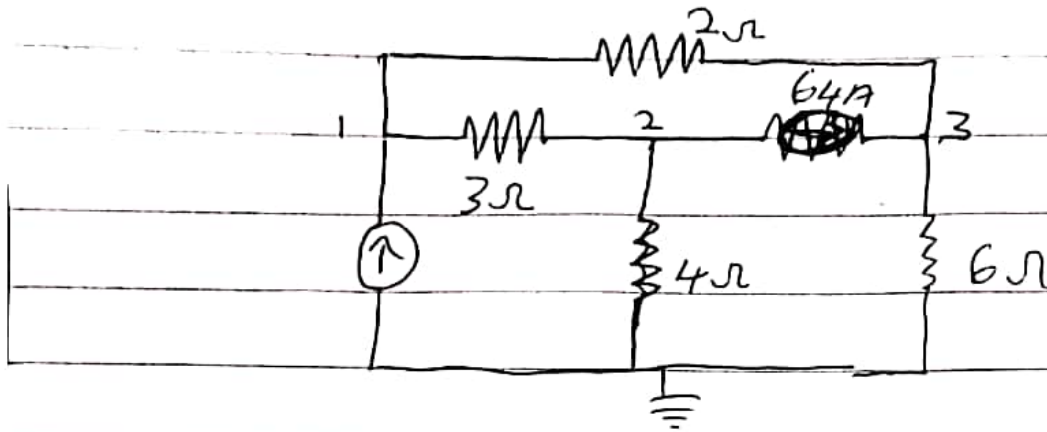

find the voltages at node 1, 2 & 3
Soln

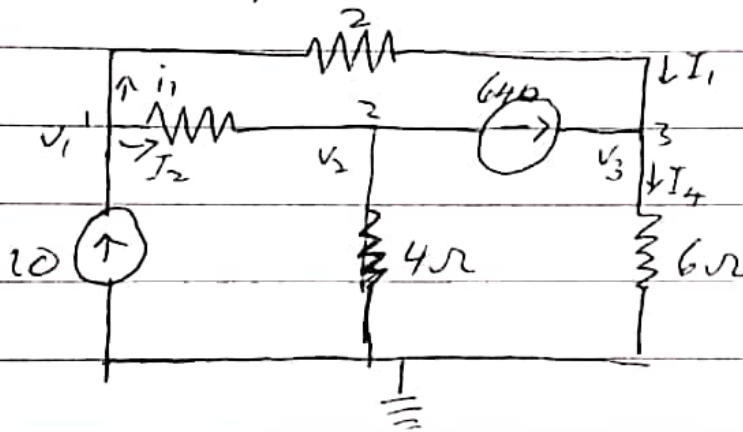

⊗ at node 1; using KCL $10 = i_1 + i_2$

$$10 = \frac{V_1 - V_2}{2} + \frac{V_1 - V_2}{3}$$

at node 2; using KCL: $i_2 = 64 + i_3$

$$\frac{V_1 - V_2}{3} = 64 + \frac{V_2}{4}$$

at node 3 using KCL; $i_4 = 64 + i_1$

$$\frac{V_3}{6} = 64 + \frac{V_2 - V_3}{2}$$

$$10 = \frac{5}{6}V_1 - \frac{1}{3}V_2 - \frac{1}{2}V_3$$

$$64 = \frac{1}{3}V_1 - \frac{7}{12}V_2 + 0V_3$$

$$64 = -\frac{1}{2}V_1 - 0 + \frac{2}{3}V_3$$

Using matrix method

$$\begin{bmatrix} 10 \\ 64 \\ 64 \end{bmatrix} = \begin{bmatrix} \frac{5}{6} & -\frac{1}{3} & -\frac{1}{2} \\ \frac{1}{3} & -\frac{7}{12} & 0 \\ \frac{1}{2} & 0 & \frac{2}{3} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

A

B


C

$$C = B^{-1}A$$

$$B^{-1}A = \begin{bmatrix} 3.73 & -2.13 & 2.8 \\ 2.13 & -2.93 & 1.6 \\ 2.8 & -1.6 & 3.6 \end{bmatrix} \begin{bmatrix} 10 \\ 64 \\ 64 \end{bmatrix}$$

$$C = \begin{bmatrix} 80 \\ -64 \\ 156 \end{bmatrix}$$
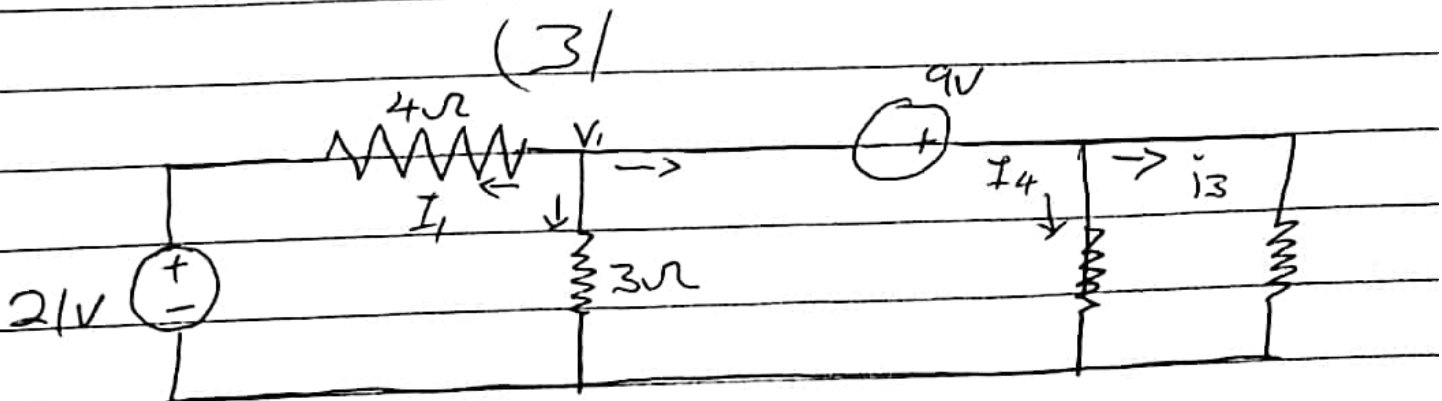
$$\therefore V_1 = 80V, V_2 = -64V, V_3 = 156V$$



6

$$2116 = \frac{246}{216} = \frac{12}{8} = 1.5$$

find the current through 3Ω resistor
using KCL at node 1

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\frac{V_1 - 21}{4} + \frac{V}{3} + \frac{V_1}{6} + \frac{V_1}{2} = 0$$

$$\Rightarrow 3(V - 21) + 4V + 2V_1 + 6V_1 = 0$$

$$= \frac{3V - 63 + 4V + 2V_1 + 6V_1}{12} = 0$$

$$= 7V + 8V_1 - 63 = 0$$

$$7V + 8V_1 = 63 \quad \text{--- (1)}$$

Using KVL at loop 1

$$\rightarrow -V - 9 + V_1 = 0$$

$$-V + V_1 = 9 \quad \text{--- (2)}$$

$$7V + 8V_1 = 63$$

$$-V + V_1 = 9$$

Using my calculator to solve simultaneously

$$V = -0.6V ; V_1 = 8.4V$$

* The current through the 3Ω resistor;

Using nodal analysis

$$I_{3\Omega} = \frac{V - 0}{3}$$

$$= \frac{-0.6 - 0}{3} = \frac{-0.6}{3}$$

$$\therefore I_{3\Omega} = \underline{\underline{-0.2A}}$$


And the current through the 2Ω resistor

$$I_{2\Omega} = \frac{V_1 - 0}{2}$$


$$= \frac{8.4 - 0}{2} = \frac{8.4}{2}$$

$$I_{2\Omega} = 4.2A$$

(4)

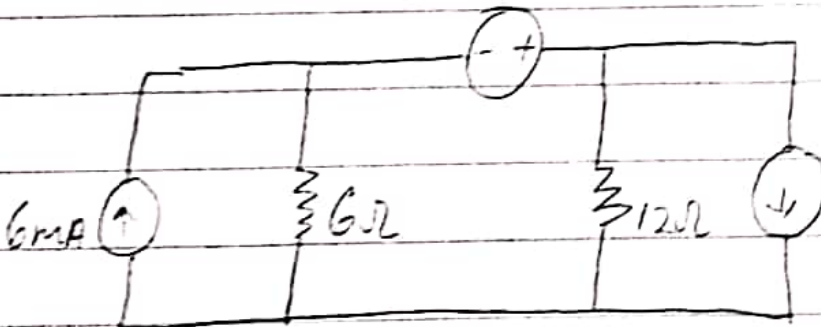

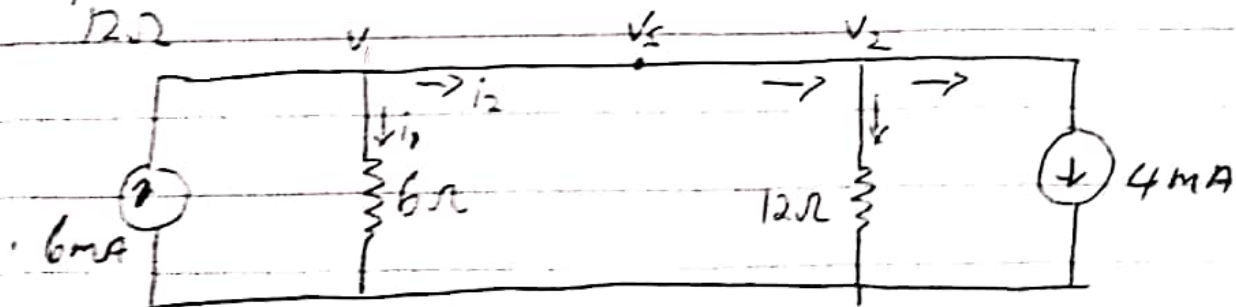find the voltages and currents through 6Ω & 12Ω



8

$$\rightarrow V_1 - V_2 = 6V$$

Assume $V_1 - V_2 = i_2$

Using KCL at node 1

$$6mA = i_1 + i_2$$

$$6mA = \frac{V_1}{6} + (V_1 - V_2)$$

$$6mA = \frac{V_1 + 6(V_1 - V_2)}{6}$$

$$6mA = \frac{V_1 + 6V_1 - 6V_2}{6}$$

$$36mA = 7V_1 - 6V_2$$

At node 2; $i_2 = i_4 + i_3$ $i_3 = 4mA$

$$\rightarrow i_2 = i_4 + 4mA \quad \therefore 4mA = i_2 - i_4$$

$$4mA = \frac{(V_1 - V_2) - V_2}{12}$$

$$4mA = \frac{12(V_1 - V_2) - V_2}{12}$$

$$48mA = 12V_1 - 12V_2 - V_2$$

$$48 = 12V_1 - 13V_2 \quad \text{--- (2)}$$

Solving Simultaneously

$$V_1 = 9.5V, \quad V_2 = 5.1V$$

Current through the 6Ω resistor

$$i_1 = \frac{V_1}{6} = \frac{9.5}{6} = 1.58A$$

9

$$\begin{aligned} I_2 &= V_1 - V_2 \\ &= 9.5 - 5.1 \\ &= \cancel{4.4} \quad 4.4 \text{ A} \end{aligned}$$

$$i_4 = \frac{V_2}{I_2} = \frac{5.1}{12} = \underline{0.43 \text{ A}}$$

$$V_1 = 9.5 \text{ V}, \quad V_2 = 5.1 \text{ V}$$

$$i_1 = 1.58 \quad i_2 = 0.43 \text{ A}$$