

Node 1

$$I_1 + I_2 + I_3 + I_4 = 0$$

$$\frac{V_1}{10} + \frac{V_1}{5} + 2 + \frac{V_1 - V_2}{4} = 0$$

$$\frac{V_1 + 2V_1 + 12 + 5V_1 - 5V_2}{10} = 0$$

$$\frac{8V_1 - 5V_2 + 120}{10} = 0$$

$$8V_1 - 5V_2 + 120 = 0$$

$$8V_1 - 5V_2 = -120 \quad \text{--- (1)}$$

Node 2

$$I_3 + I_5 + I_6 = I_7 + I_8 \quad (I_7 + I_8) \quad I_3 + I_5 + I_6 = I_7$$

$$\frac{V_1 - V_2}{4} + \frac{V_1 - V_2}{2} + 6 = \frac{V_2}{4}$$

$$\frac{V_1 - V_2 + 24 + 12}{2} = \frac{V_2}{4}$$

$$\frac{V_1 - V_2 + 36}{2} = \frac{V_2}{4}$$

$$4V_1 - 4V_2 + 144 = 2V_2$$

$$4V_1 - 6V_2 = -144 \quad \text{--- (2)}$$

$$8V_1 - 5V_2 = -120 \quad \text{--- (1)} \quad \times 6$$

$$4V_1 - 6V_2 = -144 \quad \text{--- (2)} \quad \times 3$$

~~8V1~~

$$48V_1 - 30V_2 = -720$$

$$20V_1 - 30V_2 = -720$$



18/ENAO2/106

$$48V_1 - 20V_1 = -720 = (-720)$$

$$28V_1 = 0$$

$$V_1 = 0$$

2<sup>nd</sup> eq<sup>n</sup>

$$8V_1 - 5V_2 = -120$$

Sub  $V_1 = 0$  into eq<sup>n</sup> (1)

$$8(0) - 5V_2 = -120$$

$$\Rightarrow 5V_2 = 120$$

$$\frac{5V_2}{5} = \frac{120}{5}$$

$$V_2 = 24$$

$$V_1 = 0 \quad V_2 = 24V$$

Current flowing through resistors

$$10\Omega : \frac{V_1}{10} = \frac{0}{10} = 0A$$


$$5\Omega : \frac{V_1}{5} = \frac{0}{5} = 0A$$

$$2\Omega : \frac{V_1 - V_2}{2} = \frac{0 - 24}{2} = -12A$$

$$4\Omega : \frac{V_2}{4} = \frac{24}{4} = 6A$$



6)

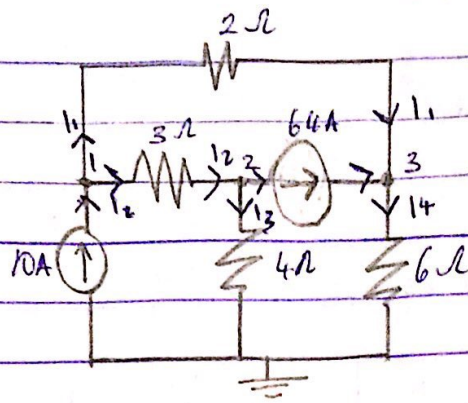

Node 1       $10 = I_1 + I_2$

$$10 = \frac{V_1 - V_3}{2} + \frac{V_2 - V_1}{3}$$

$$10 = \frac{3V_1 - 3V_3 + 2V_1 - 2V_2}{6}$$

$$60 = 5V_1 - 2V_2 - 3V_3 \quad \text{--- (i)}$$

Node 2       $64 + I_3 = I_2$

$$64 + \frac{V_2}{4} = \frac{V_1 - V_2}{3}$$

$$256 + V_2 = \frac{V_1 - V_2}{3}$$

$$768 + 3V_2 = 4V_1 - 4V_2$$

$$768 = 4V_1 - 7V_2 \quad \text{--- (ii)}$$

Node 3       $64 + I_1 = I_4$

$$64 + \frac{V_1 - V_3}{2} = \frac{V_3}{6}$$

$$2 \times \frac{128 + V_1 - V_3}{2} = \frac{V_3}{3} \times 2$$

$$384 + 3V_1 - 3V_3 = V_3$$

$$3V_1 - 4V_3 = -384 \quad \text{--- (iii)}$$



18/EN/907/106

Using Cramer's rule

$$5V_1 - 2V_2 - 3V_3 = 60$$

$$4V_1 - 7V_2 + 0 = 768$$

$$3V_1 + 0 - 4V_3 = -384$$

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ 3 & 0 & -4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ -384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta} \quad V_2 = \frac{\Delta_2}{\Delta} \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ 3 & 0 & -4 \end{vmatrix}$$

$$(+140 + 0 + 0) - (32 + 0 + 63)$$

$$+140 - (+95)$$

$$-140 + 95 \quad +140 - 95$$

$$+45 \quad \Delta = 45$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ -384 & 0 & -4 \end{vmatrix}$$

$$(1680 + 0 + 0) - (6144 + 0 - 8064)$$

$$1680 - (-1920)$$

$$\Delta_1 = 3600$$

$$\Delta_2 = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ 3 & -384 & -4 \end{vmatrix}$$

$$(-15360 + 0 + 4608) - (-960 + 0$$

$$- 6912$$

$$- 10752 - (-7872)$$

$$- 10752 + 7872$$

$$\Delta_2 = -2880$$



18/ENG02/106

$$\Delta_3 = \begin{vmatrix} 5 & -2 & 60 & 5 & -2 \\ 4 & -7 & 768 & 4 & -7 \\ 3 & 0 & -384 & 3 & 0 \\ - & - & - & - & - \end{vmatrix}$$

$$(13440 - 4608 + 0) - (3072 + 0 - 1260)$$
$$8832 - (1812)$$

$$\Delta_3 = 7020$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{3600}{45} = 80 \text{ V}$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{-2880}{45} = -64 \text{ V}$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{7020}{45} = 156 \text{ V}$$