

Name: Nwabugwu Chidubem Atwell

Matric: 17/ENG02/1048

Dept: Computer Engineering

$$V_2 = \Delta_2 \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$$

$$= 5[1968 \times 4] - 0 - 4[1968 \times 4] - [384 \times 5] - 3[0 - [768 - 3 \times 7]]$$
$$= 2880$$


$$V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64V$$

$$V_3 = \begin{vmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ -3 & 6 & 384 \end{vmatrix}$$

$$= 5[[-7 \times 384] - 0] - 4[[-2 \times 384] - 0] - 3[-2 \times 768 - [-7 \times 60]]$$
$$= -7020$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{-45} = 156V$$

$$\therefore V_1 = 86V \quad V_2 = -64V \quad V_3 = 156V$$

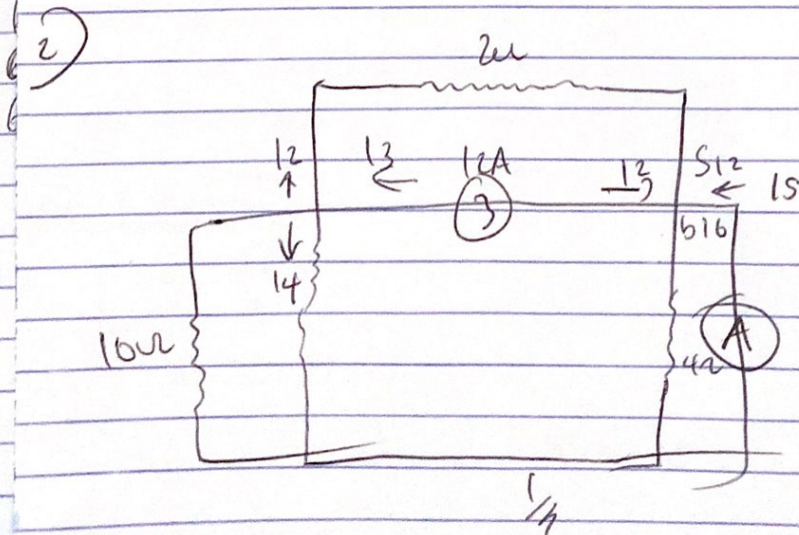

Note 102

$$11 = 12 + 13 + 14$$

$$\frac{V_0 - V_1}{10} = \frac{V_1 - V_2}{2} + 12 + \frac{V_1 - V_2}{5}$$

$$0 - V_2 = 5[V_1 - V_2] + 120 + 2[V_1 - 0]$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 2V_1$$

$$120 = -8V_1 + 5V_2 \quad \dots (1)$$

Note 2

$$13 + 12 + 15 = 16$$

$$12 + \frac{V_1 - V_2}{2} + 6 = \frac{V_2}{4}$$

$$96 + 4[V_1 - V_2] + 48 = 2[V_2]$$

$$144 + 4V_1 - 4V_2 = 2V_2$$

$$144 = -4V_1 + 6V_2 \quad \dots (2)$$

Using Elimination method

$$120 = 8V_1 + 5V_2 = \dots (1) \times 4$$

$$144 = -4V_1 + 6V_2 \dots (2) \times 8$$

$$-480 = 32V_1 - 20V_2 \quad \dots (1)$$

$$-1152 = 32V_1 - 48V_2 \quad \dots (11)$$

Sub (-) eqn 3 from 2

$$= 672 = 0 - 2842$$

$$-672 = -2842$$

$$V_2 = \frac{672}{28}$$

$$V_2 = 24V$$

$$144 = -4v_1 + 6v_2$$


$$v_1 = \frac{144 - 6(24)}{-4}$$

$$v_1 = \frac{144 - 144}{-4} \quad v_1 = 0$$

$$v_2 = 0 \quad v_2 = 24V$$

$$i_1 = 0A \quad i_2 = 0A \quad i_3 = 6A \quad i_4 = 10A$$

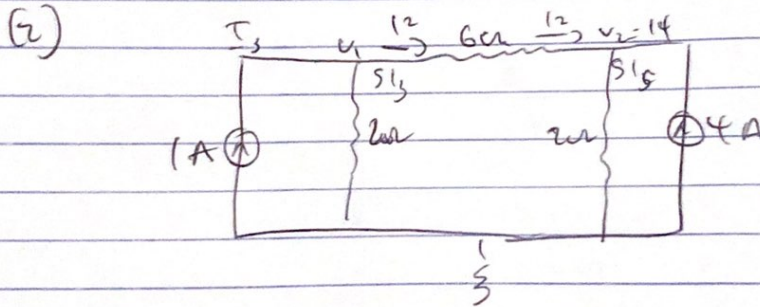2) obtain v_1 and v_2 and the currents for the rest



Note

$$i_1 = i_2 + i_3$$

$$6 = \frac{v_1 - v_2}{6} + \frac{v_2}{5}$$

$$6 = v_1 - v_2 + 3v_2$$

$$6 + 4v_1 - v_2 = 0 \quad (1)$$

Note (2)

$$i_2 = 14 + i_3$$

$$\frac{v_1 - v_2}{6} = 14 + \frac{v_2}{5}$$

$$7(v_1 - v_2) = 168 + 6v_2$$

$$168 = 7v_1 - 13v_2 = 0$$

From eqn (1)

$$v_2 = 4v_1 - 6$$

Sub $v_2 = 4v_1 - 6$ into eqn (2)

$$168 = 7v_1 - 6(4v_1 - 6)$$

$$168 = 7v_1 - 24v_1 + 36$$

$$132 = -17v_1$$

$$v_1 = -132/17$$

$$v_2 = -20$$

Sub $v_1 = -2$ into eqn (1)

$$6 = 4(-2) - v_2$$

$$6 = -8 - v_2$$

$$v_2 = -8 - 6$$

$$v_2 = -14V$$


$$v_1 = -2V \quad v_2 = -14V$$

Currents through Resistor

$$i_2 = \frac{v_1 - v_2}{6} = \frac{-2 - (-14)}{6} = 2A$$

$$i_3 = \frac{v_1}{2} = \frac{-2}{2} = -1A$$
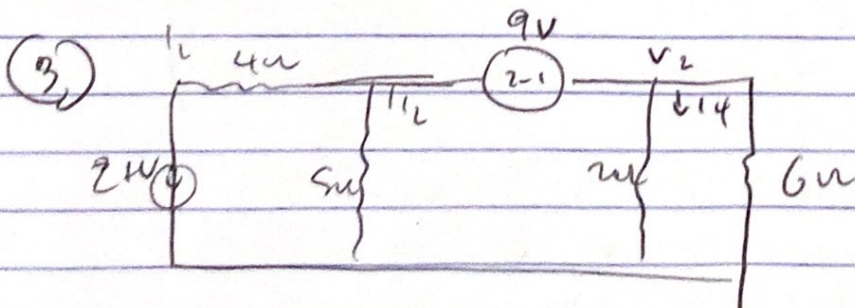
$$i_4 = \frac{v_2}{7} = \frac{-14}{7} = -2A$$



Find the current through the 3Ω & 2Ω resistance

Using KCL Node 1

$$I_1 + I_2 + I_3 + I_4 = 0$$
$$\frac{V_1 - V_2}{4} + \frac{V_1}{3} + \frac{V_2}{6} + \frac{V_2}{2}$$

$$7V_1 + 8V_2 - 63 = 0 \quad (1)$$

Taking KVL for loop

$$-V_1 - 9 + \frac{1}{2} = 0$$

$$-V_1 + V_2 = 9 \quad (2)$$

$$7V_1 + 8V_2 = 63 \quad (1) \times 1$$

$$-V_1 + V_2 = 9 \quad (2) \times 7$$

$$+ 7V_1 + 8V_2 = 63$$

$$7V_1 + 7V_2 = 63$$

$$11V_2 = 126$$

from eqn 2 $-V_1 + V_2 = 9$

$$V_2 = 9 + V_1 \quad \text{put in eqn (1)}$$

$$7V_1 + 8[9 + V_1] = 63$$

$$7V_1 + 72 + 8V_1 = 63$$

$$15V_1 + 72 = 63$$

$$15V_1 = 63 - 72$$

$$15V_1 = -9$$

$$V_1 = \frac{-9}{15}$$

$$V_1 = -0.6V$$

sub $V_1 = -0.6V$ in eqn (1)

$$-[-0.6] + V_2 = 9$$

$$0.6 + V_2 = 9$$


$$V_2 = 9 - 0.6 = 8.4 \text{ V}$$

$$V_1 = 0.6 \text{ V} \quad V_2 = 8.4 \text{ V}$$

Current through 3Ω and 2Ω

$$I_2 = \frac{V_1}{3} = \frac{-0.6}{3} = 0.2 \text{ A at } 3\Omega$$
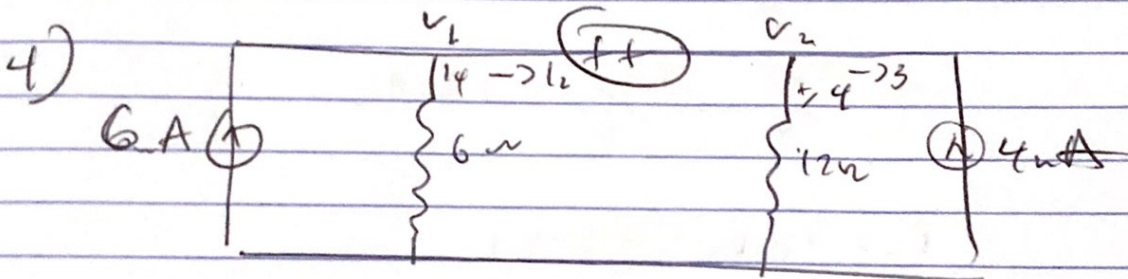
$$I_4 = \frac{V_2}{4} = \frac{8.4}{4} = 2.1 \text{ A at } 2\Omega$$



Find the and i_1 at the voltage and the current for the 6Ω and 12Ω resistor

$$\text{Take } V_1 - V_2 = 6 \text{ V} \Rightarrow I_2$$

At node 1, using KCL

$$6 \text{ mA} = I_1 + I_2$$

$$6 \text{ mA} = \frac{V_1 - 0}{6} + (V_1 - V_2)$$

$$36 = V_1 + 6 [V_1 + V_2]$$

$$36 = V_1 + 6V_1 = 6V_2$$

$$36 = 7V_1 - 6V_2 - (1)$$

AE Mode 2

$$I_2 = I_3 + I_4$$

$$V_1 - V_2 = \frac{48 \text{ mA} + V_2 - 0}{12}$$

$$12(V_1 - V_2) = 48 + V_2$$

$$48 = 12V_1 - 12V_2 - V_2$$

$$48 = 12V_1 - 13V_2 \quad \dots (2)$$

Solving V_1 and V_2 Simultaneously we have

$$V_1 = 9.5 \text{ V}$$

$$V_2 = 5.1 \text{ V}$$

Current through the 6Ω resistor

$$i_f = \frac{V_1}{6} = \frac{9.5}{6} = 1.58 \text{ A}$$

$$i_2 = V_1 - V_2 = 9.5 - 5.1 \\ = 4.4 \text{ m}$$

Current through 12Ω

$$I_4 = \frac{V_2}{12} = \frac{5.1}{12} = 0.43 \text{ A}$$

$$V_1 = 9.5 \text{ V}$$

$$V_2 = 5.1 \text{ V}$$

$$I_1 = 1.58 \text{ A}$$

$$I_4 = 0.43 \text{ A}$$