

NAME: ESADUWA ATAIRO ROBERT

DEPARTMENT: MECHANICAL ENGINEERING

COURSE CODE: EEE326


MATRIC: 17/ENG06/032

Section A

Question 1

Develop the theoretical framework required for the correction of the power factor for a multi-sectioned industrial complex from $\cos \phi_1$ to $\cos \phi_2$ where $\phi_1 > \phi_2$; $P_1 = P_2$; $Q_1 > Q_2$; and $S_1 > S_2$ to determine the kVAR rating of the capacitor (Q_{CAP}) and the magnitude of the capacitor (C) in farads required to correct the power factor of the complex. **USE APPROPRIATE PHASOR**

Diagram

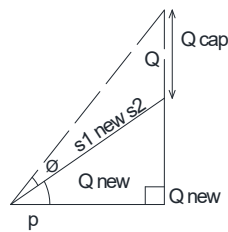

$Q_{Cap} = P (\tan \phi - \tan \phi_{new})$ The size of capacitor bank required to compensate the load reactive power to its new value.

$Q_{cap} = v^2 / x_c = \omega c v^2 =$ reactive power generated by a single phase transformer

Question 2

What determines the power factor of the Dangote Cement Factory at Abajana, Kogi State?

Answer

Power factor is an expression of energy efficiency. It is usually expressed as a percentage—and the lower the percentage, the less efficient power usage is.


Power factor (PF) is the ratio of working power, measured in kilowatts (kW), to apparent power, measured in kilovolt amperes (kVA). Apparent power, also known as demand, is the measure of the amount of power used to run machinery and equipment during a certain period. It is found by multiplying (kVA = V x A). The result is expressed as kVA units.

PF expresses the ratio of true power used in a circuit to the apparent power delivered to the circuit. A 96% power factor demonstrates more efficiency than a 75% power factor. PF below 95% is considered inefficient in many regions.

Question 3

The power factor (pf) of Eleme Petrochemical Industry PortHarcourt is given as $\cos(\alpha \pm \beta)$; what is the state of the pf of the complex when $\alpha > \beta$; $\beta > \alpha$ and $\alpha = \beta$. Draw the respective Phasor diagrams.

Answer

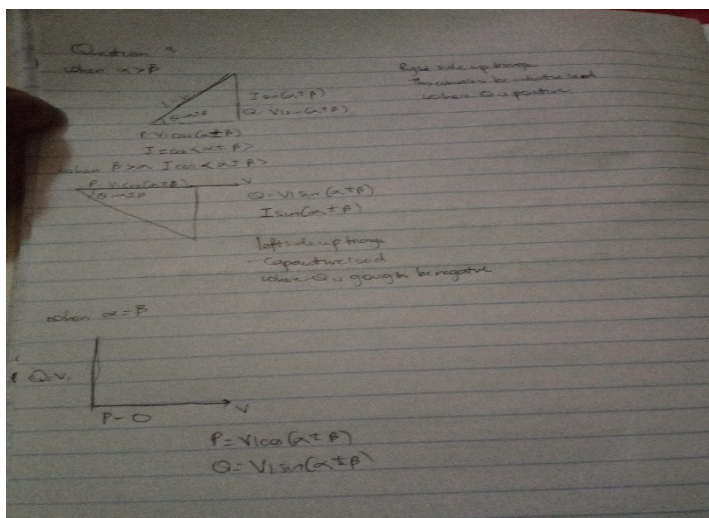

Question 4

For $\alpha > \beta$; Write an expression for P and Q respectively with units in W and VAR. What does P and Q REPRESENT?

Answer

$$P=I*V\cos(\alpha\pm\beta)$$

$$Q=I*V\sin(\alpha\pm\beta)$$

Where,

P: active power(kW)

Q: reactive power(kVAR)

Question 5

Justify the need for power factor correction to ABUAD and PHCN or an IPP

Answer

Savings on the electricity bill

Power factor correction eliminates penalties on reactive energy, decreases demand on kVA, and reduces power losses generated in the transformers and conductors of the installation.

Increased available power

Fitting PFC equipment on the low voltage side increases the power available at the secondary of a MV/LV transformer. A high power factor optimises an electrical installation by allowing better use of the components.

Reduced installation size

Installing PFC equipment allows conductor cross-section to be reduced, as less current is absorbed by the compensated installation for the same active power.

Reduced voltage drops

Installing capacitors allows voltage drops to be reduced upstream of the point where the PFC device is connected, therefore preventing overloading of the network and reducing harmonics.

Question 6

Why is Q needed in an industrial complex with numerous induction motors?

Answer

Voltage control in an electrical power system is important for proper operation for electrical power equipment to prevent damage such as overheating of generators and motors, to reduce transmission losses and to maintain the ability of the system to withstand and prevent voltage collapse.

Decreasing reactive power causing voltage to fall while increasing it causing voltage to rise. A voltage collapse may be occurs when the system try to serve much more load than the voltage can support.

When reactive power supply lower voltage, as voltage drops current must increase to maintain power supplied, causing system to consume more reactive power and the voltage drops further . If the current increase too much, transmission lines go off line, overloading other lines and potentially causing cascading failures.

If the voltage drops too low, some generators will disconnect automatically to protect themselves. Voltage collapse occurs when an increase in load or less generation or transmission facilities causes dropping voltage, which causes a further reduction in reactive power from capacitor and line charging, and still there further voltage reductions. If voltage reduction continues, these will cause additional elements to trip, leading further reduction in voltage and loss of the load. The result in these entire progressive and uncontrollable declines in voltage is that the system unable to provide the reactive power required supplying the reactive power demands

First, the transmission system itself is a nonlinear consumer of reactive power, depending on system loading. At very light loading the system generates reactive power that must be absorbed, while at heavy loading the system consumes a large amount of reactive power that must be replaced. The system's reactive-power requirements also depend on the generation and transmission configuration.

Section B

Question 7

An industrial load absorbs 5 MVA at a pf of 40% capacitive at 6kV. To improve the pf upto 85% capacitive, determine Q and C of the required capacitor. State how the correcting equipment will be integrated into the industrial power network for this load.

Answer

$$\text{Load(s)} = 5000\text{KVA}$$

$$\text{Power factor} = 40\% = 0.4 \text{ (capacitive)}$$

$$\text{Frequency} = 50\text{Hz}$$

$$P = I_s I_c \cos \theta$$

$$P = I_s I_c \text{Pf}_{(\text{old})} = 5000 \times 10^3 (0.4) = 2000\text{KW}$$

$$\theta_{(\text{old})} = \cos^{-1} \text{Pf}_{(\text{old})} = \cos^{-1} (0.4) = -66.42$$

The angle will be negative because the old power factor is inductive

Using trigonometry

$$\tan \theta_{\text{old}} = Q_{(\text{old})} / P$$

$$Q_{\text{old}} = P \tan \theta_{(\text{old})} = (2000 \times 10^3) (\tan(-66.42))$$

$$Q_{(\text{old})} = -4582178.329\text{var}$$

$$\theta_{(\text{new})} = \cos^{-1} \text{Pf}_{(\text{new})} = \cos^{-1} (0.85) = -31.79 \text{ (because also its capacitive)}$$

$$\tan \theta_{(\text{new})} = Q_{(\text{new})} / P$$

$$Q_{(\text{new})} = P \tan \theta_{(\text{new})} = 2000 \times 10^3 (\tan(-31.79)) = -1239569.332\text{var}$$

$$\Delta Q = Q_{(\text{new})} - Q_{(\text{old})}$$

$$\Delta Q = -1239569.332 - (-4582178.329)$$

$$\Delta Q = 3342608.997\text{var}$$

$$C = \Delta Q / (2\pi f (V_s^2))$$

C

$$= \frac{3342608.997}{2 \times 3.142 \times 50 \times (6000)^2}$$

$$C = 2.96 \times 10^{-4}$$

$$C = 29.6\text{mf}$$

Question 8

An industrial load absorbs 5 MVA at a pf of 40% inductive at 6kV. To improve the pf. upto 85% inductive, determine Q and C of the required and necessary capacitor. State how the correcting equipment will be integrated into the industrial power network for this load. How different are the values of Q7 and Q8 in terms of magnitude and type of pf correction?

Answer

$$\text{Load(s)} = 5000\text{KVA}$$

$$\text{Power factor} = 40\% = 0.4 \text{ (inductive)}$$

$$\text{Frequency} = 50\text{Hz}$$

$$P = |S|\cos\theta$$

$$P = |S|P_{f(\text{old})} = 5000 \times 10^3 (0.4) = 2000\text{KW}$$

$$\theta_{(\text{old})} = \cos^{-1}P_{f(\text{old})} = \cos^{-1}(0.4) = 66.42$$

The angle will be positive because the old power factor is inductive

Using trigonometry

$$\tan\theta_{\text{old}} = Q_{(\text{old})}/P$$

$$Q_{\text{old}} = P \tan\theta_{(\text{old})} = (2000 \times 10^3)(\tan(66.42))$$

$$Q_{(\text{old})} = 4582178.329 \text{ var}$$

$$\theta_{(\text{new})} = \cos^{-1}P_{f(\text{new})} = \cos^{-1}(0.85) = 31.79 \text{ (because also its inductive)}$$

$$\tan\theta_{(\text{new})} = Q_{(\text{new})}/P$$

$$Q_{(\text{new})} = P \tan\theta_{(\text{new})} = 2000 \times 10^3(\tan(31.79)) = 1239569.332 \text{ var}$$

$$\Delta Q = Q_{(\text{old})} - Q_{(\text{new})}$$

$$\Delta Q = 4582178.329 - 1239569.332$$

$$\Delta Q = 3342608.997 \text{ var}$$

$$C = \Delta Q / (2\pi f (Vs^2))$$

C

$$\frac{3342608.997}{2 \times 3.142 \times 50 \times (6000)^2}$$

=

$$C = 2.96 \times 10^{-4}$$

$$C = 29.6\text{mf}$$

If this load is an electric motor or most any other industrial AC load, it will have a lagging (inductive) power factor, which means that we'll have to correct for it with a capacitor of appropriate size, wired in parallel. This correction, of course, will not change the amount of true power consumed by the load, but it will result in a substantial reduction of apparent power.

Question 9

The National Universities Commission (NUC) Complex in Abuja has a total load of 100kW. It is powered by a 415 V, three phase, 4 wire power supply. The power factor is 0.85 lagging and NUC desires to avoid the payment of penalties for this poor power factor. What Should the facility manager advise NUC management to do? If an improved pf of 0.95 lagging is desired, determine the magnitude of the required Q and C.

Answer

Real power, $p=100\text{KW}$

$V=415\text{V}$

3 phase transformer

Original $\text{pf}=0.85$

Improved $\text{Pf desired}=0.95$

Recall, $\text{Pf}=\cos\theta$

Therefore, $\theta=\cos^{-1}(\text{pf})$

$\theta_1=\cos^{-1}(0.85)=31.7883$

$\theta_2=\cos^{-1}(0.95)=18.1949$

$\text{Tan } \theta_1=\text{tan } (31.7883)=0.6197$

$\text{Tan } \theta_2=\text{tan } (18.1949)=0.3287$

Therefore,

Reactive Power, $Q=P\sin(\theta_1 \pm \theta_2)$

$= (100 \times 10^3) \times \sin(31.7883 - 18.1949)$

$=23.503\text{KVAR}$

Required capacitor, $C=P(\tan \theta_1 \pm \tan \theta_2)$

$= (100 \times 10^3) \times (0.6197 - 0.3287)$

$=29.1\text{KVAR}$

Question 10

Undertake a comparative analysis as an Electrical Power Management Consultant and use techno – economic facts and data to advise a client (Globacom Nigeria Ltd) requiring a 20kW induction motor to power its intended fruit juice factory from motor choices M_1 and M_2 given the following details:

Motor/parameters	M_1	M_2
kW	20	20
Phases	3	3
Line Voltage	415	415
pf	0.85	0.95
S	S_1	S_2
Q	Q_1	Q_2
PREVIOUS METER	23,000	

READING (kWhr)	
NEW METER READING (kWhr)	25,000
kWhr charge	#55/kWhr
Demand(kW) Charge	#35/kW
Capacity (kVA) Charge	#70/kVA
Reactive Power (kVAR) Charge	#25/kVAR

Justify clearly your choice of recommended motor.

Answer

$$S_1 = 23529.41176 \text{ var}$$

$$S_2 = 21052.63158 \text{ var}$$

Where S_1 and S_2 are gotten from the equation P / Pf

Where P_1 and $P_2 = 20 \times 10^3$

$$\theta_1 = \cos^{-1}(0.85) = 31.79$$

$$\theta_2 = \cos^{-1}(0.95) = 18.19$$

$$Q_1 = \sin(31.79) \times 23529.41176$$

$$Q_1 = 12395.46948 \text{ var}$$

$$Q_2 = \sin(18.19) \times 21052.63158$$

$$Q_2 = 6571.981313 \text{ var}$$

The above equation is to show the different induction motor the amount of reactive power they both possess

In order to pick the best choice of induction motor, the client must consider the following factors:

Determine cost-effectiveness AC motors are available in a range of efficiencies. Although the economics will vary by application, replacing an old standard-efficiency motor with a newly installed, premium-efficiency motor under typical operation will often pay for its price in reduced energy bills within a year or two.

Consider downsizing when a motor is operating at less than 40% of its rated output. The following circumstances are opportunities for choosing premium-efficiency motors:

When purchasing a new motor where lower-energy-efficient units can still be sold Instead of rewinding failed standard-efficiency or energy-efficient motors. To replace an operable-but-inefficient motor for greater energy savings and reliability

Account for the motor's impact on power factor Power factor is an indicator of how much of a power system's capacity is available for productive work. Low power factor is undesirable because it increases the load on a building's electrical system, and utilities sometimes charge customers a penalty for facilities with low power factor. Because power factor is lower when a motor is lightly loaded, be sure to choose the right-sized motor. You can also specify a motor with a high power factor, but such models sometimes have lower efficiency. The ultimate selection depends, in part, on whether a facility is subject to power factor penalty charges. A facility with a significant number of induction motors and a low power factor can solve the problem with premium-efficiency motors that are properly sized. If new motors are not an option, other power factor–correction methods are available, including static capacitor banks, rotary condensers, and static and dynamic volt-ampere reactive devices.

From the above factors mentioned above, the best and most economical motor choice to go with would be motor 2(M2)

The calculation solved above showed that MOTOR 2 (M2) is the best option because when the reactive power is low it saves cost and increases efficiency