

415V


$f = 50$

$P = 74.6 \text{ kW}$

$\text{pf} = \cos \theta = 0.7$

~~415A~~ $415/\sqrt{3} = 239.6$

$\cos^{-1} 0.7 = \theta = 45.5$

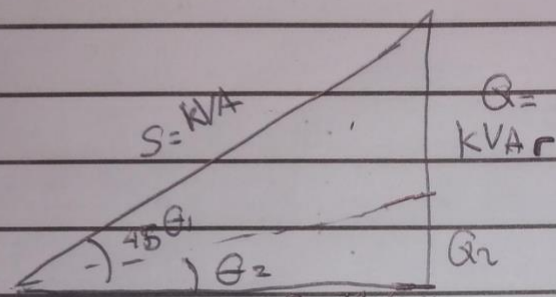

$\theta_2 = \cos^{-1}(1) = 0$
(1)

$Q (\text{kVAR}) = S (\text{kVA}) \sin \theta$

$\Rightarrow \tan \theta_1 = \frac{Q}{P} \quad \tan 45.5 = \frac{Q}{74.6}$

$Q = 75.9 \text{ kVr}$

$\tan \theta_2 = \frac{Q_2}{P} = \tan(0) \times P = Q_2$

$Q_2 = 0$

$\Delta Q = Q_1 - Q_2 = 75.9 \text{ kVr}$

~~Wk~~ ~~Q = P(\tan \theta_1 - \tan \theta_2)~~
 $\Rightarrow Q = 74.6 (\tan 45.5 - \tan 0)$

$$\Delta Q = \frac{V^2}{2\pi f C}$$

$$\Delta Q = C 2\pi f V^2$$

$$C = \frac{\Delta Q}{2\pi f V^2} \Rightarrow \frac{75.9}{2 \times \pi \times 50 \times (239.6)^2}$$

$$C = 4.20 \times 10^{-6} \text{ F}$$

I =

ii)

0.9 lag


$$\cos(\theta_2) = 0.9$$

$$\theta_2 = \cos^{-1}(0.9)$$

$$\theta_2 = -25.8$$

$$Q_2 = P \tan \theta_2$$

$$Q_2 = -36.06 \text{ kVAR}$$

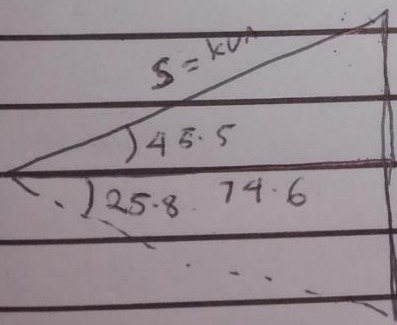

$$Q = 75.9$$

ΔQ

$$Q_2 = 111.96$$

$$= 75.9 - -36.06$$

$$= 75.9 + 36.06$$

$$= 111.96 \text{ kVAR}$$

$$C = P (\tan \theta_1 - \tan \theta_2)$$

$$= 74.6 (\tan(45.5) - \tan(-25.8))$$

$$\Delta Q = C 2\pi f V^2$$

$$C = \frac{\Delta Q}{11.96}$$

$$2\pi \times 50 \times (239.6)^2$$

$$= 6.207 \times 10^{-6} \text{ F}$$

②

$$V_L = 415 \text{ V}$$

$$V_{\text{phase}} = \frac{415}{\sqrt{3}} = 239.6 \text{ V}$$

$$p_{\text{poles}} = 6$$


$$f = 50 \text{ Hz}$$

$$\frac{\text{stator}}{\text{rotor}} = \frac{6}{5} = \frac{1}{k} \Rightarrow k = \frac{5}{6} = 0.83$$

$$\text{stator } R_1 = 0.25 + j0.75 \Omega$$

$$R_2 = 1.73 + j0.52$$

$$s = 1$$

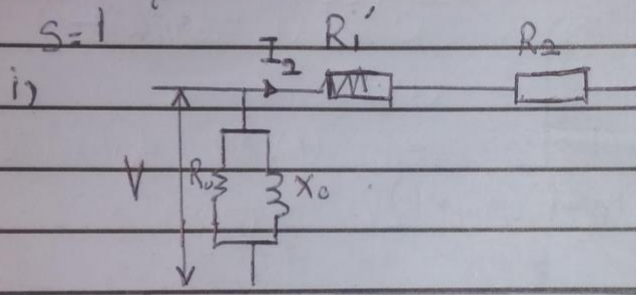

(i)

$$R_1' \text{ (referred to the rotor)} = R_1 \times k^2$$

$$R_1' = (0.25 + j0.75) \times (0.83)^2 = 0.172 + j0.516$$

$$I_2 = \frac{V_{\text{phase}}}{R_1' + R_2} = \frac{239.6}{0.172 + j0.516 + 1.73 + j0.52}$$

$$I_2 = 97.14 - j52.92$$

$$I_2 = \underline{\underline{110.62 \angle -28.57^\circ \text{ A}}}$$

BRIGGS FRANCIS (3)

$$3) f = 50 \text{ Hz}$$

$$N_{dc} = 2000 \text{ rpm}$$

$$I = 0.7 \text{ A}$$

$$R = 15 \Omega$$

$$I = 0.25 \text{ A}$$

$$V_{ac} = 220 \text{ V}$$

(i)

$$\cancel{V_{ac}} = E_b = IR$$

$$E_b = V_{dc} - IR$$

$$E_b = 220 - 0.7(15) = 209.5 \text{ V}$$

$$IR = \text{resistance drop} = 10.5 \text{ V}$$

for ac

$$\text{reactance drop} = IX = 0.7 \times 2\pi fL$$

$$= 0.75 \times 2 \times 50 \times \pi \times 0.25$$

$$= 58.904 \text{ V}$$

$$\text{Counter emf} = E = \sqrt{V^2 - (IX)^2} - IR$$

$$E = \sqrt{(220)^2 - (58.90)^2} - 10.5$$

$$E = \underline{\underline{201.46 \text{ volts}}}$$

$$N_{ac} = N_{dc} \times \frac{E}{E_b} \Rightarrow \frac{2000}{209.5} \times 201.46$$

$$= 1923 \text{ rpm Ans}$$

power factor = (ii)

$$\cos \phi = \frac{E + IR}{V} = \frac{201.46 + 10.15}{220}$$

$$\text{pf} = 0.96$$

BRIGGS FRANCIS (4)

$$\text{Torque} = \frac{9.55 \times P}{N \times r}$$

$$P = F \times l$$

$$\Rightarrow \frac{9.55 \times 1923}{1923} \quad \frac{9.55 \times 201.4 \times 0.7}{1923}$$

$$= \underline{\underline{0.70 \text{ Nm}}}$$

iv) Unvers? motor

