

Question 1

$V = 415V$, 3- ϕ , 4 wire, $f = 50Hz$
 $P = 74.6$, $P.f = 0.7$, $eff. = 85\%$

Unity $\cos \theta = 1$

$\cos \theta = \frac{KW}{KVAR}$

$$\frac{KW}{2\sqrt{3}fV^2}$$

$$KVAR = P \times \left(\frac{1}{\cos \theta} \right) \times \tan \theta$$

$$\text{actual P.f} = \cos \theta = 0.7$$

$$\theta = \cos^{-1} 0.7$$

$$= 45.57$$

$$\tan (45.57) = 1.0201$$

$$\text{target P.f} \Rightarrow \cos \theta = 1$$

$$\theta = \cos^{-1} 1 = 0$$

$$\tan 0 = 0$$

$$KVAR = 74.6 \times (1.0201 - 0)$$

$$= 76.0995$$

$$= 76.1$$



2

17/ENG06/028

1.30DL

$$C = \frac{76 \cdot 10}{2\pi \times 50 \times \left(\frac{415}{\sqrt{3}}\right)^2}$$
$$= 4.22 \times 10^{-6} \text{ C}$$

(ii) 0.9 lagging

$$\text{actual p.f} = 1.0201$$

$$\text{target p.f} = \cos \theta = 0.9$$

$$\theta = \cos^{-1}(0.9)$$

$$\theta = 154.16$$

$$\tan \theta = \tan(154.16)$$

$$= -0.48$$

$$\text{KVAR} = 74.6 \times (1.0201 - (-0.48))$$

$$= 119.90 \approx 112$$

$$C = \frac{112}{2\pi \times 50 \times \left(\frac{415}{\sqrt{3}}\right)^2}$$

$$= 6.21 \times 10^{-6} \text{ C}$$

3

27/11/ENG06/008

300L

Question 2

$$V_L = 415 \text{ V}$$


No of Poles = 6

$$f = 50 \text{ Hz}$$

$$k = \frac{5}{6} = 0.83$$

$$R_1 = Z_1 = 0.25 + j0.75 \quad \text{--- stator}$$
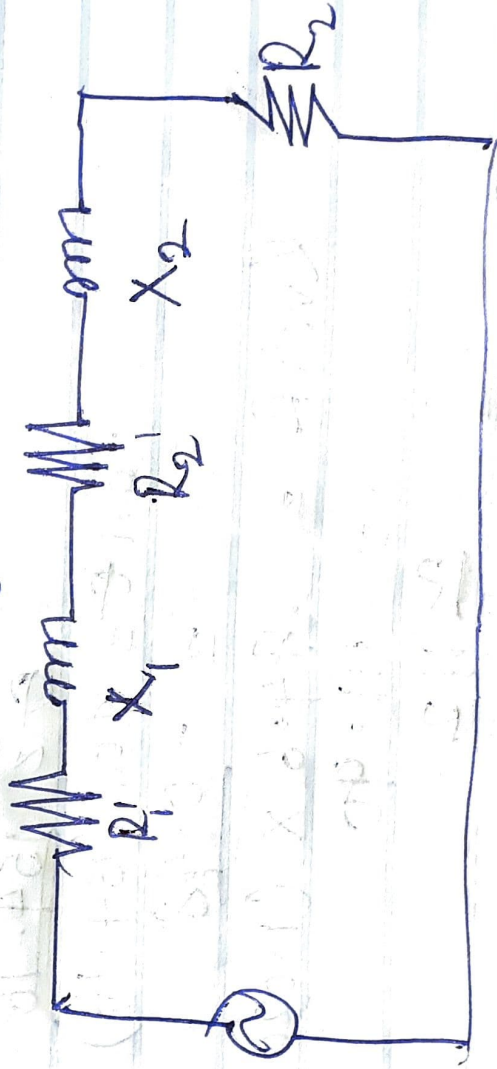
$$Z_2 = 1.173 + j0.52 \quad \text{--- rotor}$$



Supply voltage per phase; $V = \frac{415}{\sqrt{3}}$

$$= 239.60 \text{ V}$$

referring to rotor
 $R_{02} = (R_2 + k^2 R_1)$

$$= (1.173 + (\frac{5}{6})^2 \times 0.25)$$

$$= \underline{\underline{1.347 \Omega}}$$

4

2017/ENG06/008

JG 300L

$$X_{02} = (X_2 + k^2 X_1) \\ = j(0.52 + (\frac{5}{6})^2 \times 0.75) \\ = \underline{\underline{1.041}}$$

$$Z_{02} = R_{02} + X_{02} \\ = 1.347 + j1.041 \\ = \sqrt{(1.347)^2 + (j1.041)^2} \\ = \underline{\underline{1.7\Omega}}$$

to find rotor current

$$I_2 = \frac{E_2}{Z_{02}}$$

Recall that $E_2 = 2 \text{ kV}$

$$= 239.60 \times 0.85 \\ = \underline{\underline{199.67 \text{ V}}}$$

$$\therefore I_2 = \frac{199.67}{1.7} \\ = \underline{\underline{117.45 \text{ A}}}$$

300 L

300 L


Question 3

$f = 50 \text{ Hz}$, $1/4 \text{ hp}$, $N_p = 2000 \text{ rpm}$, $V = 220 \text{ V}$
 15Ω and 0.25 H

On DC supply,

Supply voltage $= 220 \text{ V}$

Currents drawn, $I = 0.7 \text{ A}$

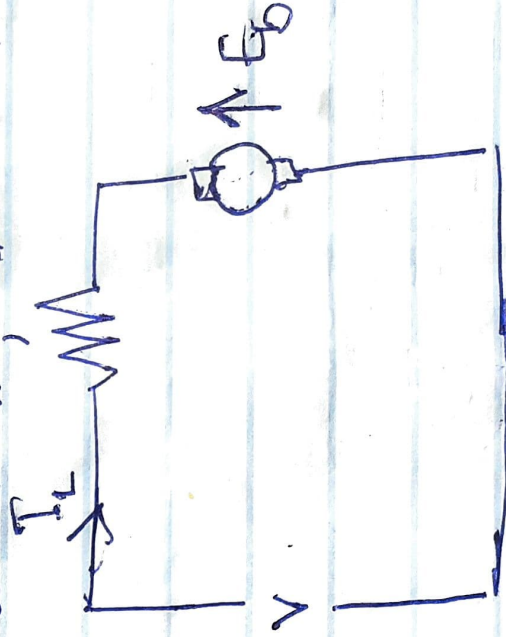

$$V - E_b = I_L * R$$

$$V - [I_L * R] = E_b$$

$$E_b = 220 - [0.7 * 15]$$

$$= 209.5 \text{ V}$$

Speed on DC,

$$N_{d0} = 2000 \text{ rpm}$$

6

11/ENG06/008

300 L

Question 3

On AC supply

supply voltage $e = 220\text{V}$ Current drawn, $I_L = 0.7\text{A}$ Reactance drop $= I_L * R = 0.7 \times 15 =$

$$= 10.5\text{V}$$


Reactance voltage drop $= I_L \times X_L$

$$= 0.7 \times 2\sqrt{3} \times 15$$

where $X_L = 2\sqrt{3} \times 15$

$$= 0.7 \times 2\sqrt{3} \times 30 \times 0.25$$

$$= 54.98\text{V}$$

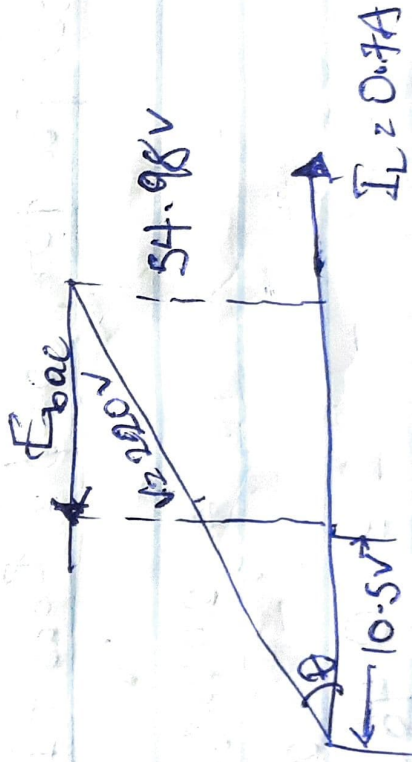

$$E_{bac} = \sqrt{V^2 - [I_L R]^2} = I_L R$$

$$= \sqrt{(220)^2 - (54.98)^2} = 10.5\text{V}$$

$$= 202.52\text{V}$$

7

17/ENG 06/08

300L

3(i) Recall speed. constant equation

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}$$

$$\text{So } \frac{E_{bac}}{E_{bdc}} = \frac{N_{ac}}{N_{dc}}$$

By making N_{ac} subject of the formula

$$N_{ac} = N_{dc} \times \frac{E_{bac}}{E_{bdc}}$$

$$= 2000 \times \frac{202.52 \text{ V}}{209.5 \text{ V}}$$

$$N_{ac} = 1933.37 \text{ rpm}$$

3(ii) Power factor, $\cos \phi = \frac{E_{bac} + IR}{V}$

$$= \frac{202.52 + 10.5}{220}$$

$$= 0.968 \text{ lagging}$$

3(iii) Torque developed $T_{wo} = E_{bac} \times I$
 $T_{ac} = \frac{E_{bac} \times I}{\omega}$

where ω is speed in rad/s

8

11/ENGT061008

300L

$W = 2\pi n$, where n is speed in rev/s

$$T_{ac} = \frac{E_{ave} \times I_L}{2\pi \times \frac{N_{ac}}{60}}$$

$$= \frac{202.62 \times 0.7 \times 60}{2\pi \times 1933.37}$$

$$= 0.700 \text{ Nm}$$

30) Universal motor