

E BARETONBOFA TIEDOR RYAN

17/EMG06/023 MECHANICAL

EEE 326 TEST.

17/06/20.

ANSWER TO QUESTION 1

$$V = 415V$$

$$P = 74.6 \text{ kW}$$

$$f = 50\text{Hz}$$

$$\% \text{ Efficiency} = 85\%$$

$$\text{Power Factor} = 0.7.$$

$$i) \text{ Unity} = 1 ; C = \frac{\text{KVAR}}{2\pi f v^2}$$

$$\text{KVAR} = P (\tan(\text{p.f. actual}) - \tan(\text{p.f. target}))$$

$$\text{P.F. (actual)} \Rightarrow \cos \theta = 0.7$$

$$\theta = \cos^{-1}(0.7) = 45.57^\circ$$

$$\tan(45.57^\circ) = 1.0201$$

$$\text{P.F. (target)} \Rightarrow \cos \theta = 1$$

$$\theta = \cos^{-1}(1) = 0$$

$$\tan(0^\circ) = 0$$

$$\text{KVAR} = 74.6 \times (1.0201 - 0)$$

$$74.6 \times 1.0201 = 76.10$$

$$C = \frac{76.10}{2 \times \pi \times 50 \times (415^2)}$$

$$= 0.0000014$$

$$= \underline{\underline{1.4 \times 10^{-6} \text{ C}}}$$

17/ENGD06/023

ii) 0.9 Lagging

$$\# \text{ P.F}_{\text{actual}} = 1.0201$$

$$\text{P.F}_{\text{target}} = \cos \theta = 0.9$$

$$\theta = \cos^{-1}(0.9)$$

$$= 26.16$$

$$\tan \theta = -0.48$$

$$\text{KVAR} = 74.6 \times (1.0201 - (-0.48))$$

$$= 111.90$$

$$\approx 112$$

$$C = \frac{\text{KVAR}}{2\pi f v} = \frac{112}{2 \times \pi \times 50 \times (415)^2}$$

$$= \frac{112}{2 \times \pi \times 50 \times (415)^2}$$

$$= \frac{112}{2 \times \pi \times 50 \times 172225} = 0.0000020706$$

$$\approx \underline{\underline{2.07 \times 10^{-6} \text{ C}}}$$

IT/ENG06/023

ANSWER To QUESTION 3

$F = 50\text{Hz}$, 0.25hp , $N = 2000\text{rpm}$
 $V = 220$, $R = 15\ \Omega$, $H = 0.25$.

On DC Supply...

Voltage supplied = 220V

Current (I) = 0.7A

$$V - E_b = I_L \times R$$


$$V - (I_L \times R) = E_b$$

$$E_b = 220 - (0.7 \times 15)$$

$$= 220 - 10.5$$

$$= 209.5\text{V}$$

DC speed, (N) = 2000rpm

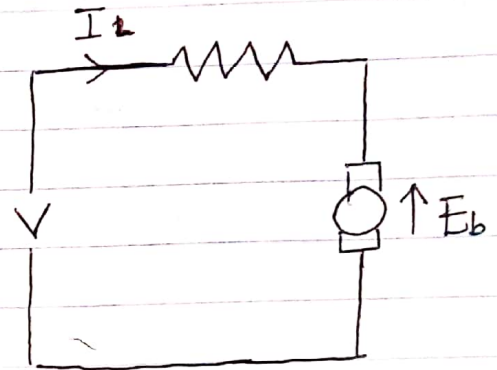

On AC Supply...

Voltage Supplied = 220V


Current, (I_L) = 0.7A

Drop in Resistance = $I_L \times R = 0.7 \times 15 = 10.5\text{V}$

Drop in Reactance Voltage = $I_L \times X_L$
 $= 0.7 \times 2\pi fL$

$$= 0.7 \times 2 \times \pi \times 50 \times 0.25$$
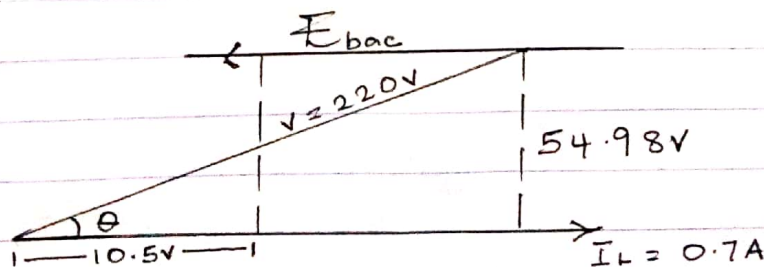
$$= \underline{\underline{54.98\text{V}}}$$



$$E_{bac} = \sqrt{V^2 - (X_L)^2} - IR$$

$$= \sqrt{(220)^2 - (54.98)^2} - 10.5 = \underline{\underline{202.52\text{V}}}$$

17/ENG06/023

(i) Equation for speed constant

$$\Rightarrow \frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}$$

Therefore;

$$\frac{E_{bac}}{E_{b1c}} = \frac{N_{ac}}{N_{dc}}$$

$$N_{ac} = \frac{N_{dc} \times E_{bac}}{E_{dc}}$$

$$= \frac{2000 \times 202.52}{209.5}$$

$$N_{ac} = \underline{\underline{1933.37 \text{ rpm}}}$$

(ii) Power Factor, $\cos \phi = \frac{(E_{bac} + IR)}{V}$

$$= \frac{202.52 + 10.5}{220}$$
$$= \underline{\underline{0.968 \text{ lagging}}}$$

(iii) Torque Developed by the motor

$$T_k \cancel{I_a} = E_{bac} \times I$$

Re-arranging;

$$T_{ac} = \frac{E_{bac} \times I}{\omega}$$

(ω is speed in rad/s).

$$\omega = 2\pi n \text{ (n is speed in rpm)}$$

$$T_{ac} = \frac{E_{bac} \times I}{2\pi \times (N_{ac} \div 60)}$$

$$= \frac{202.52 \times 0.7 \times 60}{2\pi \times 1933.37}$$

$$= \underline{\underline{0.700 \text{ Nm}}}$$

17/ENG06/023

No 3 (iv) The Universal Motor

ANSWER TO QUESTION 2.

$$V = 415$$


$$\text{No of Poles} = 6$$

$$f = 50 \text{ Hz}$$

$$k = \frac{5}{6} = 0.23$$

$$R \Rightarrow Z_1 = 0.25 + 0.75j \text{ (Stator)}$$

$$Z_2 = 1.173 + 0.52j \text{ (Rotor)}$$

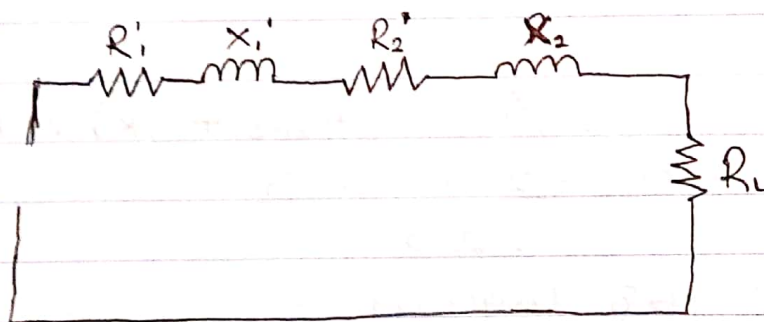

$$\text{Voltage supply per phase, } V = 415 \div (\sqrt{3}) \\ = 239.60 \text{ V}$$

With respect to Rotor;

$$R_{02} = (R_2 + k^2 R_1) \\ = (1.173 + (\frac{5}{6})^2 \times 0.25) \\ = 1.347 \Omega$$

$$X_{02} = (X_2 + k^2 X_1) \\ = j(0.52 + (\frac{5}{6})^2 \times 0.75) \\ = 1.041 \Omega$$

$$Z_{02} = R_{02} + X_{02} \\ = 1.347 + j 1.041 = \sqrt{(1.347)^2 + (1.041)^2} = \underline{\underline{1.7 \Omega}}$$

17/EN0406/023

Current in Rotor;

$$I_2 = \frac{E_2}{Z_{02}}$$
$$= \frac{K V_2}{Z_{02}}$$

$$I_2 = \frac{(239.6 \times 0.25)}{1.7}$$

$$= \underline{\underline{117.45A}}$$