

17/ENG04/071

BLECT/ELECT

3001

QUESTION 2:

$$V = 415V$$

$$V_L = 415$$

$$\text{and } V_L = \sqrt{3} V_P$$

$$P.F. = 0.7$$

$$V_P = \frac{V_L}{\sqrt{3}}$$

$$\text{Efficiency} = 85\%$$

$$f = 50 \text{ Hz}$$

$$V_P = \frac{415}{\sqrt{3}} = 239.6$$

$$P = 74.6$$

$$\text{Actual P.F.} = \cos \theta = 0.7$$

$$\theta = \cos^{-1} 0.7 = 45.57^\circ$$

$$(1) \text{ Unity} = 1$$

$$C = \frac{\text{KVAR}}{2\pi f V^2}$$

$$\rightarrow \text{KVAR} = P \times (\tan \text{ actual power factor} - \tan \text{ target power factor})$$

$$\text{Actual power factor} = \cos \theta = 0.7$$

$$\theta = \cos^{-1} 0.7$$

$$= 45.57^\circ$$

$$\tan (45.57^\circ) = 1.0201$$

$$\text{Target power factor} = \cos \theta = 1$$

$$\theta = \cos^{-1} 1 = 0$$

$$\tan 0 = 0$$

$$\text{KVAR} = 74.6 \times (1.0201 - 0)$$

$$= 76.0995 \approx 76.10$$

$$C = \frac{76.10}{2\pi \times 50 \times 415^2}$$

$$= 0.0000014 \approx 1.4 \times 10^{-6} \text{ C/F}$$

$$= 0.00000422 \approx 42.2 \times 10^{-6} \text{ C/F}$$

17/ENG041071

(i) 0.9 lagging

Actual power factor = 0.201

Target power factor =  $\cos \theta$

$$\theta = \cos^{-1}(0.9)$$

$$= 26.84^\circ$$

$$\tan \theta = -0.48$$

$$kVAR = 74.6 \times (1 - 0.201 - (-0.48))$$

$$= 111.95 \approx 112$$

$$C = \frac{kVAR}{2\pi f V}$$

$$= \frac{112}{2\pi \times 50 \times 239.6}$$

$$= 0.00086$$

$$\approx 8.6 \times 10^{-4} \text{ F}$$

$$2\pi \times 50 \times 239.6^2$$

$$C = \frac{kVAR}{2\pi f V^2}$$

$$= \frac{112}{2\pi \times 50 \times 239.6^2}$$

$$= 0.0000062$$

$$\approx 6.2 \times 10^{-6} \text{ F}$$

$$\approx 6.2 \times 10^{-6} \text{ F}$$

17/06/2021

ELECT

300L

QUESTION 2

No. of poles = 6


Frequency = 50 Hz

Voltage ratio = 5/6

$\sqrt{V_{in}} = 4.5$

$$Z_s = 0.25 + j0.75$$

$$Z_p = 1.173 + j0.52j$$

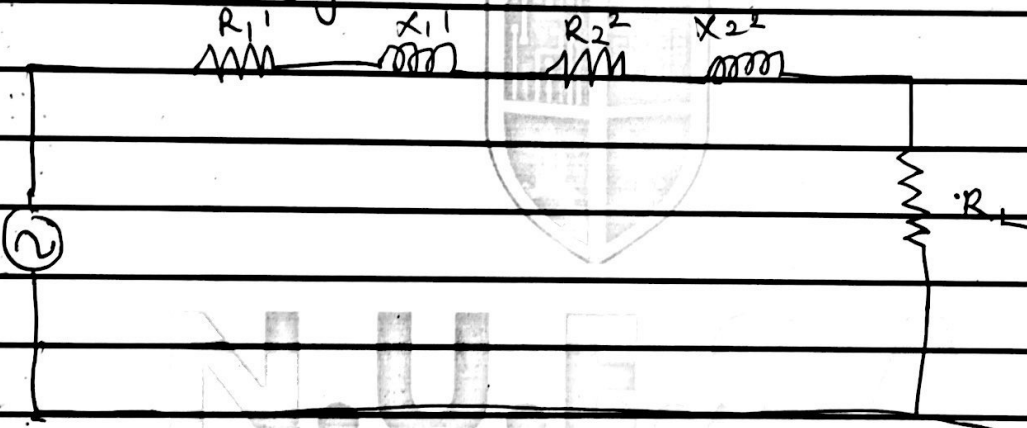

Given that

$$R_2 = 1.173$$

$$X_2 = 0.52j$$

$$R_1 = k^2 \cdot R_2$$

$$= (1.2)^2 \times 0.25 = 0.36$$

$$X_1 = k^2 \times X_2$$

$$= (1.2)^2 \times 0.75$$

$$= 1.08$$

For a series connection

$$Z_T = Z_s + Z_p + R_L$$

$$Z_T = 1.173 + j0.52 + 0.36 + j1.08$$

Referring to refer

$$R_{02} = (R_2 + k^2 R_1)$$

$$= (1.173 + (5/6)^2 \times 0.25)$$

$$R_{02} = 1.347 \Omega$$

$$X_{02} = (X_2 + k^2 X_1)$$

$$= j(0.52 + (5/6)^2 \times 0.75)$$

$$= 1.04j$$

$$Z_{02} = R_{02} + X_{02}$$

$$= 1.347 + j1.041$$

$$Z_{02} = \sqrt{1.347^2 + 1.041^2}$$

$$= 1.7 \Omega$$

12/EN604/071

To find rotor current

$$I_2 = \frac{E_2}{Z_{0L}}$$


Recall that  $E_2 = kV_1$

$$= 234.6 \times 0.83$$

$$= 199.67 \text{ V}$$

$$\therefore I_2 = \frac{199.67}{1.7} = 117.45 \text{ A}$$
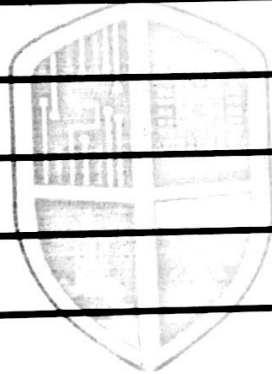
$$\therefore I_2 = \frac{199.67}{1.7} = 117.45 \text{ A}$$



N.U.A.

ABUAD ENGINEERING

17/ENG021071


ELECT/ELECT

3002

QUESTION 3

On AC supply  $F = 50 \text{ Hz}$ ,  $\frac{1}{4} \text{ hp}$ ,  $N_r = 2000 \text{ rpm}$ ,  $V = 220 \text{ V}$   
sw

On DC supply

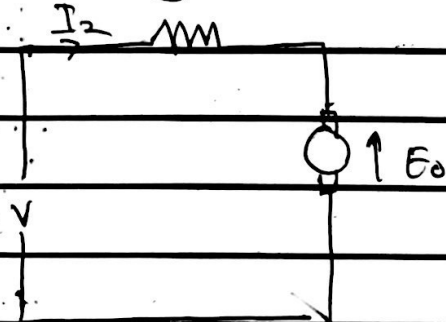

$$V - E_b = I_2 R$$

$$V - (I_L \times R) = E_b$$

$$E_b = 220 - (0.7 \times 15)$$
$$= 209.5 \text{ V}$$

Speed on DC

$$N_{dc} = 2000 \text{ rpm}$$

On AC supply

$$\text{Voltage} = 220 \text{ V}$$

$$\text{Current drawn } I_L = 0.7 \text{ A}$$

$$\text{Resistance drop} = I_L \times R = 0.7 \times 15 = 10.5 \text{ V}$$

$$\text{Reactance voltage drop} = I_L \times X_L = 0.7 \times 2\pi fL$$

$$\text{where } X_L = 2\pi fL$$

$$= 0.7 \times 2\pi \times 50 \times 0.25$$

$$= 54.98 \text{ V}$$

$$E_{bac} = \sqrt{V^2 - (X_L)^2 - IR}$$

$$= \sqrt{(220)^2 - (54.98)^2 - 10.5V}$$

$$= 202.52V$$

(i) Recou speed

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}$$

$$\frac{S_0 E_{bac}}{E_{bdc}} = \frac{N_{ac}}{N_{dc}}$$

~~Assuming~~  $N_{ac}$

$$N_{ac} = 2000 \times \frac{202.52V}{220V}$$

$$209.5V$$

$$N_{ac} = 1933.37 \text{ rpm}$$

(ii) power factor  $\cos \phi = \frac{E_{bac} + IR}{V}$

$$= \frac{202.52 + 10}{220}$$

$$= 0.968$$

$$= 0.968 \text{ W}$$

(iii) Torque developed  $T_w = E_{bac} \times I$

$$T_{ac} = \frac{E_{bac} \times I}{\omega}$$

$$\omega = 2\pi n$$

$$T_{ac} = \frac{E_{bac} \times I_L}{2\pi \times \frac{N_{ac}}{60}}$$

$$= \frac{202.52 \times 0.7 \times 60}{2\pi \times 1933.37}$$

$$= 0.700 \text{ N/m}$$

$$= 0.700 \text{ N/m}$$

$$= 0.700 \text{ N/m}$$

(iv) Universal meter