

17EN041057

ELECTRICAL ELECTRONICS ENGINEERING

300 LEVEL

Question (1)

$$V = 415 \text{ V}$$

4 wire supply - star connection.

$$\text{frequency} = 50$$



$$\text{Power factor} = 0.7$$

$$\eta = 85\%$$

$$P = 74.6 \text{ kW}$$


Capacitance per phase.

Diagrammatic Representation;

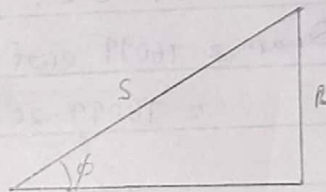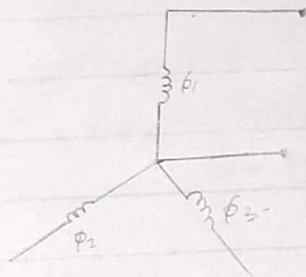

at power factor of 0.7.

Diagram.

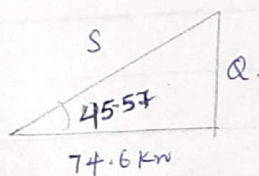

$$\cos \phi = 0.7$$

$$\phi = \cos^{-1}(0.7)$$

$$\text{Hence } \phi = 45.57$$

i. Where; $Q_1 = P \tan \phi_1$

$$Q_1 = 74.6 \times 10^3 (\tan 45.57)$$

$$Q_1 = 76099.2625$$

Recall; when rise in power factor;

$$\phi_1 < \phi_2, P_1 = P_2, Q_1 < Q_2, S_1 < S_2$$

~~5~~

1


17IENG041057

ELECTRICAL ELECTRONICS ENGINEERING

300 LEVEL

∴ at unity Power factor.

Diagram;

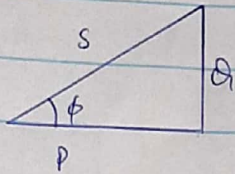

$$\cos \phi = 1$$

$$\phi = \cos^{-1} 1$$

$$\phi = 0$$

$$\phi = 0$$

$$\therefore Q_2 = P \tan \phi$$

$$\therefore Q_2 = 74.6 \text{ k} * \tan 0 = 74.6 \text{ k} * \tan(0)$$

$$Q_2 = 0$$

∴ Recall ; $Q_{\text{cap}} = Q_1 - Q_2$.

$$Q_{\text{cap}} = 76099.2625 - 0$$

$$= 76099.26$$

∴ Capacitance per phase $\Rightarrow \frac{Q_{\text{cap}}}{\omega * V_{\text{rms}}^2}$

\Rightarrow at $F = 50 \text{ Hz}$. Standard frequency Nigeria.

$$\therefore \frac{76099.26}{2\pi * 50 * 415^2}$$


$$= 0.001406$$

$$C = 0.001406$$

$$C = 1.41 \mu\text{F}$$

∴ at at Lagging PF (0.9).

Diagrammatic Representation.

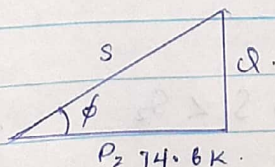


2

171ENG041057

ELECTRICAL ELECTRONICS

300 LEVEL

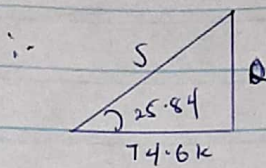

$$\cos \phi = 0.9$$

$$\phi = 25.84$$

\therefore where; $Q_1 = P \tan \phi$

$$Q_2 = 74.6k * \tan(25.84)$$

$$Q_2 = 36127.322$$

Recall Rise in power factor to 0.9

where $Q_1 = 76099.26$

$\therefore Q_2 = 36127.322$

$\therefore Q_{cap} = -Q_1 + (-Q_2)$

$$Q_{cap} = -76099.26 - 36127$$

$$= -112226.58$$

\therefore Capacitive Eff $\Rightarrow \frac{Q_{cap}}{2\pi * V_{rms}^2}$

$$= \frac{-112226.58}{2\pi * 415^2}$$

$$= 0.137 F$$

Current Value;

Current value =


$$P = V * I * \cos \phi$$

$$I = \frac{24.6 \times 10^3}{239.5 * 0.9}$$

$$I = 146.73 A$$

Type of Motor = 3 ϕ Induction motor Drive.

Q1.

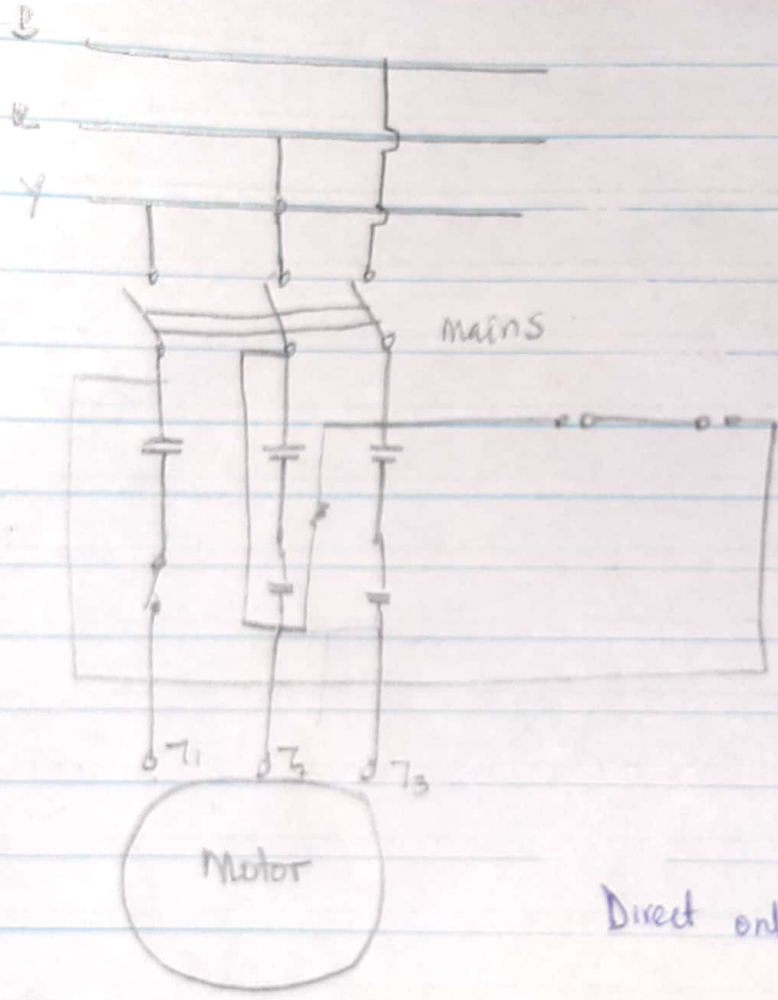

Direct online starter Diagram.

4 ~~4~~

17ENG041057
ELECTRICAL ELECTRONICS
300 LEVEL

Question (2)

Parameters:

$$V_{line} = 415 \text{ V}_{L-2}$$

$$\text{No of poles} = 6$$

$$\text{frequency} = 50\text{Hz}$$

Star-connected


$$\text{Voltage ratio} = 6/5 = 1.2$$

$$Z_s = 0.25 + j0.75$$

$$Z_R = 1.173 + j0.52$$

Diagrammatic Representation.

Equivalent Circuit Version 2.

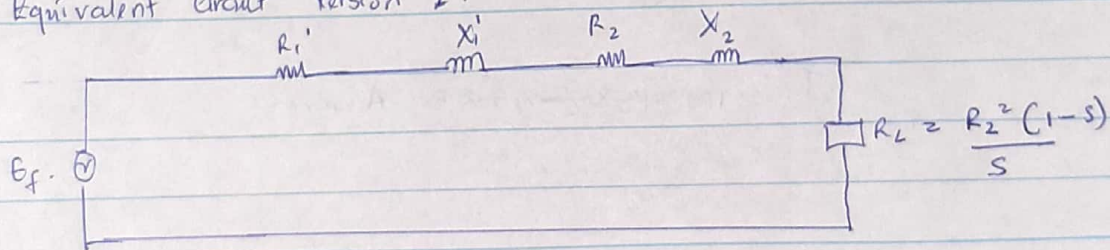

Given that

$$R_2 = 1.173 \quad \cancel{1.17302}$$

$$R_L = 0$$

$$X_2 = j0.52$$

$$R_1' = k^2 \cdot R_1$$

$$= (1.2)^2 \cdot 0.25 = 0.38$$

$$X_1' = k^2 \cdot X_1$$

$$= (1.2)^2 \cdot (0.75)$$

$$\Rightarrow 1.08$$

i. Series connection;

$$\therefore Z_T = Z_s + Z_T + R_L$$

$$Z_T = 1.173 + j0.52 + 0.38 + j1.08$$

$$= 1.553 + j1.6$$

$$= 2.2297 \angle 45.85^\circ$$

~~5~~

5

17IEM404/057
ELECTRICAL ELECTRONICS
300 LEVEL

∴ Finders (Secondary Current) I_2

Given that, $V_{line} = 415$

$$\Rightarrow \frac{415}{\sqrt{3}}$$

$$\Rightarrow 239.60 \text{ V}$$

Note, Star = ~~$\frac{V_{line}}{\sqrt{3}}$~~ ~~$\frac{V_{line}}{\sqrt{3}}$~~

$$V_{line} = \sqrt{3} \text{ Voltage}$$

$$\text{Voltage} = \frac{V_{line}}{\sqrt{3}}$$

∴ Secondary Current $I_2 = I_1$

$$\therefore I_2 = \frac{V_{max}}{Z_T}$$

$$I_2 = \frac{239.60}{2.2297} < 45.85$$

$$I_2 = 107.458 < 45.85 \text{ Amperes}$$

6

17IENG041057
 ELECTRICAL ELECTRONICS ENGINEERING
 300 LEVEL

Q_3

Given preamble;

freq = 50Hz.

NO of poles = 6.

$N = 2000 \text{ rpm}$.


Current = 0.7A.

$V_{DC} = 220$.

Resistance = 15Ω.

Inductance = 0.25.

Diagram)

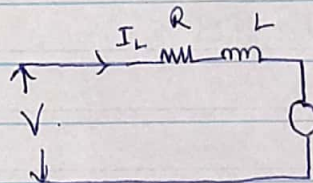

DC.


Using the formula;

$V - E_b = I_L R$.

$220 - E_b = 0.7 * 15Ω$.

$220 - E_b = 10.5$

$E_b = 209.5 \text{ V}$.

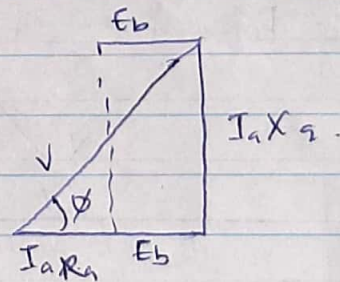

∴ at AC

i. using the formula

$\sqrt{V^2 - I_a^2 X_s^2} - I_a R_a = E_b$.

$\therefore E_b = \sqrt{(220)^2 - (0.7)^2 * (X_s)^2} - (0.7)(15) = E_b$.

Where $X_s = 2\pi fL$

$X_s = 2 * \pi * 50 * 0.25$
 $= 78.539$

Put into equation

$\therefore E_b = 201.45$

7

17ENG041057

ELECTRICAL ELECTRONICS ENGINEERING

300 LEVEL

Where,


$$\frac{E_{bAC}}{E_{bDC}} = \frac{N_{AC}}{N_{DC}}$$

$$\frac{201.45}{209.5} = \frac{N_{AC}}{2000}$$

$$N_{AC} = 1923.15$$

∴ Speed of motor = 1923.15

(b) Power factor of motor

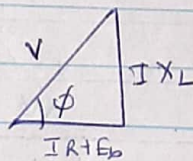

∴ at $V = 220$

$$IX_L = 54.977$$

$$\sin \phi = \frac{54.977}{220}$$

$$\phi = \sin^{-1} 0.25$$

$$\phi = 14.47^\circ$$

$$\begin{aligned} \therefore \text{Power factor} &= \cos \phi \\ &= \cos (14.47) \\ &= 0.968 \end{aligned}$$



17IENG041057

ELECTRICAL ELECTRONICS ENGINEERING

300 LEVEL

ii) Torque developed

Using the formula;

$$T_{AC} = \frac{E_{bAC} \times I_L}{2\pi \times \frac{N_{AC}}{60}}$$

$$T_{AC} = \frac{201.45 \times 0.7}{2 \times \pi \times \frac{1923.15}{60}}$$

$$T_{AC} = 0.70 \text{ Nm.}$$

④ A Universal motor could be used for the Application because it can operate on both either AC or DC.

9