

IMMAN USMAN SUNDAY ELECT / ELET
17 / ENG 04 / 067 300 level

$V = 415$, 3- ϕ , 4-wire, $f = 50$ Hz, $P = 74.6$
 $P.f = 0.7$, η efficiency = 85%

1.) Unity = 1

$$C = \frac{1 \text{hVAR}}{2\pi f V^2}$$

$\rightarrow 1 \text{hVAR} = P \times C (\tan \text{ actual } P.f \rightarrow \tan \text{ target } P.f)$

$$\text{actual } P.f \Rightarrow \cos \theta = 0.7$$

$$\theta = \cos^{-1} 0.7$$

$$= 45.57$$

$$\tan (45.57) = 1.0201$$

$$\text{target } P.f = \cos \theta = 1$$

$$\therefore \theta = \cos^{-1} 1 = 0$$

$$\tan 0 = 0$$

$$1 \text{hVAR} = 74.6 \times C (1.0201 - 0)$$

$$\approx 76.10$$

$$C = \frac{76.10}{2\pi \times 50 \times 415^3}$$

$$= 0.0000014$$

$$= 1.4 \times 10^{-6} \text{ F}$$

$$\approx 1.4 \mu\text{F}$$

IMMAN USMAN SumanDA

17/ENG 04/067

Elect/Elect 20014

1) 0.9 logging
actual p.f = 1.0201

$$\text{target p.f} = \cos \theta = -0.9$$

$$\theta = \cos^{-1}(0.9) = 154.16$$

$$\tan \theta = -0.48$$

$$I_{\text{VAR}} = 74.6 \times (1.0201 - (-0.48))$$

$$= 111.96$$

$$\approx 112$$

$$C = \frac{I_{\text{VAR}}}{2\pi fV}$$

$$= 112 /$$

$$2\pi \times 50 \times 415^2$$

$$= 0.00086$$

$$= 8.6 \times 10^{-4} \text{ C}$$

3001d

IMMAN USMAN
Sumda electric
17/EN6 04/067¹³

QUESTION 2

$$V = 415 \text{ V}$$


$$\text{no of poles} = 6$$

$$f = 50 \text{ Hz}$$

$$k = \frac{5}{6} = 0.83$$

$$R = Z_1 = 0.25 + j0.75$$

$$Z_2 = 1.173 + j0.52$$

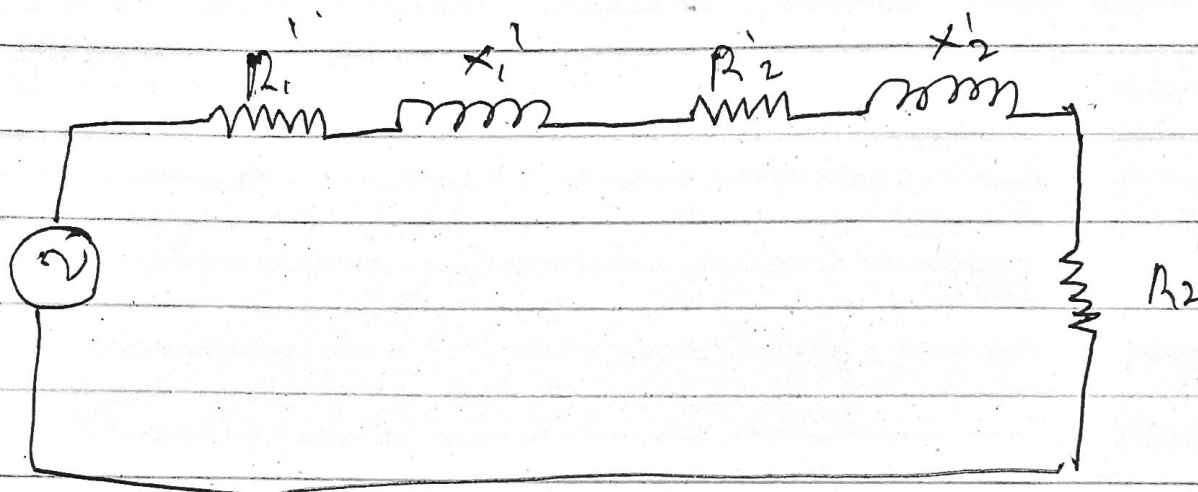

supply voltage per phase $V = \frac{415}{\sqrt{3}}$

$$= 239.60 \text{ V}$$

Referring to rotor

$$R_{02} = (R_2 + k^2 R_1)$$

$$= 1.173 + \left(\frac{5}{6}\right)^2 \times 0.25$$

$$R_{02} = 1.347 \text{ } \Omega$$

$$X_{02} = (X_2 + k^2 X_1)$$

$$= j(0.52 + \left(\frac{5}{6}\right)^2 \times 0.75)$$

$$= 1.041$$

IMMAN USMAN SUMDA
ELECT/ELECT 17ENG04/06A 3004

$$Z_{02} = R_{02} + X_{02}^2$$
$$= 1.547 + j1.041$$

$$Z_0 = \sqrt{(1.547)^2 + 1.041}$$

$$Z_0 = 1.7 - 2$$

To find the motor current

$$I_2 = \frac{E_2}{Z_{02}}$$

$$\text{Recall } E_2 = 1kV$$
$$= 239.6 \times 0.83$$
$$= 199.67V$$

$$\therefore I_2 = \frac{199.67}{1.7}$$

$$\approx 117.45A$$

300W


Imran Usman
Sumda

QUESTION 3 17/ENGR04/067 ELECT/ELET

$f = 50 \text{ Hz}$, $\frac{1}{4} \text{ hp}$, $N = 2000 \text{ rpm}$, $V = 220 \text{ V}$
 $15 \text{ } \Omega$ & 0.25 H

On AC Supply

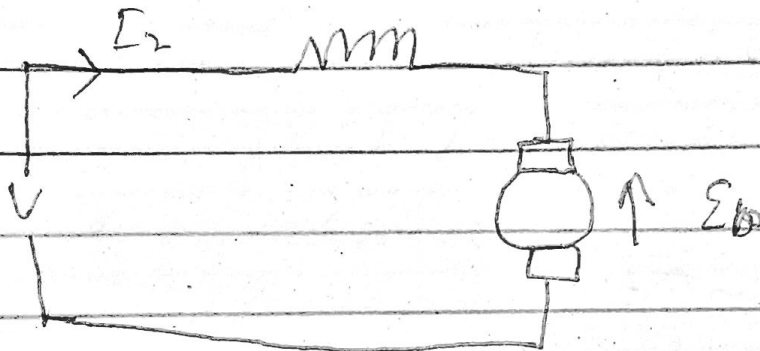Supply Voltage = 220 V
Current drawn $I = 0.7 \text{ A}$



$$V - E_b = I * R$$

$$V - (I * R) = E_b$$

$$E_b = 220 - (0.7 * 15)$$

$$= 209.5 \text{ V}$$

Speed on AC,

$$N_{ac} = 2000 \text{ rpm}$$

IMPAN USMAN SUMDA 17/02/2017
E/ET/ET

ON AC Supply

3001

Supply voltage = 220V

Current drawn, $I_2 = 0.7A$


the active drop = $I_2 \times R = 0.7 \times 15 = 10.5V$

the reactive voltage drop = $I_L \times X_L$
 $= 0.7 \times 2\pi fL$

where $X_L = \omega L = 2\pi fL$

$$= 0.7 \times 2\pi \times 50 \times 0.25$$

$$= 54.98V$$

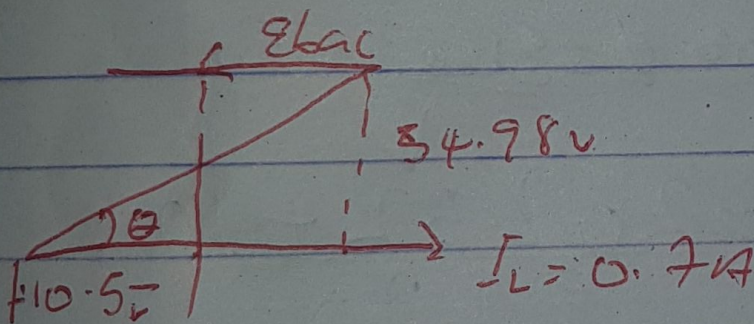

$$E_{bac} = \sqrt{V^2 [X]^2 - IR}$$
$$= \sqrt{(220)^2 - (54.98)^2} - 10.5V$$
$$= 202.52V$$

Imvan usman Saadq
Elect / elect 1712W6041067

Recall speed constant equation (3000)

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} \quad \text{so} \quad \frac{E_{bac}}{E_{bdc}} = \frac{N_{ac}}{N_{dc}}$$

making N_{ac} subject of the formula

$$N_{ac} = N_{dc} \times \frac{E_{bac}}{E_{bdc}}$$

$$= 2000 \times \frac{202.52V}{209.5V}$$

$$\therefore N_{ac} = 1933.37 \text{ rpm}$$

iv) power factor, $\cos \phi = \frac{E_{bac} + I_m}{V}$

$$= \frac{202.52 + 10}{220}$$

$$= 0.968 \text{ Lagg}$$

iii) Torque developed $T_w = E_{bac} \times I$

$$T_{ac} = \frac{E_{bac} \times I}{\omega}$$

\Rightarrow speed in rad/s

$\omega = 2\pi n$ where n is speed in rads

$$T_{ac} = \frac{E_{bac} \times I}{2\pi \times N_{ac}}$$

60

IMMAN USMAN SUNDI
17/EN0404/067 ELECT/ELECT 300W

$$= 207.52 \times 0.7 \times 60$$

$$2\pi \times 1933.37$$

$$= 0.700 \text{ Nm}$$

QUESTION

IV