

* Matrix No: 17/Eng04/039

Depts: Elect/Elect

Level: 300L

Question 1

① $V = 415 \text{ V}$, 3- ϕ , 4 wire, $f = 50 \text{ Hz}$, $P = 74.6$
 $P.f = 0.7$, % off = 85%

(i) Unity = 1.

$$C = \frac{1 \text{ kVAR}}{2\pi f V^2}$$

$\rightarrow 1 \text{ kVAR} = P \times (\text{tan actual p.f} - \text{tan target p.f})$

actual p.f $\Rightarrow \cos \theta = 0.7$

$$\theta = \cos^{-1} 0.7$$

$$= 45.57$$

$$\tan(45.57) = 1.0201$$

target p.f $\Rightarrow \cos \theta = 1$

$$= \cos^{-1} 1 = 0$$

$$\tan 0 = 0$$

$$1 \text{ kVAR} = 74.6 \times (1.0201 - 0)$$

$$= 76.0995$$

$$\approx 76.10$$

$$C = \frac{76.10}{2 \times 77 \times 50 \times 415^2}$$

$$= 0.0000014$$

$$\approx 1.4 \times 10^{-6} \text{ F}$$

Matr no: 171 Eng 041039

Dept: Elect/Elect

Level: 300

2

Question 1

i) 0.9 lagging

$$\text{actual p.f} = 1.0201$$

$$\text{target p.f} = \cos \theta = -0.9$$

$$\theta = \cos^{-1}(-0.9)$$

$$= 154.16$$

$$\tan \theta = -0.48$$

$$\text{kVAR} = 74.6 \times (1.0201 - (-0.48))$$

$$= 111.90$$

$$\Rightarrow 112$$

$$C = \frac{\text{kVAR}}{2\pi fV}$$

$$= 112$$

$$\frac{112}{2\pi \times 50 \times 415^2} = 0.00086$$

$$\Rightarrow 8.6 \times 10^{-4} \text{ Farad}$$

Question 2

$$V_0 = 415V$$

$$V_0 \text{ of pole} = 6$$

$$f = 50 \text{ Hz}$$

$$k = 5/6 = 0.83$$

$$R \times Z_1 = 0.25 + j0.75$$


Matric no: 1716ng041029

Dept: Elect/Electr

Level: 300L

Question 2
Quest

$$Z_2 = 1 - j1.73 + j0.52$$

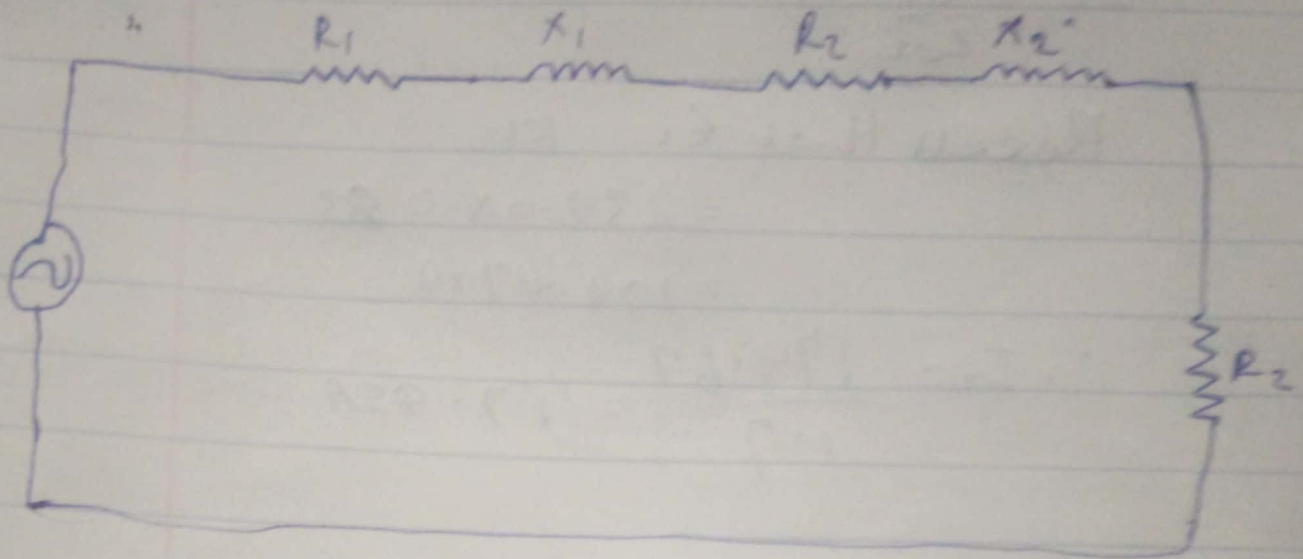

Supply Voltage per phase $V = \frac{415}{\sqrt{3}} = 239.60V$

Referring to rotor

$$R_{02} = (R_2 + k^2 R_1) \\ = (1 - j1.73 + (5/6)^2 \times 0.25)$$

$$R_{02} = 1.347 \Omega$$

$$X_{02} = (X_2 + k^2 X_1) \\ = j(0.52 + (5/6)^2 \times 0.75) \\ = 1.041$$

$$Z_{02} = R_{02} + jX_{02} \\ = 1.347 + j1.041$$

$$Z_{02} = \sqrt{1.347^2 + 1.041^2} = \underline{\underline{1.7 \Omega}}$$

Matric No: 17/Eng 04/039

Dept: Elect/Elect

Level: 300

To find the rotor current

$$I_2 = \frac{E_2}{Z_{02}}$$

Recall that $E_2 = kv_2$

$$= 239.6 \times 0.83$$

$$= 199.67 \text{ V}$$

$$\therefore I_2 = \frac{199.67}{1.7} = 117.45 \text{ A}$$


Question 3

$f = 50 \text{ Hz}$, $1/4 \text{ hp}$, $N_2 = 2000 \text{ rpm}$, $V = 220$, 45 m
 ~~$R = 1.5 \Omega$~~ and 0.25 H

on DC supply

Supply Voltage = 220 V

Current drawn, $I = 0.7 \text{ A}$

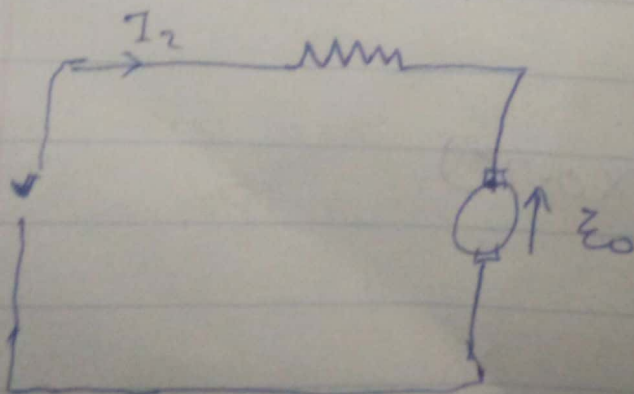

$$V - E_2 = I_2 R$$

Matrix No: 17/Eng041039

Dept: Elect/ Elect

Level: 3000

Question 3

$$V - E_b = I_2 \times R$$

$$V - [I_2 \times R] = E_b$$

$$E_b = 220 - [0.7 \times 15]$$

$$= 209.5V$$

Speed on Dc

$$N_{0b} = 2000 \text{ rpm}$$

On AC supply

$$\text{Supply Voltage} = 220V$$

$$\text{Current drawn, } I_2 = 0.7A$$

$$\text{Resistance drop} = I_2 \times R = 0.7 \times 15$$

$$= 10.5V$$


$$\text{Reactance Voltage drop} = I_2 \times X_L$$

$$= 0.7 \times 2\pi fL$$

$$\text{Where } X_L = j\omega L = 2\pi fL$$

$$= 0.7 \times 2\pi \times 50 \times 0.25$$

$$= 54.98V$$

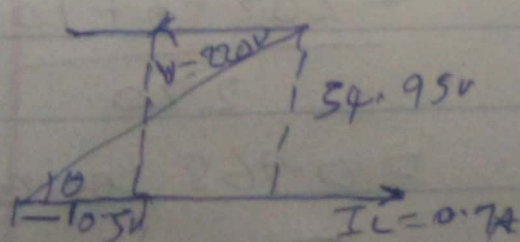

De Metric No: 17/Eng04/039
Dept: Electr/Elect
Level: 300

6

$$E_{bac} = \sqrt{V^2 - (I R)^2} - I R$$
$$= \sqrt{(220)^2 - (54.98)^2} - 10.5V$$
$$= 202.52V$$

Recall speed = constant equation

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}$$

$$\text{SO } \frac{E_{bac}}{E_{bdc}} = \frac{N_{ac}}{N_{dc}}$$

Making N_{ac} subject of the formulae

$$N_{ac} = N_{dc} \times \frac{E_{bac}}{E_{bdc}}$$

$$= 2000 \times \frac{202.52V}{209.5V}$$

$$1933.37 \text{ rpm}$$

$$\text{power factor, } \cos \theta = \frac{E_{bac} + I R}{V}$$

$$= \frac{202.52 + 10}{220}$$

$$= 0.968 \text{ leading}$$

$$\text{Torque developed } T_{wz} = E_{bac} \times I$$

17/engap/039

7

Elect/Electr
300

Question 3

$$T_{ac} = \frac{E_{bac} \times I}{\omega}$$

$\omega = 2\pi n$, where n is speed i

$$T_{ac} = \frac{E_{bac} \times I_c}{2\pi \times \frac{Nk_c}{60}}$$

$$= \frac{202.52 \times 0.7 \times 60}{2\pi \times 1938.37}$$

$$= 0.700 \text{ Nm}$$