

Matric No: 17/ENG04/069

Department: Electrical Electronics Engineering
300 level


A 25hp, 415v (line-line), 6 pole

→ Solu.

- 25hp
- 415v (line-line)
- 6 pole.
- $F = 50\text{Hz}$
- 3 phase.
- Stator/rotor phase voltage ratio of 6/5
- Stator impedance $(0.25 + j0.75)$
- Rotor $(1.173 + j0.52)$

• approximate circuit version 2

• Slip = 1 Find rotor current I_2 .

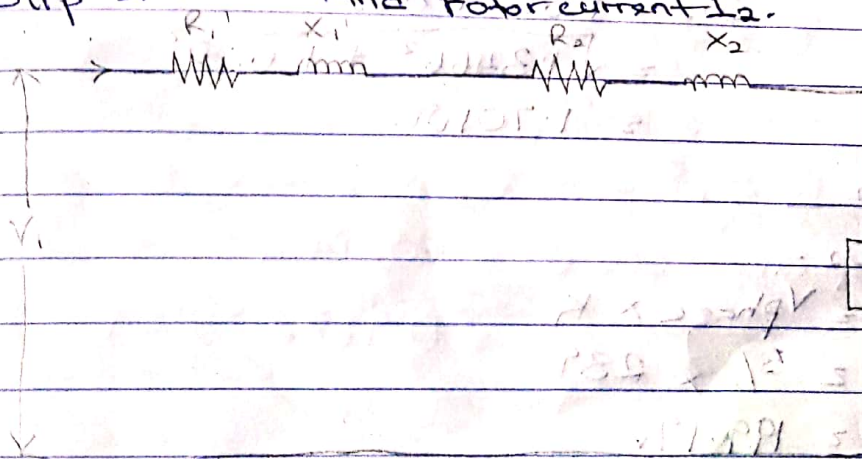

$$R_2 = \frac{R_2 [1-s]}{K^2 S}$$

Changing supply voltage to per phase

$$V_{\text{phase}} = \frac{415\text{v}}{\sqrt{3}}$$

$$= 239\text{v}$$

Recall $K = \frac{6}{5}$ $K = \frac{5}{6}$

- Changing horsepower to kilowatts

$$1\text{hp} = 0.7457$$

Name No: 17ENGE041069
 Department: Electrical Electronics Engineering
 300 level.

25hp = 0.7457 × 25

≈ 18.6425 kW.

R_{02} (referring to the motor side) = $[R_2 + K^2 R_1]$

≈ $[1.173 + (5/10)^2 × 0.25]$

≈ $[1.173 + 0.1736]$

≈ 1.3466 Ω.

X_{02} (referring to the motor side) = $[X_2 + K^2 X_1]$

≈ $[0.52 + (5/10)^2 × 0.75]$

≈ $[0.52 + 0.62]$

≈ 1.04 Ω

Total impedance $Z_{02} = R_{02} + jX_{02}$

$Z_{02} = (1.3466 + j1.04) Ω$

$Z_{02} = R_{02}^2 + X_{02}^2$

≈ $\sqrt{1.3466^2 + 1.040^2}$

≈ 1.701 Ω.

Recall: $I_a = \frac{E_a}{Z_{02}}$

Z_{02}

$E_a = V_{phase} × K$

≈ $5/10 × 239$

≈ 119.5 V

$I_a = \frac{119.5}{1.701}$

≈ 70.25 A

≈ 117.08 A

≈ 117.08 A

Matric No: 171EN041069
Department: Electrical Electronics Engineering

300 level
Question 3

$f = 50\text{Hz}$
 $1/4\text{hp} \rightarrow 0.7457 \times 0.25 = 0.186\text{KW}$

$N \rightarrow 2600\text{rpm}$

220V DC source $\rightarrow I_{sc} = 0.7A$

$R = 15\Omega$

$L = 0.25H$

Find ... when connected to 220V, 50Hz AC and loaded to take 0.7A current.

Solu.

Speed of the motor $= E_{bac} = N_{ac}$
 $E_{bd} = N_{dc}$

Calculate back emf generated by DC

$$E_b = V - IR$$
$$E_b = 220 - (0.7 \times 15)$$
$$= 209.5\text{V}$$

Calculate back emf generated by AC.

$$E_b = \sqrt{V^2 - (I \times L)^2} - IR$$
$$X_L = 2\pi fL$$
$$= 2 \times \pi \times 50 \times 0.25$$
$$= 78.539$$

$$E_b = \sqrt{220^2 - (0.7 \times 78.539)^2} - 12$$
$$= 213.0199 - 10.5$$
$$= 202.51\text{V}$$

Marka Nac 50F

$N_{ac} = N_{dc} \times E_{bac}$

E_{bd}

Matr No: 1711504041061
 Department: Electrical Electronics Engineering
 300 level


$z = \frac{1000 \times 1000}{200 \times 1000}$
 200×5

$N_s = 1911.82 \text{ rpm} \cdot 1923.06 \text{ rpm}$

ii) Power Factor:

Total Resistance: $15 + j0.05$

Power Factor = $V \cos \theta$

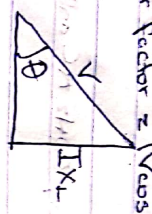

$\sin \theta = \frac{IX}{V} = \frac{0.05}{220}$

$\sin \theta = 0.2272$

$\theta = \sin^{-1} 0.2272$

$\theta = 14.47^\circ$

Power factor = $\cos \theta = \cos 14.47^\circ$

≈ 0.9682

iii) Torque developed

$T = \frac{KEa^2 R_2}{R_2^2 + X_2^2}$

$K = \frac{3}{2\pi N_s}$

$T = \frac{0.0148 \times (200)^2 \times 15}{15^2 + 0.25^2}$

Since $N_s = 1923.06 \text{ rpm}$

$N_s = \frac{1923.06}{60}$

$\approx 40.45 \text{ Nm}$

$K = \frac{3}{2\pi \times 1923.06}$

≈ 0.0148

Admin. Machine No: 171 ENR 04/2017

Department: Electrical & Electronics Engineering

300 level.

ii) A universal Motor.

LC

1000000

1000000

2000000

2000000

2000000

2000000

2000000

2000000

2000000

2000000

2000000

2000000

2000000

2000000

2000000

2000000

Matric No: 1711ENG041069
Department: Electrical Electronics Engineering
300 level

Question 1.

$F = 50\text{Hz}$

415 V

3-phase.

4 wires, 50Hz.

$P = 74.6\text{KW}$

$P.F = 0.7$

$E = 0.85$

Original P.F = 0.7

Final P.F = 1.

$\theta_1 = \cos^{-1}(0.7) = 45.57^\circ ; \tan^{-1}(45.57) = 1.02$

$\theta_2 = \cos^{-1}(1) = 0 ; \tan^{-1}(0) = 0.$

Required capacitor KVAR = $P[\tan\theta_1 - \tan\theta_2]$

$= 74.6[1.02 - 0]$

$= 76.092\text{KVAR}.$

in each phase $= \frac{76.092}{3} = 25.364\text{KVAR per phase}$

Original P.F = 0.7

Final P.F = 0.9

$\theta_1 = \cos^{-1}(0.7) = 45.57^\circ ; \tan^{-1}(45.57) = 1.02$

$\theta_2 = \cos^{-1}(0.9) = 25.84^\circ ; \tan^{-1}(25.84) = 0.484$

Required capacitor KVAR = $P[\tan\theta_1 - \tan\theta_2]$

$= 74.6[1.02 - 0.484]$

$= 39.9856\text{KVAR}.$

in each phase $= \frac{39.9856}{3} = 13.328\text{KVAR per phase}$

Q

- The drive motor type is an induction motor.