

18/ENC04/081

800 LVL

3) $V = 415V$

Supply voltage per phase $\frac{415}{\sqrt{3}} = 239.6$

$f = 50Hz$

$P = 74.6 \text{ kW}$

Power factor = 0.7,

$\eta_{\text{eff}} = 85\%$

i) unity is 1

where $C = \frac{\text{kVAR}}{2\pi f V^2}$

$\text{kVAR} = P \times (\tan P.f_1 - \tan P.f_2) = (P \times C \Delta \tan P.f)$

lagging $P.f_1 = \cos \theta = 0.7$

$\theta = \cos^{-1} 0.7$

$= 45.5729$

$\tan(45.5729)$

$= 1.020204$

$P.f_2 = \cos \theta = 1$

$\theta = \cos^{-1}(1)$

$= 0$

$\tan(0) = 0$

thus $= 74.6 (1.020204 - 0)$

$\text{kVAR} = 76.1072$

Correction

$76.1072 = 42.2 \times 10^{-6} C$

18035305.37

$C = 76.1072$

=

$\frac{76.1072}{544000 \times 1.748}$

$= 1.407 \times 10^{-6}$

$2\pi \times 50 \times (239.6)^2$

~~544000×1.748~~

$C = 1.407 \times 10^{-6} C$

18/ENewy/001
ELECT/ELECT

ii) 0.9 lagging

$$\text{(lagging) } P.F_1 = 1.020204$$

$$P.F_2 = \cos \theta = 0.9$$

$$\theta = \cos^{-1}(0.9)$$

$$= 154.15806$$

$$\approx 154.16$$

$$\tan(154.16) = -0.4843$$

$$\text{KVAR} = 74.6 \times (1.020204 - (-0.4843))$$

$$= 74.6 (1.020204 + 0.4843)$$

$$= 74.6 (1.504504)$$

$$= 112.235$$

$$\approx 112.24$$

$$C' = \text{KVAR} = 112 = \frac{112}{2\pi f V^2} = \frac{112}{2\pi \times 50 \times (230)^2} \Rightarrow 2.07 \times 10^{-6} \text{ F}$$

Correction

$$= 112$$

$$\cos^{-1} 0.9 = 154.15806$$

$$= 6.21004 \times 10^{-6} \text{ F}$$

W) ENCL 1081
ELECT / ELECT

3) $f = 50 \text{ Hz}$

$\frac{1}{4} \text{ HP}$


$N = 2000 \text{ rpm}$

$V = 220 \text{ V}$

* From DC supply

Supply voltage = 220V

$I = 0.7 \text{ A}$

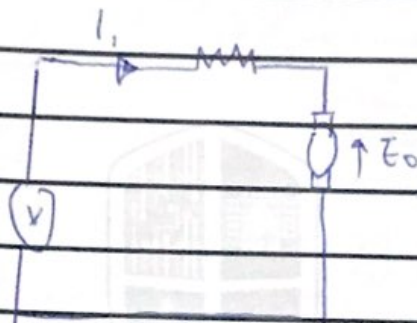

$V = E_b + I_1 R$

$V - (I_1 R) = E_b$

$E_b = 220 - (0.7 \times 15)$

$= 209.5 \text{ V}$

Speed on DC

$N_{50} = 2000 \text{ rpm}$

* From AC supply

$V = 220 \text{ V}$

$I = 0.7 \text{ A}$

$X_L = [2\pi f L] = 2\pi \times 50 \times 0.25$
 $= 54.98 \text{ V}$

R_2 (reactance drop) $= I_1 R = 0.7 \times 15 = 10.5 \text{ V}$


$I_1 \times X_L = \text{reactance voltage } (R_v)$

$\hookrightarrow 0.7 \times 2\pi f L$

$= 0.7 \times 54.98 \text{ V}$

38.486 V

18) Find out lost
ELECTRICITY

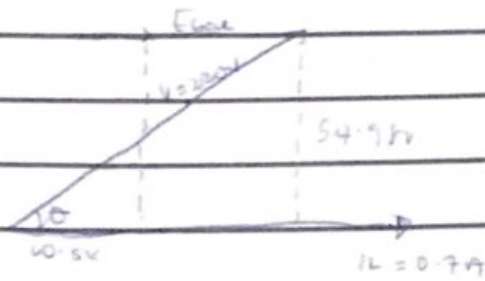

$$E_{bac} = \sqrt{V^2 - (I_L r_a)^2} - I_L r_a$$

$$= \sqrt{220^2 - 54.9^2} - 10.5$$

$$= 202.52 \text{ V}$$

Speed ω $N_2 = E_{b2}$
 $N_1 = E_{b1}$

$$\therefore \frac{E_{bac}}{E_{bdc}} = \frac{N_{ac}}{N_{dc}}$$

$$N_{ac} = 2000 \times \frac{202.52 \text{ V}}{209.5 \text{ V}}$$

$$N_{ac} = 1933.37 \text{ rpm}$$

ii) Power factor $\cos \theta = \frac{E_{bac} + I_L r_a}{V}$ $V = 220$
 $E_{bac} = 202.52$

$$\text{Watt} = \frac{202.52 + 10.5}{220}$$

$$= 0.988 \text{ lagging}$$

iii) Torque produced $T_a = E_{bac} \times I$

$$T_{ac} = \frac{E_{bac} \times I}{\omega}$$

$$\omega \text{ (speed in rad/s)} = 2\pi n$$

$$T_{ac} = \frac{E_{bac} \times I}{2\pi n} = \frac{202.52 \times 0.7 \times 60}{2\pi \times 1933.37} = 0.702 \text{ Nm}$$

iv) The motor type is a universal motor

Let $V_{line-line} = 415V$
ELECT/ELECT

2) $V_{line-line} = 415V$

No of pole = 6


$P = 50W$

$k = \frac{P}{6} = 0.833$

$Z_1 = 0.25 + j0.75$ — Statu

$Z_2 = 1.173 + j0.52$ — rotor

i)

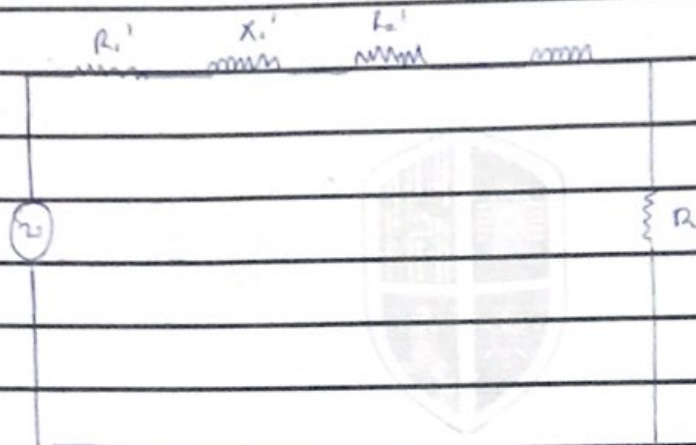

ii) voltage per phase = $V = \frac{415}{\sqrt{3}} = 239.60V$

Rotor

$R_{02} = (R_2 + k^2 R_1)$

$= (1.173 + (0.833)^2 \times 0.25)$

$R_{02} = 1.347 \Omega$

$X_{02} = (X_2 + k^2 X_1)$

$= j(0.52 + (0.833)^2 \times 0.75)$

$= 1.041$

$Z_{02} = R_{02} + X_{02}$

$= 1.347 + j1.041$

$Z_{02} = \sqrt{1.347^2 + 1.041^2}$

$= 1.72 \Omega$

ELECT/ELECT
LET ENERGY LOSS

For rotor current

$$I_2 = \frac{T_2}{Z_{02}}$$


$$Z_{02}$$

Recall that $T_2 = K\omega_r$

$$= 289.6 \times 0.83$$

$$= 199.67 \text{ N}$$
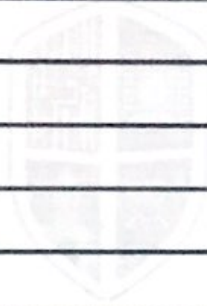
$$\therefore I_2 = \frac{199.67}{1.7} = 117.45 \text{ A}$$



N.U.E.S.A.

BOARD OF ENGINEERING