

Bakare Sharafadeen omogbolahan.

17/Eag04/014

ELECT/ELECT

①

②

② unity = 1

$$C = \frac{KVAR}{2\pi fV^2}$$

$$KVAR = P \times [\tan \text{Caetual P.F}] - (\tan \text{target P.F}]$$

$$\text{Actual Pof} = \cos \theta = 0.7$$

$$\theta = \cos^{-1} 0.7$$

$$\theta = 45.57^\circ$$

$$\tan [45.57] = 1.020111$$

17/Eng02/1014

ELECT

$$1) (b) \text{ KVAR} = P \times [\tan(\text{Power factor}) \times \tan(\text{P. factor})]$$

$$1 = \cos \theta = 1$$

$$\theta = \cos^{-1}$$

$$\theta = 0$$

$$\tan \theta = 0$$

$$\text{KVAR} = 74.6 [1.0201 - 0]$$

$$\text{KVAR} = 76.10$$

$$\therefore C = \frac{76.10}{2 \times \pi \times 50 \times 239.6^2}$$

$$C = 0.00000422$$

$$C = 42.2 \times 10^{-6} \text{ C}$$

For 0.9 laggy = -0.9 negative because its laggy  
target P.F =  $\cos \theta = -0.9$

$$\theta = \cos^{-1}(-0.9)$$

$$\theta = 154.16$$

$$\tan \theta = -0.48$$

$$\text{KVAR} = 74.6 \times [1.0201 - (-0.48)]$$

$$\text{KVAR} = 111.90$$

$$C = \frac{\text{KVAR}}{2 \pi F V^2}$$

$$C = \frac{112}{2 \times \pi \times 50 \times 239.6^2}$$

$$C = 0.0000062$$

$$C = 62 \times 10^{-6} \text{ C}$$

$$C = 62 \times 10^{-6} \text{ C} //$$

17/Eng04/1014

ELECT/ELECT (2)

(1) (2) (3) Given 415V (line-line)

$$N_s : N_r = 6 : 5$$


$$Z_B = (0.25 + j0.75) \Omega$$

$$Z_r = (1.173 + j0.52) \Omega$$

$Z'_s$  = stator impedance refers to rotor side

$$Z'_s = (0.25 + j0.75) \times \left(\frac{5}{6}\right)^2$$

$$Z'_s = (0.1736 + j0.5208) \Omega$$

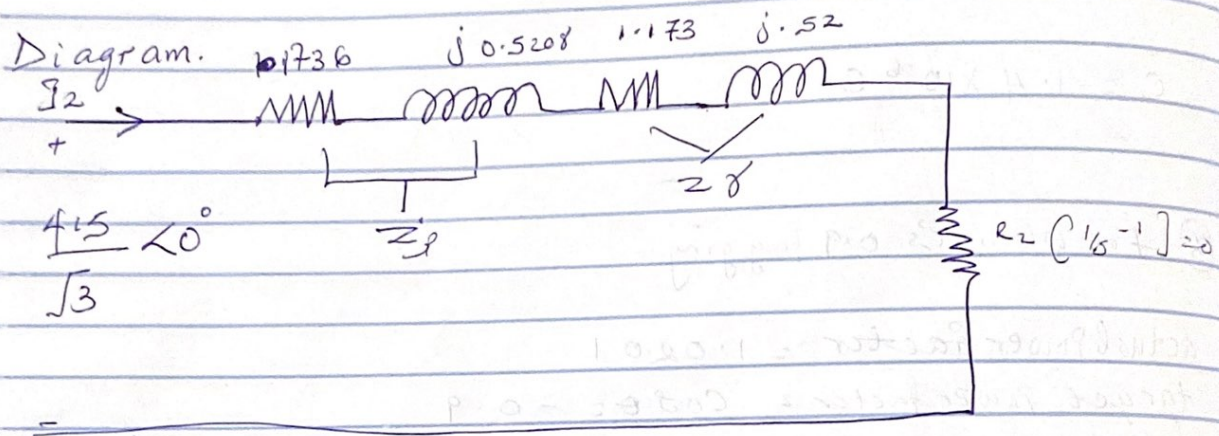

$$\therefore R_2 \left(\frac{1}{s} - 1\right) = 0$$

↳ mechanical load

$$\text{as at } s = 1, R_2 \left(\frac{1}{s} - 1\right) = 0$$

(b) (i) from the approximate circuit of (c)

$$I_2 = \frac{415/\sqrt{3}}{(0.1736 + 1.173) + j(0.5208 + 0.52)}$$

$$I_2 = 140.780 \angle -37.70^\circ \text{ A.}$$

Bakare Sharatadeen omogbolahan  
171Eng041014

ELECT/ELECT

- ③ For the DC supply  
Supply voltage = 220V  
Current draws,  $I = 0.7A$ .

$$V - E_b = I_L * R$$

$$V - (I_L * R) = E_b$$

$$E_b = 220 - (0.7 * 15)$$

$$E_b = \underline{\underline{209.5V}}$$

Speed on DC

$$N_{dc} = 2000 \text{ rpm}$$

For the AC supply.

$$\text{Supply voltage} = 220V$$

$$\text{Current} = I_L = 0.7A$$


$$\text{Reactance drop} = I_L * R = 0.7 * 15 \\ = 10.5V$$

$$\text{Reactance voltage} = I_L * X_L \\ = 0.7 * 2\pi fL$$

$$\text{Where } X_L = j\omega L = 2\pi fL$$

$$= 0.7 * 2\pi * 50 * 0.25$$

$$= 54.98$$

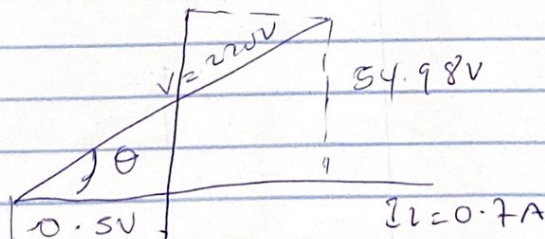

$$E_b \text{ ac} = \sqrt{V^2 - (X_L)^2} - IR$$

$$= \sqrt{(220)^2 - (54.98)^2} - 10.5V$$

$$E_b = 202.52V$$

(i) Recall Speed Constant Equation

$$\frac{n_2}{n_1} = \frac{E_{b2}}{E_{b1}}$$

$$\text{So } \frac{E_{bac}}{E_{bdc}} = \frac{n_{ac}}{n_{dc}}$$

$$\text{making } n_{ac} = n_{dc} \times \frac{E_{bac}}{E_{bdc}}$$

$$= 2000 \times \frac{202.52 \text{ V}}{209.5 \text{ V}}$$

$$n_{ac} = 1933.37 \text{ rpm}$$

(ii) Power factor,  $\cos \phi = \frac{E_{bac} + IR}{V}$

$$= \frac{202.52 + 10}{220}$$

$$= 0.968 \text{ lagging}$$

$$\frac{n_2}{n_1} = \frac{E_{b2}}{E_{b1}}$$

$$\frac{E_{bac}}{E_{bdc}} = \frac{n_{ac}}{n_{dc}}$$

$$n_{ac} = n_{dc} \times \frac{E_{bac}}{E_{bdc}}$$

$$= 2000 \times \frac{202.52 \text{ V}}{209.5 \text{ V}}$$

$$= 1933.37 \text{ rpm}$$

3 (iii)

$\omega = 2\pi n$ , where  $n = \text{speed}$

$$T_{ac} = \frac{E_{bac} \times I_c}{2\pi \times \frac{N_{ac}}{60}}$$

$$= \frac{202.52 \times 0.7 \times 60}{2\pi \times 1733.37}$$

$$= 0.700 \text{ Nm}$$

Torque developed = 0.700 Nm.

3 (iv) It is a universal motor because it has both direct current or single phase AC supply.

ELECT/ELECT  
17/Engg/1014