

17/ENG06/064
Mechanical
300 Level.

Olayide Anjo Alex

①

Solution

Question 1

Given data: $\text{Eff} = 85\%$
 $P \cdot \text{factor} = 0.7$
 $f = 50 \text{ Hz}$
 $P = 74.6$
 $V = 415 \text{ V}$

A.P.f = Actual power factor
T.P.f = Target power factor

(i) $\text{unity} = 1$

formula

$$C = \frac{\text{KVAR}}{2\pi f V^2}$$

$$\therefore \text{KVAR} = P \times [\tan \text{A.P.f} - \tan \text{T.P.f}]$$

$$\text{A.P.f} = \cos \theta = 0.7$$

$$\theta = \cos^{-1} 0.7$$

$$\theta = 45.57$$

$$\therefore \text{tangent of } 45.57 = 1.0201$$

$$\text{T.P.f} = \cos \theta = 1$$

$$\theta = \cos^{-1} 1 = 0$$

$$\tan \theta, \tan \theta = 0$$

$$\begin{aligned} \therefore \text{KVAR} &= 74.6 \times (\tan \text{A.P.f} - \tan \text{T.P.f}) \\ &= 74.6 \times (1.0201 - 0) \\ &= 76.0995 \\ &= 76.10 \end{aligned}$$

17/ENG06/06P
Mechanical
300 level.

Olayide Ariyo Alex

②

Soln

$$C = \frac{76.10}{2\pi \times 50 \times 415^2}$$

DLH/M/M

$$C = \frac{76.10}{54,113,097}$$

$$C = 0.0000014$$

$$(ii) A.P.f = 1.0201$$

Given = 0.9 lagging

$$T.P.f = \cos \theta = -0.9$$

$$\theta = \cos^{-1}(-0.9) \\ = 154.16$$

$$\tan \theta = -0.48$$

$$KVAR = 74.6 \times (1.0201 - (-0.48)) \\ = 111.90$$

$$\text{Appro} = 112$$

$$C = \frac{KVAR}{2\pi fV}$$

$$= \frac{112}{2\pi \times 50 \times 415^2}$$

$$= \frac{112}{54,113,097}$$

$$= 0.0000020700$$

17EN906/064 Olayide Arigo Alex.

Mechanical
300 Level.

3

Electrical Machines II Question 2

Solutions

① $V_1 = 415V$

$N \cdot \text{pole} = 6$


$k = 0.83$

$f = 50 \text{ Hz}$

$R_x = Z_1 = 0.25 + j0.75$ for stator

$= Z_2 = 1.173 + j0.52$ for rotor

Diagram

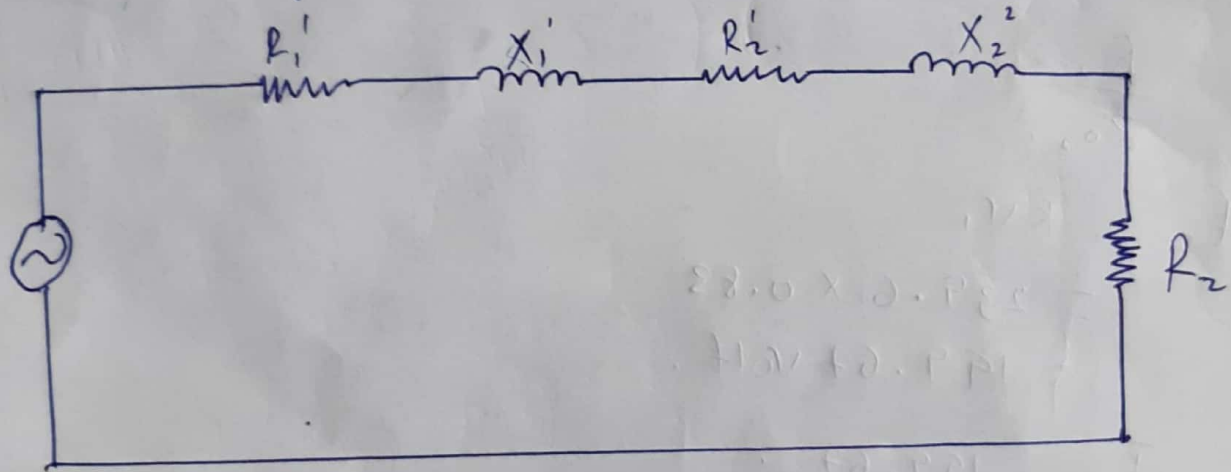

$\text{S.V. per phase } v = \frac{415}{\sqrt{3}} = 239.60V$

Rotor

$R_{02} = (R_2 + k^2 R_1)$
 $= (1.173 + (\frac{5}{6})^2 \times 0.25)$

$R_{02} = 1.347 \text{ Ohms}$

$X_{02} = (X_2 + k^2 X_1)$
 $= j(0.52 + (\frac{5}{6})^2 \times 0.75)$
 $= 1.041$

OLAYIDE ARYO ALEX.
171ENC061064.

Mechanical
300 level.



$$Z_{02} = R_{02} + jX_{02}$$

$$= 1.347 + j1.041$$

$$Z_{02} = \sqrt{1.347^2 + 1.041^2}$$

$$Z_{02} = \underline{\underline{1.7 \text{ ohms}}}$$

(ii) Rotor current.

$$I_2 = \frac{E_2}{Z_{02}}$$


$$E_2 = KV_1$$

$$= 239.6 \times 0.83$$

$$= 199.67 \text{ volt.}$$

$$\therefore I_2 = \frac{199.67}{1.7}$$
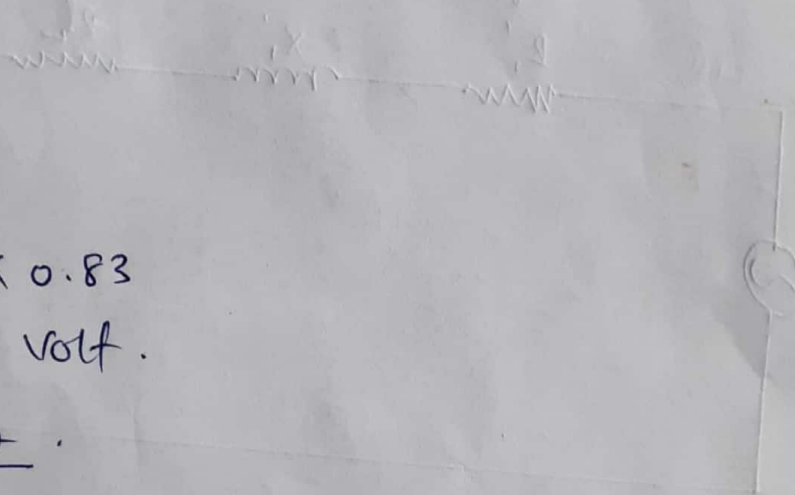
$$= \underline{\underline{117.45 \text{ Ampere}}}$$



Solutions

Question 3

Given data: $f = 50 \text{ Hz}$

$\frac{1}{4} \text{ hp}$

$N_{oc} = 2000 \text{ rpm}$

DC Supply

S.V = 220V

Current drawn $I_2 = 0.7 \text{ A}$

$$V - E_b = I_2 \times R$$

$$V - [I_2 \times R] = E_b$$

$$E_b = 220 - [0.7 \times 15]$$

$$= 209.5 \text{ V}$$

AC Supply

S.V = 220V

Current drawn $I_2 = 0.7 \text{ A}$

Resistance drop $I_2 \times R = 0.7 \times 15$

$$= 10.5 \text{ V}$$

Reactance voltage drop $= I_2 \times X_2$

$$= 0.7 \times 2\pi f l$$

$$= 0.7 \times 2 \times 3.142 \times 50 \times 0.25$$

$$= 54.98 \text{ V}$$

17ENG061064.

Olayide Ariyo Alex.

⑥

Mechanical

300 level

Electrical Machine.


Solution

Continuation.

Where $X_L = j\omega l = 2\pi f l$

$$X_L = 2\pi f l$$

$$X_L = 54.98 \Omega$$

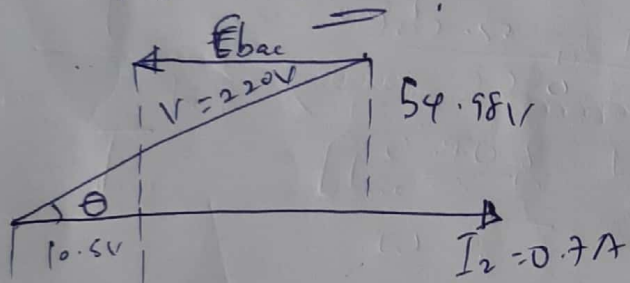

$$E_{bae} = \sqrt{V^2 - [X_L I_2]^2} - I_2 R$$

$$= \sqrt{(220)^2 - (54.98)^2} - 10.5 \text{ V}$$

$$= \underline{\underline{202.52 \text{ V}}}$$

Speed.

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}$$

$$\frac{E_{bae}}{E_{bdc}} = \frac{N_{ae}}{N_{dc}}$$

$$N_{ae} = N_{dc} \times \frac{E_{bae}}{E_{bdc}}$$

$$= 2000 \times \frac{202.52 \text{ V}}{209.54}, N_{dc} = 1933.37 \text{ rpm.}$$

17/EUG06/064

Olayide Anjo Alex

Mechanical

300 Level

Solution

(7)

$$\begin{aligned} \text{(ii) Power factor, } \cos\phi &= \frac{E_{bac} + I_r}{V} \\ &= \frac{202.52 + 10.5}{220} \\ &= \underline{\underline{0.968}} \text{ lagging} \end{aligned}$$

(iii) Torque developed $\omega = \text{speed, in rad/s}$

$$\bar{T}_w = E_{bac} \times \bar{I}$$

$n = \text{speed, in rev/s}$

$$\bar{T}_{ac} = \frac{E_{bac} \times \bar{I}}{\omega}$$

$$\omega = 2\pi n$$

$$\bar{T}_{ac} = \frac{E_{bac} \times \bar{I}}{2\pi \times \frac{M_{ac}}{60}} \quad \text{to convert to rad/sec}$$

$$\bar{T}_{ac} = \frac{202.52 \times 0.7 \times 60}{2\pi \times 1933.37}$$

$$= 0.700 \text{ Nm}$$

$$\underline{\underline{= 0.7 \text{ Nm}}}$$