

Question 3.

$$V - E_b = I \times R$$

~~$$E_b = 220 - [15 \times 0.7]$$~~

$$E_b = 220 - [15 \times 0.7]$$


$$= 209.5V$$

$$\text{Reactive voltage drop} = I \times R$$

$$= 0.7 \times 2\pi fL$$

$$= 0.7 \times 2\pi \times 50 \times 0.25$$

$$= 54.98V$$

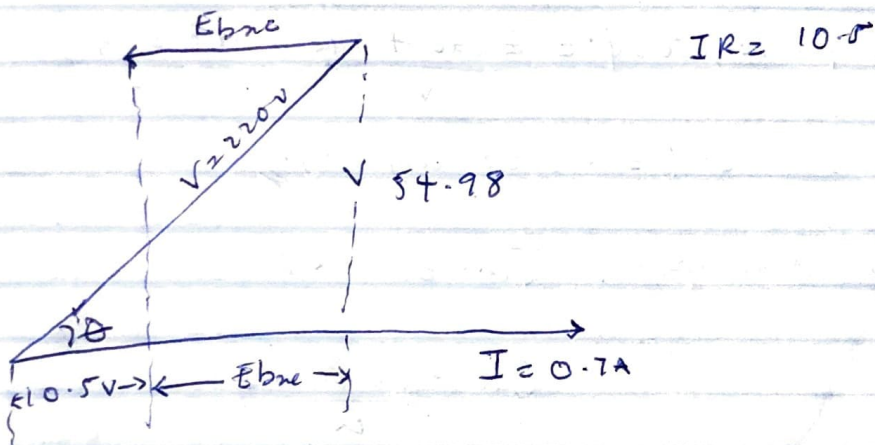

$$E_{bqc} = \sqrt{V^2 - (I \times R)^2} - IR$$

$$= \sqrt{[220]^2 - [54.98]^2} - 10.5$$

$$E_{bqc} = \sqrt{48400 - 3022.8} - 10.5$$

$$E_{bqc} = \sqrt{45377.2} - 10.5$$

$$E_{bqc} = 213.019 - 10.5$$

$$E_{bqc} = 202.51V$$

Recall speed control equation

$$\frac{N_a}{N_i} = \frac{E_{b2}}{E_{b1}} = \frac{E_{bac}}{E_{bdc}} = \frac{N_{ac}}{N_{dc}}$$

$$N_{ac} = N_{dc} \times \frac{E_{bac}}{E_{bdc}}$$

$N_{dc} = 2000 \text{ rpm}$
 $E_{bac} = 202.5 \text{ V}$
 $E_{bdc} = 229.5 \text{ V}$

$N_{ac} = 2000 \times \frac{202.5}{229.5}$

$N_{ac} = 2000 \times 0.882$
 $= 1764.8 \text{ rpm} \quad 1933.37 \text{ rpm}$

i) speed = $N_{ac} = 1764.8 \text{ rpm} \quad 1933.37 \text{ rpm}$

ii) power factor, $\cos \phi = \frac{E_{bac} + IR}{V} = \frac{202.5 + 10.5}{220}$

$\cos \phi = 0.968 \text{ lagging.}$

iii) Torque developed $T_w = E_{bac} \times I$

$T_{ac} = \frac{E_{bac} \times I}{\omega}$

$\omega = 2\pi n$

$T_{ac} = \frac{E_{bac} \times I}{2\pi \times \frac{N_{ac}}{60}}$

$= \frac{202.5 \times 0.7 \times 60}{2\pi \times 1933.37}$

$= \frac{202.5 \times 0.7 \times 60}{2\pi \times 1934.8}$

$= \frac{8505.42}{12149.3}$

$T_{ac} = \frac{8505.42}{11090.0}$

$= 0.700 \text{ Nm}$

$T_{ac} = 0.767 \text{ Nm}$

$T_{ac} = 0.700 \text{ Nm}$

Question 2

$$V_{me} = 415V$$


$$\text{No of poles} = 6$$

$$f = 50\text{Hz}$$

$$k = \frac{5}{6} = 0.83$$

$$Z_1 = 0.25 + j0.75 \quad \text{--- stator}$$
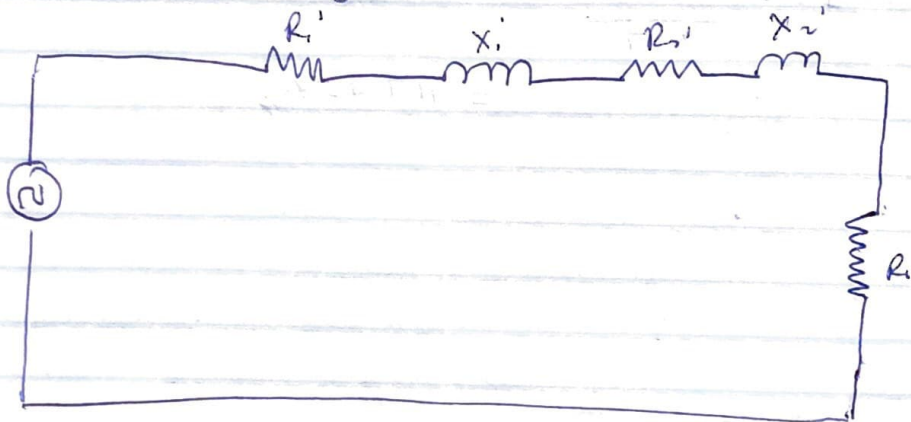
$$Z_2 = 1.173 + j0.52 \quad \text{--- rotor}$$



$$\text{supply voltage per phase, } V = \frac{415}{\sqrt{3}}$$

$$= 239.60V$$

Referring to rotor side

$$R_{02} = (R_2 + k^2 R_1)$$
$$= (1.173 + (\frac{5}{6})^2 \times 0.25)$$

$$R_{02} = 1.347 \text{ ohms}$$

$$X_{02} = (X_2 + k^2 X_1)$$
$$= j(0.52 + (\frac{5}{6})^2 \times 0.75)$$
$$= 1.041$$

$$Z_{02} = R_{02} + X_{02}$$
$$= 1.547 + j1.041$$

$$Z_{02} = \sqrt{1.547^2 + 1.041^2}$$
$$= 1.75 \text{ ohms}$$

to find the rotor current

$$I_2 = \frac{E_2}{Z_{02}}$$

Note that $E_2 = kV_1$

$$= 239.6 \times 0.85$$

$$= 199.67 \text{ V}$$

$$\therefore I_2 = \frac{199.67}{1.7}$$

$$= 117.45 \text{ A}$$

Question 1

16) $V = 415V$, 3 phase,
4 wire, $f = 50Hz$, $P = 74.6$
power factor = 0.7
efficiency = 85%

i) unity = 1

$$C = \frac{kVAR}{2\pi fV^2}$$

$$\therefore kVAR = P \times (\tan \text{ actual p.f} - \tan \text{ target p.f})$$

$$\text{actual p.f} = \cos \theta = 0.7$$

$$\theta = \cos^{-1} 0.7$$

$$= 45.57$$

$$\tan (45.57) = 1.0201$$

$$\text{target p.f} \Rightarrow \cos \theta = 1$$

$$\theta = \cos^{-1} 1 = 0$$

$$\tan 0 = 0$$

$$kVAR = 74.6 \times (1.0201 - 0)$$

$$= 76.0995$$

$$\approx 76.10$$

$$C = \frac{76.10}{2\pi \times 50 \times 415^2} = \frac{76.10}{54113095}$$

$$= 0.0000014 = 1.4 \times 10^{-6} C_{\mu}$$

ii) 0.9 lagging

$$\text{actual p.f} = 1.0201$$

$$\text{target p.f} = \cos \theta = -0.9$$

$$\theta = \cos^{-1}(-0.9)$$

$$= 154.16$$

$$\tan \theta = \tan(154.16)$$

$$= -0.48$$

$$\text{kVAR} = 74.6 \times (1.0201 - (-0.48))$$
$$= 111.90 = 112$$

$$C = \frac{\text{kVAR}}{2\pi fV^2}$$

$$= \frac{112}{2\pi \times 50 \times 415^2} = \frac{112}{54113095}$$

$$= 2.07 \times 10^{-6} \text{ C} = 0.0086 \mu\text{F}$$
$$= 8.6 \times 10^{-4} \mu\text{F}$$