

QUESTION 2

V = 415V


is of Phase C

f = 50Hz

$\cos \phi = 0.85$

$R = Z \cdot \cos^2 \phi + j0.85X$

$\cos^2 \phi = 0.7225$ motor

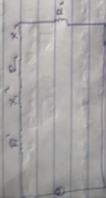

Supply voltage = 415V

Phase V = 45°

$\sqrt{3} = 237.600$

difference

$R_{02} = (1.173 + 0.95) \times 4.025$

$R_{02} = 1.547$

$X_{02} = (X_1 + X_2)$

$j \cos^2 \phi (0.95) \times 0.75$

$= 1.041$

$Z_{02} = R_{02} + jX_{02}$

$= 1.547 + j1.041$

$Z_{02} = \sqrt{1.547^2 + 1.041^2}$

$= 1.76$

To find motor current

$I = \frac{V}{Z_{02}}$

Z_{02}

Recall that $G = kV$,

$= 237.6 \times 0.85$

$= 179.670$

$\therefore I = \frac{415}{1.76} = 11.45A$

1.1

$$2000 \sqrt{1 + \frac{2000}{2000}} = 2000 \sqrt{2} = 2828.4$$

Recall speed constant equation.

$$\frac{N_s \cdot G_{sh}}{N_s \cdot G_{sh}}$$

$$\frac{20 \text{ ft} \cdot \text{min} \cdot N_{nc}}{\text{ft} \cdot \text{min}} \cdot \frac{N_{dc}}{N_{dc}}$$

$$= 2000 \times 202.52 \times 209.5 \text{ V}$$

$$N_{nc} = 1133.51 \text{ rpm}$$

$$\text{power factor} = \cos \phi = G_{sh} \cdot T_{dc}$$

$$= 202.52 \times 10$$

$$= 220$$

$$\text{Torque developed } T_{dc} = G_{sh} \cdot 0.768 \text{ m} = 220$$

Recall speed constant eqn

$$\frac{N_s \cdot G_{sh}}{N_s \cdot G_{sh}}$$

$$G_{sh} = \frac{N_{dc}}{N_{dc}}$$

$$\frac{2000 \times 202.52 \times 209.5}{209.5}$$

$$\text{Torque developed } T_{dc} = G_{sh} \cdot X$$

$$2000 \times 202.52 \times 209.5$$

$$= 209.5$$

$$N_{nc} = 1733.51 \text{ rpm}$$

$$\text{Power factor} = \cos \phi = \frac{G_{sh} \cdot T_{dc}}{V}$$

$$= \frac{202.52 \times 0.768}{209.5}$$

$$= 0.706 \text{ Nm}$$

$$= 0.706 \text{ Nm}$$

MATRIC NO: 11ENR061078
 DEPARTMENT: MECHANICAL ENGINEERING
 COURSE CODE:

QUESTION 1

$$1.4(5v)^3 - 0 + \dots \text{where } f = 50 \text{ Hz} \therefore f = 74 \text{ m}$$

$$Pf = 0.7 \text{ To eff} = 25\%$$

i) $V = f_0 - 1$
 $C = \text{KVAR}$

$$\frac{2PFV}{K - \text{ma}} = P \times C \text{ then actual P.f. then target P.f.}$$

$$\text{actual P.f.} = \cos \theta = 0.7$$

$$\approx 45.57$$

$$\text{then } C = 5.5 \text{ D} = 1.0201$$

$$\text{target P.f.} = \cos \theta = 1$$

$$\theta = \cos^{-1} a = 0$$

$$\text{then } \theta = 0$$

$$\text{KVAR} = 74.6 \times C (1.0201 - 1)$$

$$\approx 76.10$$

$$C = 76.10$$

$$\frac{2 \times 1.50 \times (4.5)^2}{\sqrt{3}}$$

$$= 4.22 \times 10^{-6}$$

ii) $0.7 \text{ lag} \rightarrow$

$$\text{actual P.f.} = 1.0201$$

$$\text{target P.f.} = \cos \theta = 0.7$$

$$\theta = \cos^{-1} (0.7)$$

$$\theta = 154.11$$

$$\text{then } \theta = \tan^{-1} (0.16)$$

$$\approx 0.146$$

$$\text{KVAR} = 74.6 \times C (1.0201 - \cos \theta)$$

$$\approx 11.70$$

$$C = 11.2$$

$$\frac{2 \times 1.50 \times (4.5)^2}{\sqrt{3}}$$

$$= 6.21 \times 10^{-6}$$

QUESTION 3

$f = 50 \text{ Hz}$ $N = 2000$ $p = 220$ $V = 220$

$15 - 10$

On AC supply

Supply voltage $= 220 \text{ V}$

Current draw $= I = 0.7 \text{ A}$



$V = E_b + I_a R$

$V = [I_a R] + E_b$

$220 = 220 + [0.7 \times 15]$
 $= 209.5 \text{ V}$

Speed on DC

$N_{dc} = 2000 \text{ rpm}$

On AC supply

Supply voltage $= 220 \text{ V}$

Reactance drop $I_a X_L = 0.7 \text{ A}$

$I_a R = 0.7 \times 15$

$= 10.5 \text{ V}$

Reactance voltage drop $I_a X_L$

$= 0.7 \times 220$

$= 154 \text{ V}$

$= 0.7 \times 25 + 30 + 0.7 \times 25$

$= 34.75 \text{ V}$

