

① 17/ENG 06/037 MECHANICAL ENG 300LVL

415V, 3-phase, 4-wire, 50Hz

$$P_{\text{mech}} = 74.6 \text{ kW}$$

Power factor = 0.7 lagging

$$\text{Efficiency} = 85\%$$

$$\therefore \text{Since efficiency} = 85\% \therefore 85 = \frac{74.6}{x} \times 100$$

$$\therefore 85 = \frac{7460}{x}$$

$$x = 87.76 \text{ kW}$$

$$\therefore \text{Power Input} = 87.76 \text{ kW}$$

$$\therefore V_{\text{phase}} = \frac{V_{\text{line}}}{\sqrt{3}} \therefore V_{\text{phase}} = \frac{415}{\sqrt{3}} = 239.6 \text{ V}$$

$$\therefore \text{P.F} = \frac{\text{Real Power}}{\text{Apparent Power}} \therefore 0.7 = \frac{87.76 \times 10^3}{S}$$

$$\therefore S = 125371.43 \text{ VA} = 125.371 \text{ kVA}$$

It is a Synchronous Motor

Recall S Apparent Power = $\sqrt{(\text{Real Power})^2 + (\text{Reactive Power})^2}$

Reactive Power (Q) = $\sqrt{(\text{Apparent Power})^2 - (\text{Real Power})^2}$

\therefore Reactive Power (Q) = $\sqrt{(125.371 \times 10^3)^2 - (87.76 \times 10^3)^2}$

Reactive Power (Q) = 89532.5 VAR = 89.533 kVAR

(a) When power factor = 1

~~$\therefore 1 = \frac{\text{Real Power}}{125.371 \times 10^3}$~~

~~125.371×10^3~~

~~\therefore Real Power = 125.371×10^3 kVA~~

~~\therefore Reactive Power (Q) = $\sqrt{(125.371 \times 10^3)^2 - (125.371 \times 10^3)^2}$~~

$1 = \frac{87.76 \times 10^3}{S} \quad \therefore S = 87.76 \times 10^3$ VA

\therefore Reactive Power (Q) = $\sqrt{(87.76 \times 10^3)^2 - (87.76 \times 10^3)^2}$

Reactive Power $Q_{\text{new}} = 0$ kVAR

$\therefore Q_{\text{cap}} = 0 - (89.533 \times 10^3) = -89.533$ kVAR

\therefore Recall $X_c = \frac{V^2}{Q} \quad \therefore X = \frac{(415.4)^2}{(-89.533 \times 10^3)}$

$X_c = 1.924 \Omega$

\therefore Recall $X_c = \frac{1}{2\pi f C}$

$\therefore C = \frac{1}{2\pi f X_c}$

$\therefore C = \frac{1}{2 \times \pi \times 50 \times 1.924}$

$C = 1.65 \times 10^{-3}$ F

①

(b) When power factor = 0.9 .

$$\therefore 0.9 = \frac{87.76 \times 10^3}{S}$$

$$\therefore S = 97511.11 \text{ kVA}$$

$$\therefore \text{Reactive Power (Q)} = \sqrt{(97.511 \times 10^3)^2 - (87.76 \times 10^3)^2}$$
$$= 42503.85 \text{ kVAR}$$

$$\therefore Q_{\text{capacitor}} = 42503.85 - 89532.5 = -47028.65 \text{ VAR}$$

$$\therefore X = \frac{V^2}{Q} \quad \therefore X = \frac{(415)^2}{(47028.65)}$$

$$X_c = 3.66 \Omega$$

$$\therefore C = \frac{1}{2\pi f X_c}$$

$$\therefore C = \frac{1}{2 \times \pi \times 50 \times 3.66}$$

$$C = 8.7 \times 10^{-4} \text{ F}$$

(2) Power = 25hp No. of poles = 6 pole

Voltage $\Rightarrow V_{line} = 415V$ $f = 50Hz$

Star connected: $V_{line} = \sqrt{3} \cdot V_{phase}$

Stator/Rotor phase voltage = 6/5

$Z_1 \rightarrow (0.25 + j0.75)$

$Z_2 \rightarrow (1.173 + j0.52)$


$s = 1$

$$\therefore V_{phase} = \frac{V_{line}}{\sqrt{3}} = \frac{415}{\sqrt{3}} = 239.6V$$

$$\therefore \frac{E_1}{E_2} = \frac{6}{5} \quad \therefore \frac{239.6V}{E_2} = \frac{6}{5}$$

$$E_2 = 199.67V \quad \therefore k = \frac{6}{5} = 1.2$$

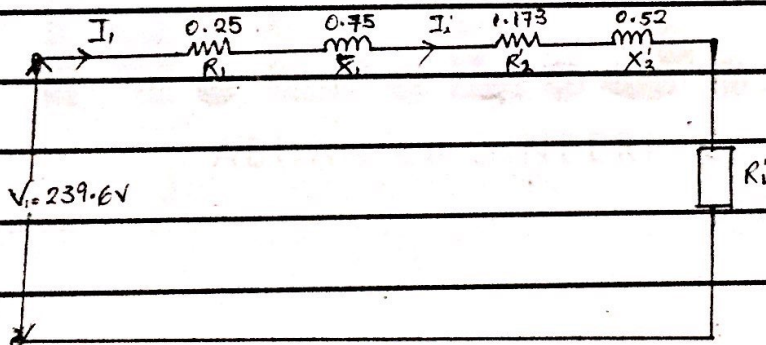
(a) Approximate Circuit Version 2 ~~Diagram~~ Diagram referred to the rotor side.



$$I_1 = I_2' \quad R_L' = \frac{R_2'}{k^2} \left[\frac{1-s}{s} \right]$$

$$\therefore R_L' = \frac{1.173}{(1.2)^2} \left[\frac{1-1}{1} \right] \therefore R_L' = 0\Omega$$

\therefore Resulting Diagram:

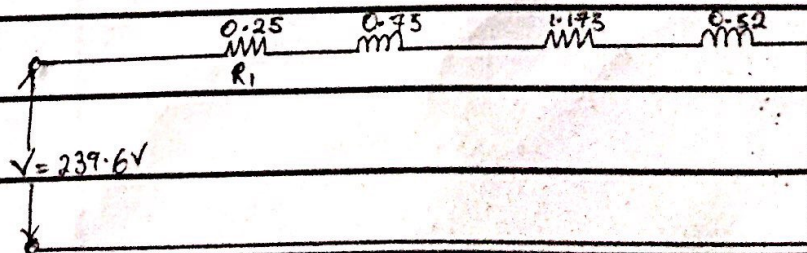

② 17/ENG06/037

MECHANICAL ENGINEERING

300LVL

$$(b) \therefore Z_{total} = Z_1 + Z_2'$$

$$= (0.25 + j0.75) + (1.173 + j0.52)$$

$$= 1.423 + j1.27$$

$$\therefore I_1 = \frac{E_1}{Z_{total}}$$

$$I_1 = \frac{239.6}{(1.423 + j1.27)}$$

$$I_1 = 93.724 \angle -83.65^\circ \rightarrow 125.62A \angle -41.75^\circ$$

\therefore Since it is the approximate version II

$$I_1 = I_2'$$

$$\therefore I_2' = 125.62A \angle -41.75^\circ$$

3

When connected to DC: $f = 50\text{Hz}$, Power = 0.25Hp , $N_r = 2000\text{rpm}$
 $i = 0.7\text{A}$, $V = 220\text{V}$, $R = 15\Omega$, $L = 0.25\text{H}$

When connected to AC: $V = 220\text{V}$, $f = 50\text{Hz}$, $i = 0.7\text{A}$

$$\therefore \text{On DC: } E_b = V - IR$$

$$\therefore X_L = 2\pi fL$$

$$X_L = 2\pi \times 50 \times 0.25 = 78.54\Omega$$

$$\therefore E_b = V - IR$$

$$E_b = 220 - (0.7)(15)$$

$$E_b = 209.5\text{V}$$

$$\text{(i) On AC: } E_b = \sqrt{V^2 - [iX_L]^2} - IR$$

$$\text{Also } \frac{E_{bac}}{E_{bdc}} = \frac{N_{ac}}{N_{dc}}$$

$$E_{bac} = \sqrt{(220)^2 - [0.7 \times 78.54]^2} - (0.7 \times 15)$$

$$E_{bac} = 202.52\text{V}$$

$$\therefore \frac{202.52}{209.5} = \frac{N_{ac}}{2000}$$

$$\therefore N_{ac} = 1933.37\text{rpm}$$

$$\text{(ii) Power Factor} \Rightarrow \frac{IR + E_b}{V} = \frac{(0.7)(15) + 202.52}{220} = 0.97$$

(iii) Torque (Power) Power = $T\omega$ where $T = \text{torque}$, $\omega = \text{Angular speed}$.

③ 17/ENG 06/037th MECHANICAL ENG 300 LVL

$$\therefore \text{Torque} = \frac{\text{Power}}{\omega}$$

$$\therefore \omega = \frac{2\pi N}{60} = \frac{2 \times \pi \times 1933.37}{60} = 202.46 \text{ rad/s}$$

$$\therefore \text{Power} \rightarrow V_{\text{line}} \cdot I_{\text{line}} \cdot \cos \theta$$

$$\therefore \text{Power} = 220 \times 0.7 \times 0.97$$

$$\text{Power} = 149.38 \text{ watts}$$

$$\therefore \text{Torque} = \frac{149.38}{202.46} = 0.74 \text{ Nm}$$

(iv) A Universal Meter is to be used for this application.