

Okuong, David Victor
17/ENG006/063

Page 1

EEE326 Electrical Machines II Test

Question 1 (b)

Given: $V = 415\text{ V}$, 3- ϕ , 4-wire, $f = 50\text{ Hz}$, $P = 74.6$ P.F. = 0.7, % reg = 85.1.

i) Unity = 1

$$C = \frac{\text{KVAR}}{2\pi f V^2}$$

$$\rightarrow \text{KVAR} = P \times (\tan \text{ actual P.F.} - \tan \text{ target P.F.})$$

$$\text{Actual P.F.} \Rightarrow \cos \theta = 0.7$$

$$\theta = \cos^{-1} 0.7$$

$$= 45.57$$

$$\tan(45.57) = 1.0201$$

$$\text{target P.F.} = \cos \theta = 1$$

$$\theta = \cos^{-1}(1) = 0$$

$$\tan 0 = 0$$

$$\text{KVAR} = 74.6 \times (1.0201 - 0)$$

$$= 76.0995$$

$$= 76.10$$

$$C = \frac{76.10}{2\pi f V^2} = \frac{76.10}{2 \times \pi \times 50 \times (415)^2} = \frac{76.10}{2 \times \pi \times 50 \times (415)^2}$$

$$= 0.0000014$$

$$\therefore \approx 1.4 \times 10^{-6} \text{ C/F}$$

ii) 0.9 lagging

$$\text{actual P.F.} = 1.0201$$

$$\text{target P.F.} = \cos \theta = 0.9$$

$$\theta = \cos^{-1}(0.9)$$

$$= 26.10$$

$$\tan \theta = 0.48$$

$$\text{KVAR} = 74.6 \times (1.0201 - (-0.48))$$

$$= 111.90 \approx 112$$

Page 2

OKwong David Victor
17/EN606/063

$$C = \frac{kVAR}{2\pi fV}$$

$$= \frac{112}{2 \times \pi \times 50 \times 415^2}$$

$$= 0.00086$$

$$\approx 8.6 \times 10^{-4} \text{ C}$$

Question 2

$$V = 415 \text{ v}$$


$$N_s \text{ of Poles} = 6$$

$$f = 50 \text{ Hz}$$

$$k = \frac{5}{6} = 0.83$$

$$R = Z_1 = 0.25 + j0.75 \text{ — 8 turns}$$
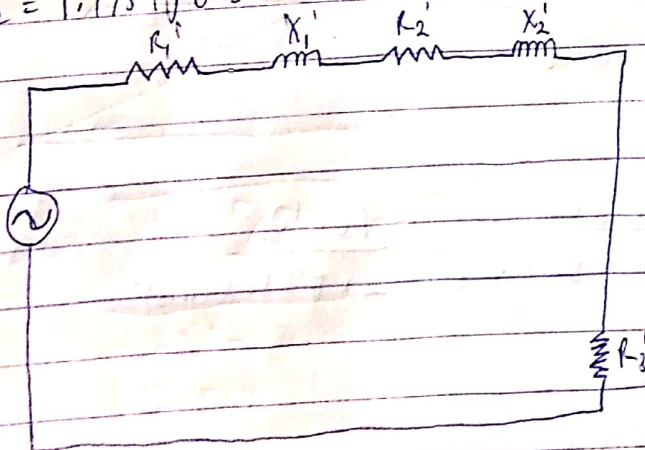
$$Z_2 = 1.173 + j0.52 \text{ — 10 turns}$$



$$\text{Supply Voltage per Phase, } V = \frac{415}{\sqrt{3}} = 239.60 \text{ v}$$

~~Part a~~

$$R_{02} = (R_2 + k^2 R_1)$$
$$= 1.173 + \left(\frac{5}{6}\right)^2 \times 0.25$$

$$R_{02} = 1.347 \Omega$$

$$X_{02} = (X_2 + k^2 X_1)$$
$$= j(0.52 + \left(\frac{5}{6}\right)^2 \times 0.75)$$
$$= 1.041$$

Page 3
Okuong, David Victor
17/EN606/063

$$\begin{aligned}Z_{02} &= R_{02} + X_{02} \\ &= |0.347 + j1.041| \\ &= \sqrt{0.347^2 + 1.041^2} \\ &= \underline{1.1} = 1.7\Omega\end{aligned}$$

ii) To find rotor current

$$I_2 = \frac{E_2}{Z_{02}}$$

$$E_2 = kx_1$$

$$= 239.6 \times 0.83$$

$$= 199.67\text{V}$$

$$\therefore I_2 = \frac{199.67}{1.7} = \underline{117.45\text{A}}$$


Question 3

i) $f = 50\text{Hz}$, $\frac{1}{4}\text{Hp}$, $N_r = 2400\text{rpm}$, $V = 220\text{V}$
 $R = 15\Omega$, Inductance $= 0.25\text{H}$

DC supply,

Supply Voltage $= 220\text{V}$

Current draw $I = 0.7\text{A}$

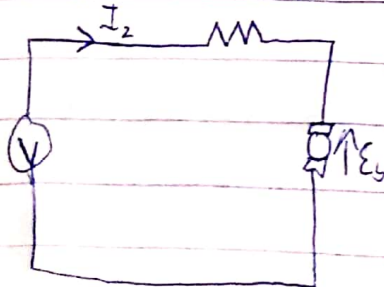

$$V - E_b = I_2 * R$$

$$V - [I_2 * R] = E_b$$

$$E_b = 220 - [0.7 * 15]$$

$$= 209.5\text{V}$$

Page 4
 Okwong, David Victor
 17/ENG06/063

Speed on DC,
 $N_d = 2000 \text{ rpm}$

On AC Supply



Supply Voltage = 220V

Current drawn = $I_L = 0.7 \text{ A}$

Resistance drop = $I_L \times R = 0.7 \times 15 = 10.5 \text{ V}$

Reactance Voltage drop = $I_L \times X_L$
 $= 0.7 \times 2\pi fL$

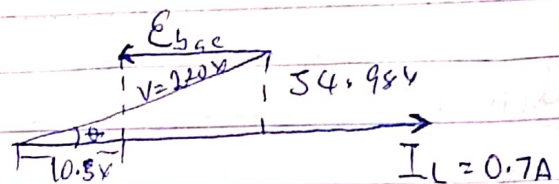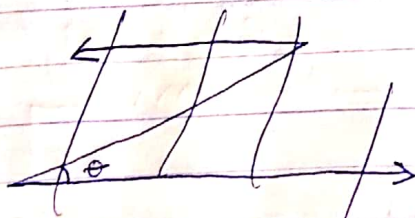Where $X_L = j \omega L = 2\pi fL$
 $= 0.7 \times 2\pi \times 80 \times 0.25$
 $= 54.98 \text{ V}$



$$E_{bac} = \sqrt{V^2 - [X_L]^2} - IR$$

$$= \sqrt{(220)^2 - (54.98)^2} - 10.5 \text{ V}$$

$$= 202.52 \text{ V}$$

Speed Constant Equation

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}$$

$$s_1 \frac{E_{bac}}{E_{bdc}} = \frac{N_{ac}}{N_{dc}}$$

Making N_{ac} subject of the formula

$$N_{ac} = N_{dc} \times \frac{E_{bac}}{E_{bdc}}$$

Page 5

Okeonye, David Victor
17/ENG006/063

$$2000 \times \frac{202.52 \text{ V}}{209.5 \text{ V}}$$

$$N_{ac} = \underline{1933.37 \text{ rpm}}$$

ii) Power Factor, $\cos \phi = \frac{E_{bac} + IR}{V}$

$$= \frac{202.52 + 10.5}{220}$$
$$= 0.968 \text{ Lagging}$$

iii) Torque developed $T_w = E_{bac} \times I$

$$T_{ac} = \frac{E_{bac} \times I}{\omega}$$

ω is speed in rad/s

$\omega = 2\pi n$, where n is speed in

$$T_{ac} = \frac{E_{bac} \times I}{2\pi \times \frac{N_{ac}}{60}}$$

$$= \frac{202.52 \times 0.7 \times 60}{2\pi \times 1933.37}$$
$$= 0.700 \text{ Nm}$$

iv)