

17/EMG06/048

Mechanical Engineering

300 Level

Question 1

ABUAD Marge juice factory is serviced by a 415V, 3-phase 4-wire, 50Hz. This supply powers the main drive motor having an output of 74.6kW and running on full load at a power factor of 0.7 Lagging with an efficiency of 85%. Identify the drive motor type and sketch the motor-supply circuit with a direct-online starter.

Determine the capacitance per phase of a mesh connected capacitor necessary to raise the power factor to i) unity ii) 0.9 Lagging.

Solution

$$V = 415V$$

$$F = 50Hz$$

$$P = 74.6$$

$$P.f = 0.7$$

$$\text{eff} = 85\%$$

$$3$$

$$i) \text{ unity} = 1$$

$$C = \frac{KVAR}{2\pi f V^2}$$

$$\left(KVAR = P \times \left(\frac{\tan \text{ actual P.F}}{\tan \text{ target P.F}} \right) \right)$$

$$\Rightarrow \text{actual P.f} = \cos \theta = 0.7$$

$$\theta = \cos^{-1} 0.7$$

$$\theta = 45.573$$

$$\tan(45.573) = 1.0202$$

$$\text{target P.f} = \cos \theta = 1$$

$$\theta = \cos^{-1} 1 = 0$$

$$\tan(0) = 0$$

17/EMG06(048

Mc
3,
Q

$$K_{VAR} = 74.6 \times (1.0202 - 0)$$

$$= 76.10692$$

$$\approx 76.1 \text{ var.}$$

Question 1

A 5
Gor
of
the
AC

$$C = 76.1 / (2 \times \pi \times 50 \times 415^2)$$

$$= 76.1 \times 1.405930403 \times 10^{-6} \text{ var}$$

i)
ii) 0.9 lagging

m) actual P.F = 1.0202

target P.F = $\cos \theta = -0.9$

$$\theta = \cos^{-1}(-0.9)$$

$$= 154.16$$

$$\tan \theta = -0.48$$

$$K_{VAR} = 74.6 \times (1.0202 - (-0.48)) = 111.91492$$

$$\approx 112 \text{ var}$$

$$C = \frac{K_{VAR}}{2\pi fV} = \frac{112}{2\pi \times 50 \times 415^2} = \cancel{0.0086} \approx 8.2069174837 \times 10^{-6} \text{ var}$$

Drive motor type is

17/EMG06(048

Mechanical Eng 30061

17/EMG06/048

Mechanical Engineering
300 Level

Question 2


A 25 hp, 415 V (Line-Line), 6-pole, 50 Hz, star-star connected 3-phase induction motor has used in the production factory of PZ cursons stator/rotor phase voltage ratio of 6/5.

The stator and rotor impedances per phase are $(0.25 + j0.75)$ ohms and $(1.173 + j0.52)$ ohms respectively.

Using the approximate circuit version 2 referred to the rotor side at a slip of unity. Find the following:

i) Draw the equivalent circuit diagram referred to the rotor side (version 2)

ii) Rotor (secondary) current I_2

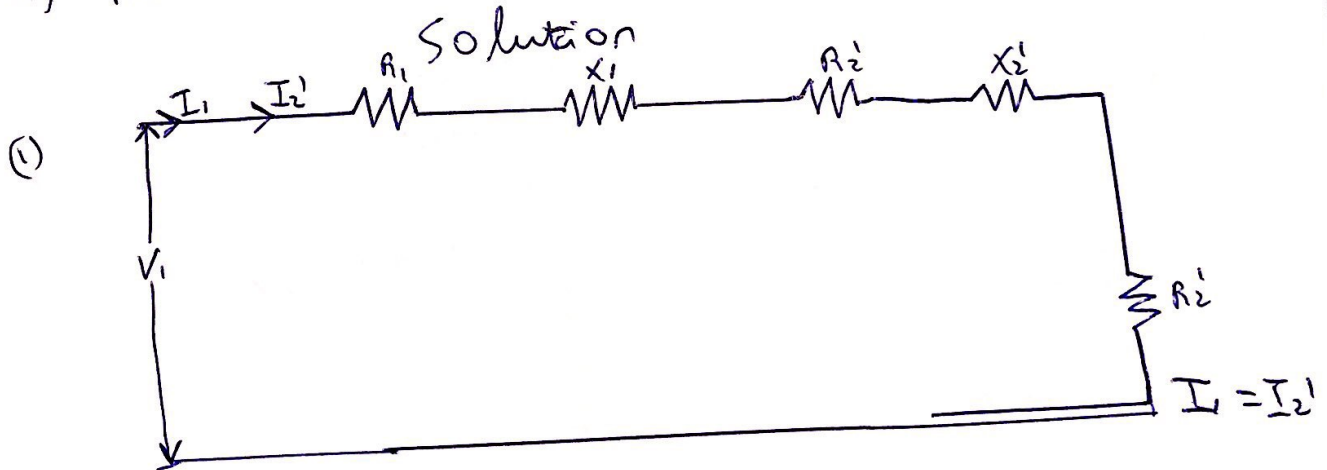

ii) Supply voltage per phase, $V = 415/\sqrt{3} = 239.60V$

$$\begin{aligned} \text{Rotor } R_{02} &= (R_2 + k^2 R_1) \\ &= (1.173 + (5/6)^2 \times 0.25) \\ &= 1.347 \Omega \end{aligned}$$

$$\begin{aligned} X_{02} &= \cancel{X_2} + j(0.52 + (5/6)^2 \times 0.75) \\ &= 1.041 \end{aligned}$$

$$\begin{aligned} Z_{02} &= R_{02} + X_{02} \\ &= 1.347 + j1.041 \end{aligned}$$

$$\begin{aligned} Z_{02} &= \sqrt{1.347^2 + 1.041^2} \\ &= 1.7 \Omega \end{aligned}$$

To find rotor current

$$I_2 = E_2 / Z_{02}$$

Recall that $E_2 = kV_1$

$$= 239.6 \times 0.85$$

$$= 199.67 \text{ Volt}$$

$$\therefore I_2 = \frac{199.67}{1.7} = 117.45 \text{ A} \quad \checkmark$$

17/EMU06/048' 300kwh Measurement Eng

17/EM606(048

Mechanical Engineering

300 Level

Question 3

A 50Hz, 1/4hp motor runs at 2000rpm and takes 0.7A when connected to a 220V DC source. If the resistance and inductance of the machine are given as 15Ω and $0.25H$ respectively. Determine the following when the motor is connected to a 220V, 50Hz AC supply and is loaded to take 0.7A of current;

- i) Speed of the motor
- ii) Power factor of the motor
- iii) Torque developed by the motor
- iv) What type of motor could be used for this application

Solution


$$F = 50 \text{ Hz} \quad V = 220$$
$$1/4 \text{ hp}, (15\Omega), 0.25 \text{ H}$$

On DC supply; Supply voltage = 220V
Current draw, $I_L = 0.7 \text{ A}$

$$\text{Resistance drop} = I_L \times R = 0.7 \times 15 = 10.5 \text{ V}$$

$$\text{Reactance voltage drop} = I_L \times X_L = 0.7 \times 2\pi fL$$
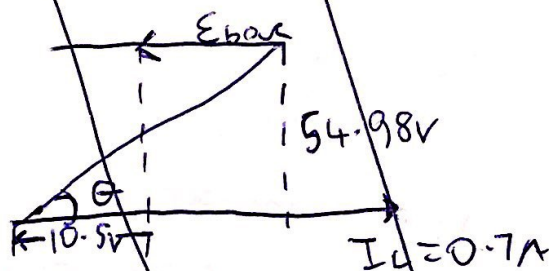
$$\text{where, } X_L = j\omega L = 2\pi fL$$
$$= 0.7 \times 2\pi \times 50 \times 0.25$$
$$= 54.98 \text{ V}$$



$$E_{bac} = \sqrt{V^2 - (X_L)^2} - IR$$
$$= \sqrt{(220)^2 - (54.98)^2}$$
$$= 213.019$$

17/04/2016/048


$$V - E_b = I_L \times R$$

$$V - [I_L \times R] = E_b$$

$$E_b = 220 - [0.7 \times 15]$$

$$= 209.5V$$

Speed on DC; $N_k = 2000 \text{ rpm}$

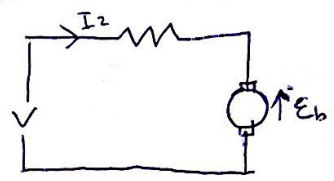


On AC Supply
 Supply Voltage = 220V
 Current, $I_L = 0.7A$

Reactance drop = $I_L \times R = 0.7 \times 15 = 10.5V$

Reactance voltage drop = $I_L \times X_L = 0.7 \times 2\pi fL$

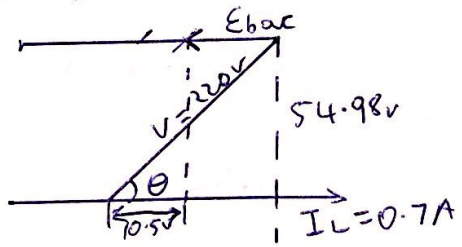Where, $X_L = 0.7 \times 2\pi \times 50 \times 0.25 = 54.98V$



$$E_{bac} = \sqrt{V^2 - (X_L)^2} - IR$$

$$= \sqrt{(220)^2 - (54.98)^2} - 10.5$$

$$= 213.019247 - 10.5$$

$$= 202.519247V$$

$$\approx 202.52V$$

1) $\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}$ so $\frac{E_{bac}}{E_{bac}} = \frac{N_{ac}}{N_{ac}}$

making N_{ac} subject of formula

$$N_{ac} = N_{dc} \times \frac{E_{bac}}{E_{bdc}} = 2000 \times \frac{202.52}{209.5}$$

$$N_{ac} = 1933.37 \text{ rpm}$$

$$\begin{aligned} \text{i) Power Factor, } \cos \phi &= \frac{E_{bac} + IR}{\sqrt{\quad}} \\ &= \frac{202.52 + 10}{\sqrt{220}} \\ &= 0.968 \text{ unit} \end{aligned}$$

17/EM606(048)

$$\begin{aligned} \text{ii) Torque developed, } T_w &= E_{bac} \times I \\ T_{ac} &= \frac{E_{bac} \times I}{\omega} \end{aligned}$$

$$\omega = 2\pi n$$

$$\begin{aligned} T_{ac} &= \frac{E_{bac} \times I_L}{2\pi \times 1933.37/60} \\ &= \frac{202.52 \times 0.7 \times 60}{2\pi \times 1933.37} \\ &= 0.700 \text{ Nm} \end{aligned}$$