

17/ENG06/040

Mechanical Engineering

300 Level

Question 1

$$V = 45$$

$$3 - \phi$$

4 wire

$$f = 50 \text{ Hz}$$

$$P = 74.6$$

$$P.f = 0.7$$

$$\text{eff} = 85\%$$

$$b(i) \text{ Unity} = 1$$

$$C = \frac{\text{KVAR}}{2\pi f V^2}$$

$$\text{KVAR} = P \times (\tan \text{ actual P.f} \times \tan \text{ target P.f})$$

actual P.f

$$\cos \theta = 0.7$$

$$\theta = \cos^{-1} 0.7$$

$$\theta = 45.57$$

$$\tan (45.57) = 1.02$$

target P.f

$$\cos \theta = 1$$

$$\theta = \cos^{-1} 1 = 0$$

$$\tan 0 = 0$$

$$\text{KVAR} = 74.6 \times (1.020 - 0)$$

$$\text{KVAR} = 76.092$$

$$\text{KVAR} = \approx 76.1$$

17/ENG06/040

$$C = \frac{76.1}{2\pi \times 50 \times 415^2} = 0.0000014 \approx 1.4 \times 10^{-6} \text{ C}$$

ii) 0.9 lagging

$$\text{Actual P.f} = 1.02$$

$$\text{target P.f} = \cos \theta = -0.9$$

$$\theta = \cos^{-1}(-0.9)$$

$$= 154.16$$

$$\tan \theta = -0.48$$

$$\text{KVAR} = 74.6 \times (1.020 - (-0.48))$$
$$= 111.90 \approx 112$$

$$C = \frac{\text{KVAR}}{2\pi f V}$$

$$= \frac{112}{2\pi \times 50 \times 415^2}$$

$$= 0.00086$$

$$= 8.6 \times 10^{-4} \text{ C}$$

17/ENG06/040

Mechanical Engineering

300L

Question 2

$$V = 415V$$


$$\text{No of poles} = 6$$

$$F = 50\text{Hz}$$

$$K = 5/6 = 0.83$$

$$R \times Z_1 = 0.25 + j0.75 \quad \text{--- stator}$$
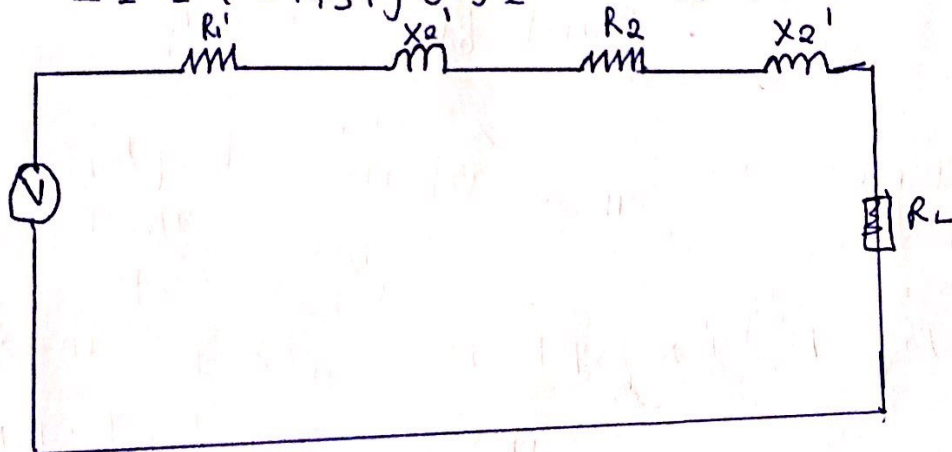
$$Z_2 = 1.173 + j0.52 \quad \text{--- Rotor}$$



$$\text{Supply Voltage } V = \frac{415}{\sqrt{3}} = 239.60V$$

referring to

$$\begin{aligned} R_{02} &= (R_2 + K^2 R_1) \\ &= (1.173 + (5/6)^2 \times 0.25) \\ &= 1.347 \Omega \end{aligned}$$

$$\begin{aligned} X_{02} &= (X_2 + K^2 X_1) \\ &= (0.52 + (5/6)^2 \times 0.75) \\ &= 1.041 \end{aligned}$$

$$\begin{aligned} Z_{02} &= R_{02} + jX_{02} \\ &= 1.347 + j1.041 \end{aligned}$$

$$\begin{aligned} Z_{02} &= \sqrt{1.347^2 + 1.041^2} \\ &= 1.7 \Omega \end{aligned}$$

17/ENG06/040

~~I_2~~ + rotor current

$$I_2 = \frac{E_2}{Z_{0.2}}$$

recall that $E_2 = KV$

$$= 0.83 \times 239.60 = 198.87V$$

$$I_2 = \frac{198.87}{1.7} = 116.99A$$

17/ENG06/040
Mechanical Engineering
300 L

Question 3

$$V = E_b = I_{\text{load}} \times R$$

$$E_b = 220 - [15 \times 0.7]$$

$$E_b = 209.5 \text{ V}$$

For the reactive voltage drop;

$$I_L \times R = 0.7 \times 2\pi f L$$


where $f = 50 \text{ Hz}$, $L = 0.25$

$$I_L \times R = 0.7 \times 2\pi \times 50 \times 0.25 \\ = 54.9 \text{ V}$$

For AC Supply

The Supply Voltage = 220V

Current drawn = 0.7 A

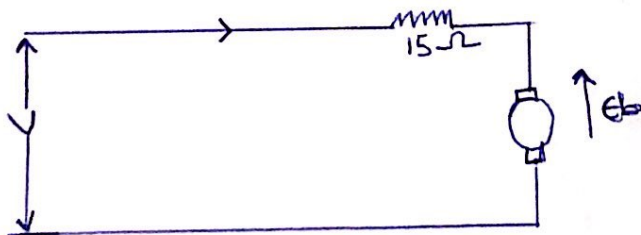

$$V - E_b = I_L \times R$$

$$V - I_L \times R = E_b$$

$$E_b = 220 - [15 \times 0.7]$$

$$E_b = 209.5 \text{ V}$$

∴ The speed ^{on AC} ~~with~~ ~~have~~ supply will have a back emf of 209.5V

On AC Supply

Supply Voltage = 220V

Current drawn $I = 0.7 \text{ A}$

Resistance drop = $I_L \times R = 0.7 \times 15 = 10.5 \text{ V}$

Resistance Voltage drop = $I_L \times X_L = 0.7 \times 2\pi f L$

Where $F = 50$, $L = 0.25$ 17/ENG061040

$$\therefore I_L \times X_L = 0.7 \times 2\pi \times 50 \times 0.25$$
$$= 54.9V$$

$$E_{bae} = \sqrt{V^2 - [I_L X_L]^2 - IR}$$
$$= \sqrt{[220]^2 - [54.9]^2}$$

$$E_{bae} = 213V$$

Recalling Speed control Equation

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}$$

$$\frac{E_{bae}}{E_{bde}} = \frac{N_{ae}}{N_{de}}$$

~~$N_{de} E_{bae} = N_{ae} E_{bde}$~~

$$E_{bde} N_{ae} = E_{bae} N_{de}$$

$$N_{ae} = \frac{E_{bae} N_{de}}{E_{bde}}$$

$$N_{ae} = \frac{213 \times 2000}{220}$$

(i) $N_{ae} = 1936 \text{ rpm}$

(ii) Power factor, $\cos \phi = \frac{E_{bae} + IR}{V} = \frac{213 + 10.5}{220} \text{ var}$

$$\cos \phi = 1.01 \text{ lagging}$$

(iii) Torque developed $T_w = E_{bae} \times I$

$$T_{ae} = \frac{E_{bae} \times I}{\omega}$$

$$\omega = 2\pi n$$

$$T_{ae} = \frac{E_{bae} \times I_L}{2\pi n \times \frac{60}{\text{rpm}}}$$

$$T_{ae} = \frac{213 \times 0.7 \times 2000 \times 60}{2\pi \times 1925 \rightarrow 1936} = 1470 \text{ Nm}$$