

UDOSEN EKEMINI JOHN
17/ENG04/070

GROUP 1

ELECTRICAL/ELECTRONICS ENGINEERING

EEE 326 TEST

Question 3

$f = 50 \text{ Hz}$, $I = 0.7 \text{ A}$, $V = 220 \text{ V}_{DC}$, $R = 15 \Omega$, $L = 0.25 \text{ H}$,
 $N_{dc} = 2000 \text{ rpm}$

Using: $V - E_b = IR \Rightarrow E_b = V - IR$

$$\begin{aligned} E_b(dc) &= 220 - (0.7 \times 15) \\ &= 220 - 10.5 \\ &= 209.5 \text{ V} \end{aligned}$$

$$\begin{aligned} E_b(ac) &= \sqrt{V^2 - [IX_L]^2} - IR \\ &= \sqrt{220^2 - [0.7 \times 15]^2} - (0.7 \times 15) \end{aligned}$$

$$X_L = 2\pi fL = 2\pi \times 50 \times 0.25 = 78.54 \Omega$$

$$\begin{aligned} \therefore E_b(ac) &= \sqrt{220^2 - (0.7 \times 78.54)^2} - (0.7 \times 15) \\ &= 213.02 - 10.5 \\ &= 202.52 \text{ V} \end{aligned}$$

a) Speed of the motor = $\frac{E_{bac}}{E_{bdc}} = \frac{N_{ac}}{N_{dc}}$, Cross multiply and make N_{ac} subject.

$$\therefore N_{ac} = \frac{E_{bac} \times N_{dc}}{E_{bdc}} = \frac{202.52 \times 2000}{209.5} = 1933.4 \text{ rpm}$$

b) Power factor = $\cos \theta$

$$\cos \theta = \frac{IR + E_b(ac)}{V} = \frac{(0.7 \times 15) + 202.52}{220} = \frac{213.02}{220}$$

$$\therefore \text{P.f} = 0.97$$

c) Torque

Recall: $T_{\omega} = E_{bac} \times I \Rightarrow T = \frac{E_{bac} \times I}{\omega}$

where: $\omega = \text{speed in rad/s}$ and $\omega = 2\pi n$ and $n = \text{speed in rev.}$

$$\therefore T_{ac} = \frac{E_{bac} \times I}{2\pi \times \frac{N_{ac}}{60}} = \frac{202.52 \times 0.7 \times 60}{2\pi \times 1933.4}$$

$$\therefore T_{ac} = 0.700 \text{ Nm}$$

d) Universal motor

17/ENG04/070

Question 1

$V = 415V$, $f = 50Hz$, $Pf = 0.7$, Efficiency = 85%, $P = 74.6 kW$
B) (i) Unity = 1

$$C = \frac{kVAR}{2\pi f V^2}$$

$$kVAR = P \times (\tan \text{ actual } Pf + \tan \text{ target } P.f)$$

$$\text{Actual } P.f = \cos \theta = 0.7$$

$$\theta = \cos^{-1} 0.7 = 45.57^\circ$$

$$\tan(45.57) = 1.02$$

$$\text{Target } P.f = \cos \theta = 1$$

$$\theta = \cos^{-1} 1 = 0$$

$$\tan 0 = 0$$

$$C. kVAR = 74.6 \times (1.02 - 0) = 74.6 \times 1.02 = 76.092 \approx 76.1$$

$$C = \frac{76.1}{2\pi \times 50 \times 415^2} = \frac{76.1}{54106079.48} = 1.405 \times 10^{-6} C_{||}$$

H) 0.9 lagging

$$\text{Actual } P.f = 1.02$$

$$\text{target } P.f = \cos \theta = 0.9$$

$$\theta = \cos^{-1}(0.9) = 26.16^\circ$$


$$\tan \theta = \tan 26.16 = 0.48$$

$$kVAR = 74.6 \times (1.02 - (-0.48))$$

$$= 74.6 \times 1.5 = 111.9 \approx 112$$

$$C = \frac{kVAR}{2\pi f V^2} = \frac{112}{2\pi \times 50 \times 415^2} = \frac{112}{13037601} = 8.59 \times 10^{-4} C_{||}$$

c) Phasor diagram

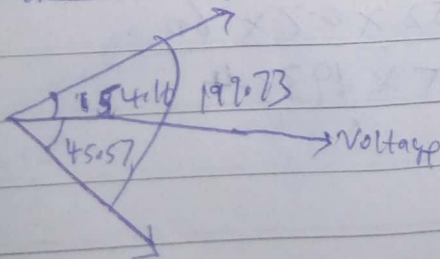

17/ENG04/070


74.6 kW

Question 2

$V = 415 \text{ V}$, No. of pole = 6, $f = 50 \text{ Hz}$, $k = \frac{5}{6} = 0.83$

$R_1 = (0.25 + j0.75) \Omega$ stator

$Z_2 = (1.173 + j0.5) \Omega$ rotor

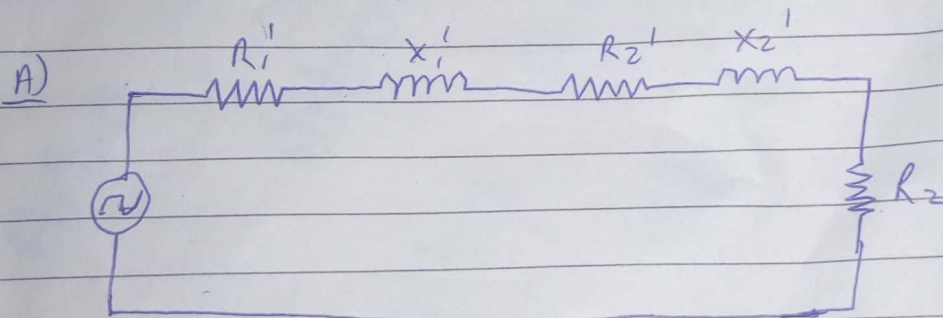

Supply voltage per phase, $V = \frac{415}{\sqrt{3}} = 239.60 \text{ V}$

Referring to rotor

$$R_{02} = (R_2 + k^2 R_1)$$
$$= (1.173 + \left(\frac{5}{6}\right)^2 \times 0.25)$$
$$= 1.347 \Omega$$

$$X_{02} = (X_2 + k^2 X_1)$$
$$= j(0.52 + \left(\frac{5}{6}\right)^2 \times 0.75)$$
$$\approx j1.04$$

$$Z_{02} = R_{02} + jX_{02}$$
$$= 1.347 + j1.041$$

$$= \sqrt{0.347^2 + 1.041^2}$$

$$= 1.07 \Omega //$$

To find rotor current

$$I_2 = \frac{E_2}{Z_{02}}$$

Recall that $E_2 = kV_1$

$$= 239.6 \times 0.83$$

$$= 199.67 \text{ V}$$

$$\therefore I_2 = \frac{199.67}{1.07}$$

$$= 186.6 \text{ A}$$