

17/11/2019/04/046

Elect / Elect

Machines test : Test answered in this order

: Q2, Q3, and Q1

No 2)Question 2

Solution

$$b) \text{ Supply voltage phase } V = \frac{400}{\sqrt{3}} = 230.600$$

the rotor to stator phase voltage ratio $k = \frac{5}{6}$

Equivalent resistance of motor as referred to rotor

$$R_{02} = R_2 + k^2 R_1 = 1.172 + \left(\frac{5}{6}\right)^2 \times 0.25$$

$$= 1.3466 \Omega$$

Equivalent reactance of motor as referred to motor

$$X_{02} = X_2 + k^2 X_1 = 0.52 + \left(\frac{5}{6}\right)^2 \times 0.75$$

$$= 1.0408 \Omega$$

Equivalent rotor impedance

~~$$Z_{01} = \sqrt{(R_1 + k^2 R_2)^2 + (X_1 + k^2 X_2)^2} = \sqrt{1.3466^2 + 1.0408^2}$$~~

$$Z_{02} = \sqrt{(R_{02})^2 + (X_{02})^2}$$

$$= \sqrt{(1.3466)^2 + (1.0408)^2}$$

$$= 1.7019 \Omega$$

①

To find rotor current


$$I_2 = \frac{E_2}{Z_{02}}$$

recall that $E_2 = kV_1$

$$= 239.6 \times 0.85$$

$$= 199.67 \text{ V}$$
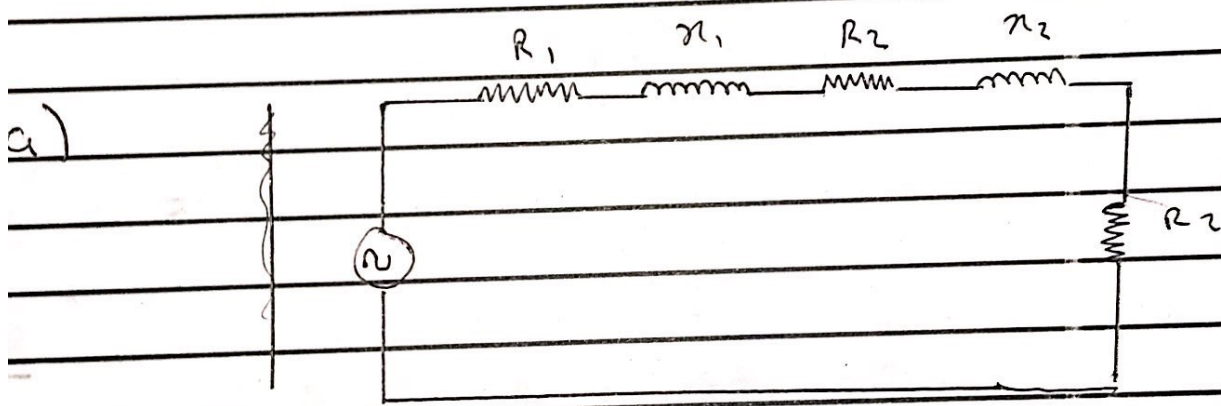
$$\therefore I_2 = \frac{199.69}{1.7} = \underline{\underline{117.45 \text{ A}}}$$



Equivalent circuit diagram referred to the rotor side

Supply voltage = per phase

No. 3

Question 3

$$f = 50 \text{ Hz}$$

$$R = 15 \Omega$$

$$N_s = 2000 \text{ rpm}$$

$$L = 0.25 \text{ H}$$

$$I = 0.7 \text{ A}$$

$$V = 220 \text{ V}$$

(2)

$$E_{dc} = V - IR$$

$$= 220 - (0.7 \times 15)$$

$$= 209.5 \text{ V}$$

$$E_{ac} = \sqrt{V^2 - (I\omega_r)^2} - I\omega_r$$

$$I\omega_r = 0.7 \times 2 \times \pi \times 50 \times 0.25$$

$$= 54.94 \text{ V}$$

$$I\omega = 0.7 \times 15$$

$$= 10.5 \text{ V}$$

$$\therefore E_{ac} = \sqrt{220^2 - 54.94^2} - 10.5$$

$$= 215.02 - 10.5$$

$$= 202.52 \text{ V}$$

1) Speed of motor

remember:
$$\frac{N_{ac}}{N_{dc}} = \frac{E_{ac}}{E_{dc}}$$

$$\frac{N_{ac}}{2000} = \frac{202.52}{209.5}$$

$$N_{ac} = \frac{2000 \times 202.52}{209.5}$$

$$N_{ac} = 1933.37 \text{ RPM}$$

1b) power factor

$$pf = \frac{E + I\omega}{V} = \frac{202.52 + 10.5}{220} = 0.97$$

1c) Torque developed

$$(3) \quad T = \frac{E I}{2\pi n / 60} = \frac{202.52 \times 0.7}{2\pi \times 1933.37 / 60} = 0.7 \text{ Nm}$$

17 (EN1904 1066)

1111) Universal
Synchronous motor - Both AC and DC

No 1

Question 1

Parameters

$$V = 415V \quad 3-\phi \quad 4-wire \quad f = 50Hz, \quad p = 74.6$$
$$pf = 0.7, \quad \text{to } \text{eff} = 85\%$$

b)

1) cond. = 1

$$C = \frac{kVAR}{2\pi f V^2}$$

$$\Rightarrow kVAR = P \times (\tan \text{ actual pf} - \tan \text{ target p.f.})$$

actual p.f. $\Rightarrow \cos \theta = 0.7$

$$\theta = \cos^{-1} 0.7$$
$$= 45.57$$

$$\tan (45.57) = 1.0201$$

Target pf $\Rightarrow \cos \theta = 1$

$$\theta = \cos^{-1} 1 = 0$$

$$\tan 0 = 0$$

$$kVAR = 74.6 \times (1.0201 - 0)$$

$$= 76.0995$$

$$\approx 76.104$$

$$C = \frac{76.10}{2 \times \pi \times 50 \times 415^2}$$

$$= \frac{76.10}{2 \times \pi \times 50 \times 172225}$$

$$= 0.00000422 \quad \approx 4.22 \times 10^{-6} \text{ F}$$

$$\approx 4.22 \times 10^{-6} \mu\text{F}$$

(c)

b) 0.9 (lagging)

$$\text{actual p.f} = 1.0201$$

$$\text{Target p.f} = \cos \theta = -0.9$$

$$\theta = \cos^{-1}(-0.9)$$

$$= 154.16$$

$$\tan \theta = -0.48$$

$$\text{KVAR} = 74.6 \times (1.0201 - (-0.48))$$

$$= 111.90$$

$$\approx 112$$

$$C = \frac{\text{KVAR}}{2\pi f V}$$

$$= \frac{112}{2 \times \pi \times 50 \times 239.60^2}$$

$$= \frac{112}{2 \times \pi \times 50 \times 239.60^2}$$

$$= \frac{112}{2 \times \pi \times 50 \times 239.60^2} = 0.00000621$$

$$= 6.21 \times 10^{-6} \text{ F}$$

Sketch phasor diagram

(i) lagging


$$I_{\text{line}} = \frac{P}{\sqrt{3} V_L \cos \theta}$$

$$I_a = \frac{74500}{\sqrt{3} \times 415 \times 0.7} = 148.06 \text{ A}$$

$$V_f = \frac{V_L}{\sqrt{3}} = \frac{415}{\sqrt{3}} = 239.60$$

(3)


$E_{fph} = \vec{V}_{tph} + I_a X_a$

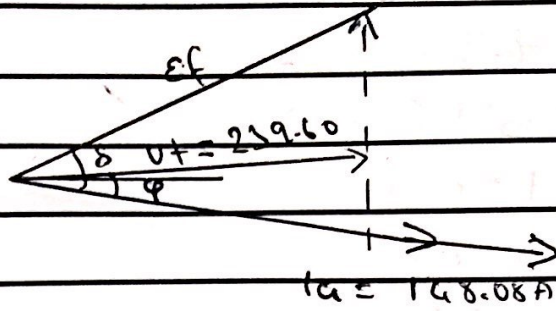



Phasor diagram
for lagging
 $E_f > V_t$ &
 δ positive.

1a) Identify the drive motor type:

ANS: three phase induction motor

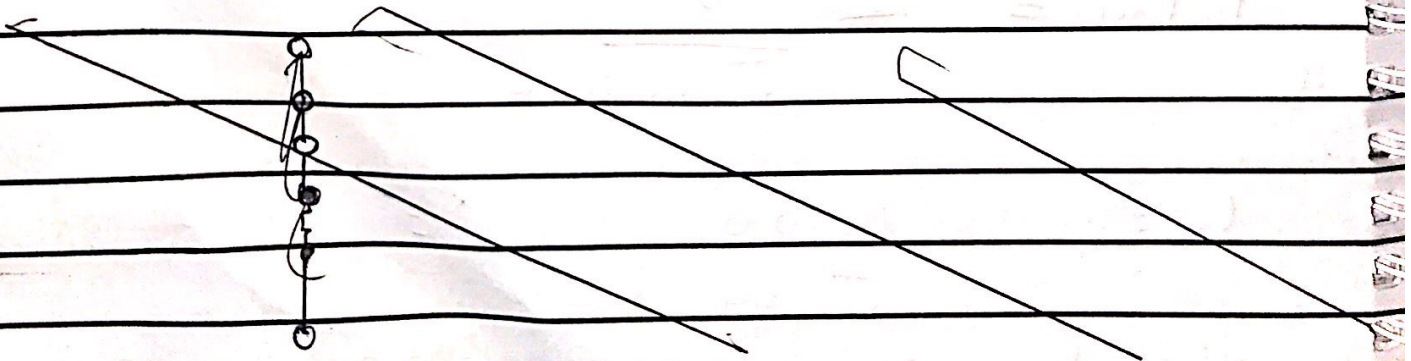

(6)

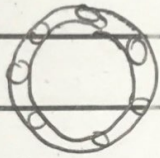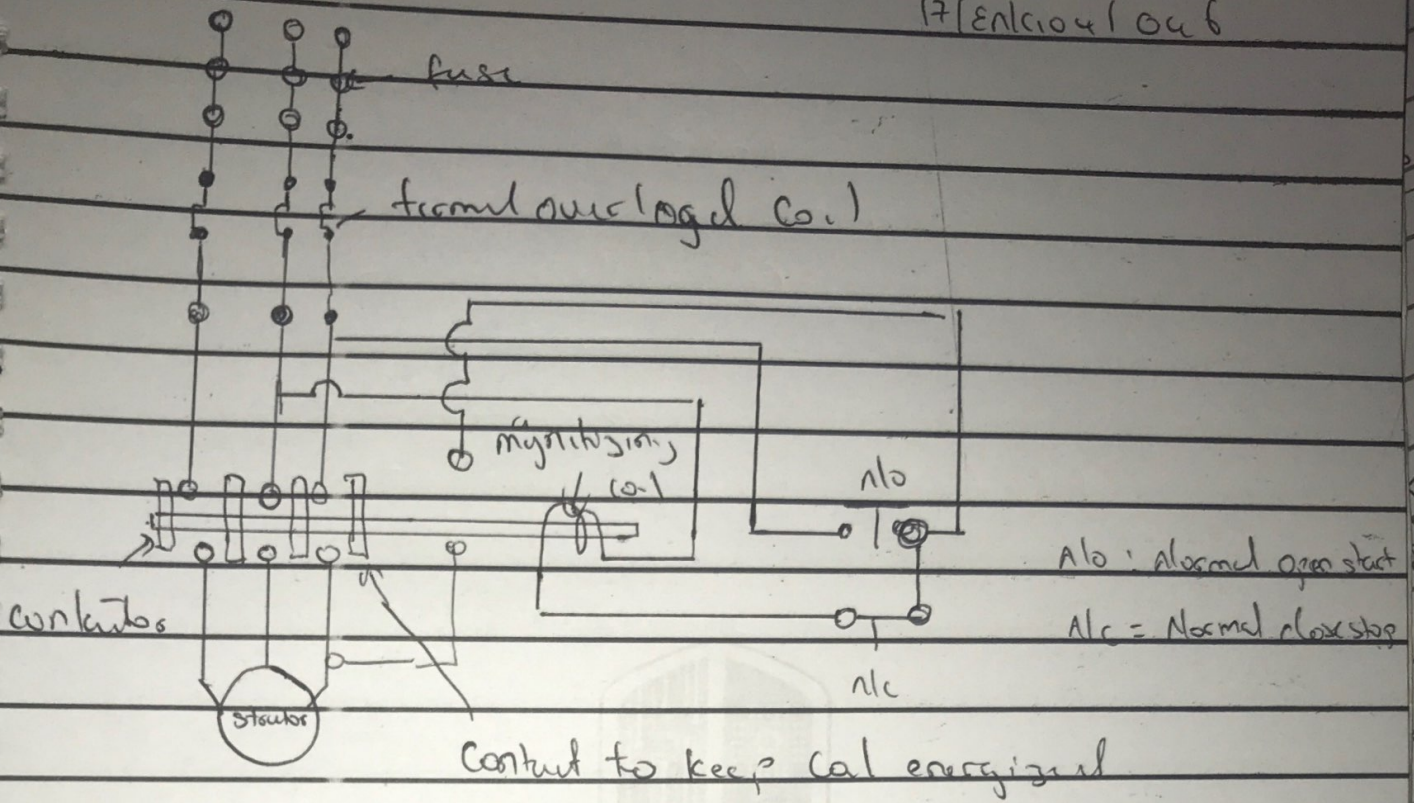

Sketch of three phase motor with direct online starter