

Scanned Documents

①

MARK NO: 17ENG06/003 ADAM EMMANUEL
 DEPARTMENT: MECHANICAL ENGINEERING
 LEVEL: 300 LEVEL

Question 3

$f_s = 50\text{Hz}$, $N = 2000\text{rpm}$, $\phi = 0.18$, $V_s = 220\text{V}$, $R = 15\Omega$, $X = 0.25\Omega$

(a) Speed of the motor?

$E_b = V - IR$
 $= 220 - (0.18 \times 15)$
 $= 209.5\text{V}$

$E_{ac} = \sqrt{V^2 - (IX)^2} - IR$
 $E_{ac} = \sqrt{220^2 - (15)^2} - 15$
 $IX = 0.18 \times 2 \times 3.14 \times 50 \times 0.25$
 $= 54.9\text{V}$
 $IR = 0.18 \times 15 = 10.5\text{V}$

$E_{ac} = \sqrt{220^2 - 54.9^2} - 10.5$
 $= \sqrt{48377.1946} - 10.5$
 $= 219.92 - 10.5$
 $= 209.52\text{V}$

Speed of motor

Result $\frac{N_{ac}}{N_{bc}} = \frac{E_{ac}}{E_{bc}}$

$\frac{N_{ac}}{2000} = \frac{209.52}{209.5}$

$\therefore N_{ac} = \frac{209.52 \times 2000}{209.5} = 1995.37\text{rpm}$

$N_{ac} = 1995.37\text{rpm}$

②

ADAH EMMANUEL

17/ENG061002

② TWO LEVEL MECHANICAL ENGF.

3b) The power factor of the motor

$$\text{Power factor} = \cos \phi = \frac{E_b I_a + I_a^2 R_a}{V}$$

$$\text{Power factor} = \frac{202.52 + 10.5}{220} = 0.968$$

220

$$\text{ans} = \underline{0.968} \text{ lagging}$$

c) Torque developed $T_{dev} = \frac{E_b I_a}{\omega}$ ω where: I_a = current in Amps ω = Angular velocity in rad/s \rightarrow Recall that $\omega = 2\pi n$

$$T_{dev} = \frac{E_b I_a}{2\pi \times \frac{N_s}{60}}$$

$$2\pi \times \frac{N_s}{60}$$

60

$$\therefore T_{dev} = \frac{E_b I_a \times 60}{2\pi \times N_s}$$

$$T_{dev} = \frac{202.52 \times 0.7 \times 60}{2\pi \times 1935.37}$$

$$T_{dev} = \frac{8505.84}{12147.72198}$$

$$\therefore T_{dev} = 0.7002004175 \text{ Nm}$$

$$T_{dev} = \underline{0.700 \text{ Nm}}$$

d) The universal motor type can be used in this application

3

MATRIC NO: 17120101008 ADAM Emmanuel

DEPARTMENT: MECHANICAL ENGINEERING

LEVEL: 200

Question 2

$V = 415\text{V}$


no. of pole = 6

$f = 50\text{Hz}$

$k = \frac{5}{6} = 0.833$

$Z_1 = 0.25 + j0.15$

$Z_2 = 1.173 + j0.52$

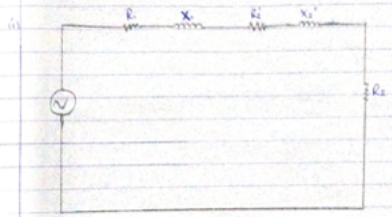

the supply voltage per phase, $V = \frac{415}{\sqrt{3}} = 239.6003611\text{V}$
 $V = 239.6\text{V}$

$R_{02} = (R_2 + k^2 R_1)$
 $R_{02} = (1.173 + (0.6)^2 \times 0.25)$
 $R_{02} = 1.173 + 0.1736$
 $R_{02} = 1.347\Omega$

$X_{02} = (X_2 + k^2 X_1)$
 $= j [0.52 + (0.6)^2 \times 0.15]$
 $= j (0.52 + 0.5208)$

(4)

ALAH EMMANUEL

MECHANICAL ENGINEERING 17/ENGG061002 300 LEVEL

$$X_{02} = 1.041j$$

$$Z_{02} = \sqrt{(R_{02})^2 + (X_{02})^2}$$

$$Z_{02} = \sqrt{1.81^2 + j1.041^2}$$

$$Z_{02} = \sqrt{3.47689} = 1.82 \text{ } \underline{1.70 \Omega}$$

$$Z_{02} = \underline{1.70 \Omega}$$

ii) To Find current:

$$I_2 = \frac{E_2}{Z_{02}}$$

Recall that $E_2 = K V_1$

$$E_2 = 0.83 \times 239.6$$

$$E_2 = 199.67 \text{ V}$$

$$\text{Therefore } I_2 = \frac{199.67}{1.70} = 117.4529412$$

$$\therefore I_2 = \underline{117.45 \text{ A}}$$

5

MATHS NO: 1710404002 ACAM CONDRIEL

DEPARTMENT: MECHANICAL ENR

LEVEL: 200

29.05.2021

Question 1

$v = 150$, $b = 1$, 4×10^4 , $f = 200$, $S = 746$
 Plane film = 0.1, surface = 90%

Work 1

Cs KVAR

 $221V^2$ $\rightarrow KVAR = P \times (\cos \theta_{actual} - \cos \theta_{target})$ actual pf = 0.7 $\cos \theta = 0.7$ $\theta = \cos^{-1}(0.7) = 45.57^\circ$ $\sin (45.57^\circ) = 0.7161$ target pf = 1 $\cos \theta = 1$ $\theta = \cos^{-1}(1) = 0^\circ$ $\sin 0 = 0$

KVAR = 74.6 x C (1.0201 - 0)

KVAR = 76.09016

KVAR is 76.10

C = 76.10

 $28 \times 30 \times 45^2$ C = $\frac{76.10}{5410609.44} = 1.406 \times 10^{-6} C$ 5410609.44

C = 0.0000014

n 0.9 lagging

actual pf = 1.0201

target pf = $\cos \theta = 0.9$

6
ADAH EMMANUEL

MECHANICAL ENGR. 17/ENG 06/001 300LEVEL

$$\theta = \cos^{-1}(0.9)$$

$$= 154.16$$

$$\cos \theta = -0.48$$

$$K_{VAR} = 74.6 \times (1.0201 - (-0.48))$$

$$K_{VAR} = 74.6 \times (1.0201 + 0.48)$$

$$K_{VAR} = 111.90$$

$$K_{VAR} \approx 112.0$$

$$C = \frac{K_{VAR}}{2\pi f^2} = \frac{112}{2\pi \times 50 \times 415^2} = \frac{112}{54106079.48}$$

$$C = \frac{0.00086}{\underline{\underline{2}}} \approx \underline{\underline{8.6 \times 10^{-4} C}}$$