

17/Elec/1012: Elec/Elect Engineering 3rd Level  
Question 2

25 hp

$$V_{line} = 415V$$

pole = 6-pole

f = 50 Hz

3-phase induction motor


$$V_{pk} = \frac{415}{\sqrt{3}} = 239.6V$$

$$Z_s = (0.25 + j0.75)$$

$$Z_r = 1.75 + j0.52$$

Solution

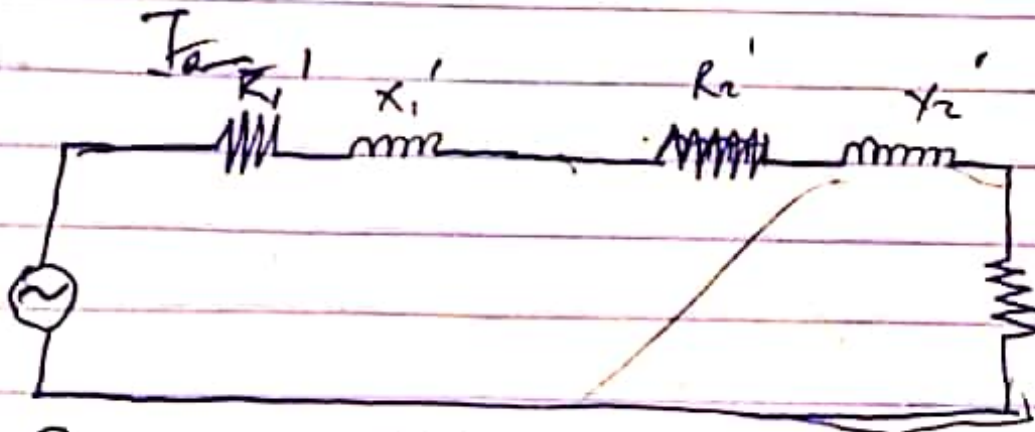Equivalent Circuit Diagram referred to the rotor side



Supply per Voltage per phase

$$V_{ph} = \frac{V_{line}}{\sqrt{3}} = \frac{415}{\sqrt{3}} = 239.6V$$

## Question 2

17/ENG04102 Elect/Elect Eng 3rd level

Referring to rotor

$$R_{02} = (R_2 + k^2 R_1)$$

$$= (1.175 + (5/6)^2 \times 0.25)$$

$$R_{02} = \cancel{1.3475} \quad 1.858 \quad 1.347 \Omega$$

$$X_{02} = (X_2 + k^2 X_1)$$

$$= j(0.52 + (5/6)^2 \times 0.75)$$

$$= \cancel{1.041} \quad j \times 1.858$$

$$= 1.041$$

$$Z_{02} = (R_{02} + jX_{02})$$

$$Z_{02} = R_{02} + jX_{02}$$

$$= 1.347 + j1.041$$

$$= \sqrt{(1.347)^2 + (1.041)^2}$$

$$= 1.7 \Omega$$

To find rotor current

$$I_2 = \frac{E_2}{Z_{02}}$$

Result that  $E_2 = kV_1$

$$= 289.6 \times 0.7$$

$$= 199.67 \text{ V}$$

$$\therefore I_2 = \frac{199.67}{1.7} = 117.45 \text{ A}$$

## Question 2

$$V = 415V, \quad \phi = 0, \quad 4\text{-wire}, \quad f = 60\text{Hz}, \quad P = 97.6\text{KW}$$

$$P_f = 0.9, \quad \text{to} \rightarrow \text{Efficiency} = 88\% = 0.88$$

Capacitors per phase of a mesh - Connected  
 necessary to raise the power factor  
 to

Solution

$$(1) \quad \text{Unity} = 1$$

$$C = \frac{\text{KVAR}}{2\pi f V^2}$$

$$V_{ph} = \frac{V_{line}}{\sqrt{3}} = \frac{415}{\sqrt{3}}$$

$$= 239.6$$

$$\text{KVAR} = P \times (\tan \text{ actual } P.f - \tan \text{ target } P.f)$$

$$\text{actual } P.f \Rightarrow \cos \phi = 0.9$$

$$\theta = \cos^{-1} 0.9$$

$$= 45.57$$

$$\tan (45.57) = 1.0204$$

$$\text{target } P.f \Rightarrow \cos \phi = 1$$

$$\theta = \cos^{-1} 1$$

$$= 0$$



Question 1

$$kVAR = 74.6 \times (1.0201 - 0)$$

$$= 76.10$$

$$C = 76.10$$

$$2 \times \pi \times 50 \times \cancel{239.6}$$

$$= 6.00006422$$

$$= \cancel{1.4 \times 10^{-5}} \quad 42.2 \times 10^{-6} \text{ C}$$

ii) 0.9 lagging

actual p.f = 1.0201

target p.f  $\Rightarrow \cos \theta = -0.9$

$$\theta = \cos^{-1} 0.9$$

$$= 154.16$$

$$\tan \theta = -0.48$$

$$kVAR = 74.6 \times (1.0201 - (-0.48))$$

$$= 111.90$$

$$\approx 112$$

$$C = \frac{kVAR}{2\pi f V^2} = \frac{112}{2\pi \times 50 \times \cancel{239.6^2}}$$

$$= 0.00062$$

$$\approx 6.2 \times 10^{-4} \text{ F}$$

B.2

## Question 3


$$k_f = 0.2517$$

$$f = 50 \text{ Hz}$$

$$N_s = 2000 \text{ rpm}$$

$$V = 220 \text{ V DC}$$

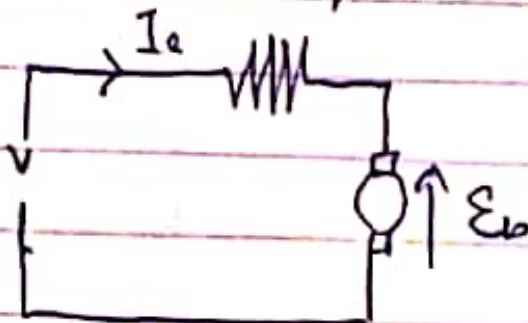DC Supply  
Voltage = 220 V  
Current drawn  $I = 0.7 \text{ A}$



$$V - E_b = I_a R$$

$$V - [I_a R] = E_b$$

$$E_b = 220 - [0.7 \times 15]$$

$$= 209.5 \text{ V}$$

1) Speed on DC  
 $N_{DC} = 2000 \text{ rpm}$

# Question 3

17/0004/012 /N2

Elect/Elect Eng

3m L

Ac supply


$$\text{Supply Voltage} = 220\text{V}$$

$$\text{Current drawn} = I_L = 0.7$$

$$\begin{aligned} \text{Resistance Drop} &= I_L \times R = 0.7 \times 15 \\ &= 10.5\text{V} \end{aligned}$$

$$\begin{aligned} \text{Reactance Voltage drop} &= I_L \times X_L \\ &= 0.7 \times 2\pi f L \end{aligned}$$
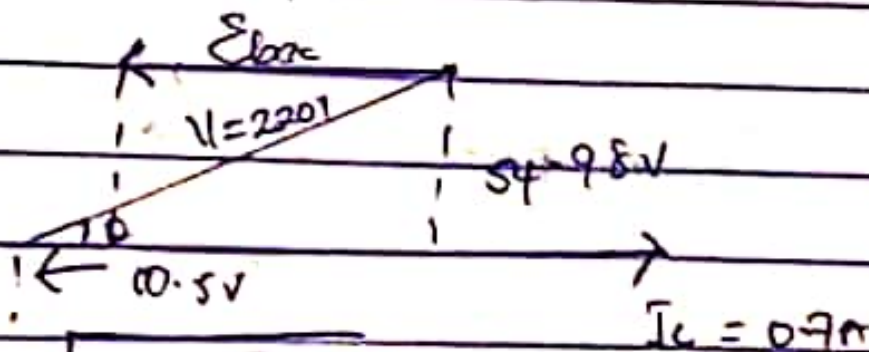
$$\begin{aligned} \text{Where } X_L &= \omega L = 2\pi f L \\ &= 0.7 \times 2\pi \times 50 \times 0.25 \\ &= 54.98\text{V} \end{aligned}$$



$$\begin{aligned} E_{t,ac} &= \sqrt{V^2 - [X_L]^2} - IR \\ &= \sqrt{(220)^2 - (54.98)^2} - 10.5\text{V} \\ &= \sqrt{45397.1996} - 10.5 \\ &= 213.019 - 10.5 \\ &= 202.519 \\ &= 202.52\text{V} \end{aligned}$$



## Question 3

Recall speed that

$$\frac{N_2}{N} = \frac{E_{b2}}{E_{b1}}$$

$$\text{So, } \frac{E_{bac}}{E_{bac}} = \frac{N_{ac}}{N_{ac}}$$

$$N_{ac} = N_{ac} \times \frac{E_{bac}}{E_{bdc}}$$

$$= 2000 \times \frac{202.52\text{V}}{209.5\text{V}}$$

$$N_{ac} = 1933.37 \text{ rpm}$$

(ii) Power factor,  $\cos \phi$

$$\cos \phi = \frac{E_{bac} + I_a}{V}$$

$$= \frac{202.52 + 10}{220}$$

$$= 0.968 \text{ lagging}$$

(iii) Torque developed by the motor

$$T_{wo} = E_{bac} \times I_a$$

## Question 3

$$T_{ac} = \frac{E_{bac} \times I}{\omega}$$

$\omega$  is speed in rad/s

$$\omega = 2\pi n, \text{ where } n \text{ is speed in rev/s}$$

$$T_{ac} = \frac{E_{bac} \times I_c}{2\pi \times \text{NAC}} \times 60$$

$$= \frac{200.52 \times 0.7 \times 0.6}{2\pi \times 1733.57}$$

$$= 0.700 \text{ Nm}$$

w) What type of motor could be used for this application?

Universal motor