

Tungo Kelm
18 Aug 2018
300L

Back speed constant equation

$$\frac{n_s}{2\pi} = \frac{E_b}{E_s}$$

$$\text{So } E_{ba} = \frac{n_s}{n} E_s$$

Making n the subject of the formula

$$n_s = n \frac{E_b + E_{ba}}{E_s}$$

$$= 2000 + \frac{202.52 V}{209.5 V}$$

$$n_s = 1933.37 \text{ rpm}$$

Power factor $\cos \phi = \frac{E_{ba} + I R}{V}$

$$= \frac{202.52 + 10}{220}$$

$$= 0.965 \text{ lag}$$

Torque develop $\tau_w = S_{sc} + I$

Back speed = constant equation

$$\tau_{sc} = \frac{E_{ba} + I R}{\omega}$$

where ω is speed in rad/s

$\omega = 2\pi n$, about ω as in rev/s

$$\tau_{sc} = \frac{E_{ba} + I R}{2\pi + \frac{n_s}{60}}$$

$$= \frac{202.52 + 0.7 + 60}{2\pi \times 1933.37}$$

$$= 0.700 \text{ Nm}$$

19/08/2018
 TMSD Kilm. Abgama
 300h

Question 2

$$V_s = 415 \text{ V}$$


$$U_p \text{ of poles} = 6$$

$$f = 50 \text{ Hz}$$

$$k = \frac{5}{6} = 0.83$$

$$Z_1 = 2 = 0.25 + j0.75 \quad \dots \text{ stator}$$
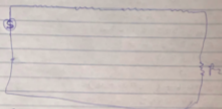
$$Z_2 = 1.173 + j0.52 \quad \dots \text{ rotor}$$



Supply Voltage per phase $U_2 = \frac{415}{\sqrt{3}} = 239.60 \text{ V}$

Referring to rotor

$$R_{02} = (R_1 + k^2 R_2)$$

$$= (0.25 + (0.83)^2 \times 1.173)$$

$$R_{02} = 1.347 \Omega$$

$$X_{02} = (X_1 + k^2 X_2)$$

$$= j(0.75 + (0.83)^2 \times 0.52)$$

$$= j1.041$$

$$Z_{02} = R_{02} + jX_{02}$$

$$= 1.347 + j1.041$$

$$= \sqrt{1.347^2 + 1.041^2}$$

$$= 1.72 \Omega$$

∴ find rotor current

$$I_2 = \frac{U_2}{Z_{02}}$$

Power fact $(\cos \phi_2 = R_{02} / Z_{02})$

$$= \frac{239.6}{1.72}$$

$$= 139.67 \text{ A}$$

$$I_2 \cos \phi_2 = \frac{139.67}{1.72} = 81.45 \text{ A}$$

Name: Tareq Kaban ABUJAWA


Level: 300L

① $f = 60 \text{ Hz}$, $V_{AC} = 220 \text{ V}$, $V_E = 220 \text{ V}$, $v = 220 \text{ V}$, $R = 15 \Omega$
 $I = 0.7 \text{ A}$

on DC Supply.

Supply voltage = 220 V

Current draw $I = 0.7 \text{ A}$

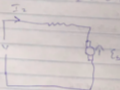

$$V = E_b + I \times R$$

$$V - [I \times R] = E_b$$

$$E_b = 220 - [0.7 \times 15]$$

$$= 209.5 \text{ V}$$

Speed on DC

$$N_{DC} = 2000 \text{ rpm}$$

on AC Supply

Supply voltage = 220 V

Current draw, $I = 0.7 \text{ A}$


Resistor drop = $I \times R = 0.7 \times 15 = 10.5 \text{ V}$

Rectifier voltage drop = $I \times r_f = 0.7 \times 28 = 19.6 \text{ V}$

where $r_f = 28 \text{ m}\Omega$

$$= 0.7 \times 28 + 50 + 0.25$$

$$= 64.98 \text{ V}$$

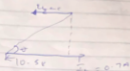

$$E_{bac} = \sqrt{V^2 - (I \times R)^2} - I \times R$$

$$= \sqrt{(220)^2 - (10.5)^2} - 10.5 \text{ V}$$

$$= 202.82 \text{ V}$$

Tugas Kelen

Aljabar

18/engob1078

3006

Quesion

① $v = 415v$, $3-\phi$, 4 $\omega = 50\text{Hz}$
 $P = 74.0$, $P.F = 0.7$, $\text{eff} = 85\%$

$\omega =$

$$C = \frac{KVAR}{2\pi fV^2}$$

$KVAR = P \tan(\theta - \text{actual P.F.})$

$$\text{actual P.F.} = \cos \theta = 0.7$$

$$\theta = \cos^{-1} 0.7$$

$$= 45.57$$

$$\tan(45.57) = 1.0201$$

$$\text{lag P.F.} \Rightarrow \cos \theta = 1$$

$$\theta = \cos^{-1} 1 = 0$$

$$\tan \theta = 0$$

$$KVAR = 74.6 + (1.0201 - 0)$$

$$= 76.0995$$

$$= 76.1$$

$$C = \frac{7610}{2\pi \times 50 \times 415^2} = 1.4 \times 10^{-6} \text{ F}$$

⑩ 0.9 lagging

$$\text{actual P.F.} = 1.0201$$

$$\text{lagging P.F.} = \cos \theta = 0.9$$

$$\theta = \cos^{-1}(0.9)$$

$$\theta = 26.106^\circ$$

$$\tan \theta = \tan(26.106^\circ)$$

$$= 0.48$$

$$KVAR = 74.6 + (1.0201 - 0.48) \times 74.6$$

$$= 111.90$$

$$= 112$$

$$C = \frac{KVAR}{2\pi fV^2} = \frac{112}{2\pi \times 50 \times 415^2}$$

$$= 2.069 \times 10^{-6} \text{ F}$$

$$= 2.069 \mu\text{F}$$