

MATRIC NO: 19/ERG06/002

DEPARTMENT: MECHANICAL ENGR.

COURSES: ELECTRICAL MACHINES (EEE 326)

LEVEL: 3RD L

(1)

$$\sqrt{V} = 415V$$

Induction motor = 3-phase

$$f = 50 \text{ Hz}$$

$$\text{Power} = 74.6$$

$$P.F = 0.7$$

$$\text{Efficiency} = 85\%$$

i) Unity & slip = 1

$$C = \frac{kVAr}{2\pi f V^2}$$

$$kVAr = P \times (\tan \theta \text{ of the actual P.F.} - \tan \theta \text{ target P.F.})$$

$$\text{To get actual P.F.} = \cos \theta = 0.7$$

$$\theta = \cos^{-1}(0.7)$$

$$= 45.57^\circ$$

$$\tan(45.57^\circ) = 1.0201$$

$$\text{For the target P.F.} = \cos \theta = 1$$

$$\theta = \cos^{-1}(1) = 0^\circ$$

$$\tan 0^\circ = 0$$

$$kVAr = 74.6 \times (1.0201 - 0)$$

$$= 76.0995$$

$$\approx 76.10$$

$$\therefore C = \frac{76.10}{2\pi \times 50 \times 415^2}$$

$$\approx 0.0000014$$

$$C = 1.4 \times 10^{-6} \text{ C}$$

① contd

17/EMG06/002

ii) 0.9 Lagging

$$\text{Actual P.F} = 1.0201$$

$$\text{Target P.F} = \cos \theta = -0.9$$

$$\theta = \cos^{-1}(-0.9)$$

$$\theta = 154.16^\circ$$

$$\tan \theta = -0.48$$

$$kVAR = 74.6 \times (1.0201 - (-0.48))$$

$$\approx 111.90$$

$$\approx 112$$

$$C = \frac{kVAR}{2\pi f V^2}$$

$$\begin{aligned} &= \frac{112}{2\pi \times 50 \times 415^2} \\ &= 2.068 \times 10^{-6} \text{ F} \end{aligned}$$

$$= \frac{112}{2\pi \times 50 \times \left(\frac{415}{\sqrt{3}}\right)^2}$$


$$\approx 6.21 \times 10^{-6} \text{ F}$$

MATRIC NO: 17/ENG06/002

DEPARTMENT: MECHANICAL ENGR.

COURSE: ELECTRICAL MACHINES (EEE 826)

LEVEL: 300L

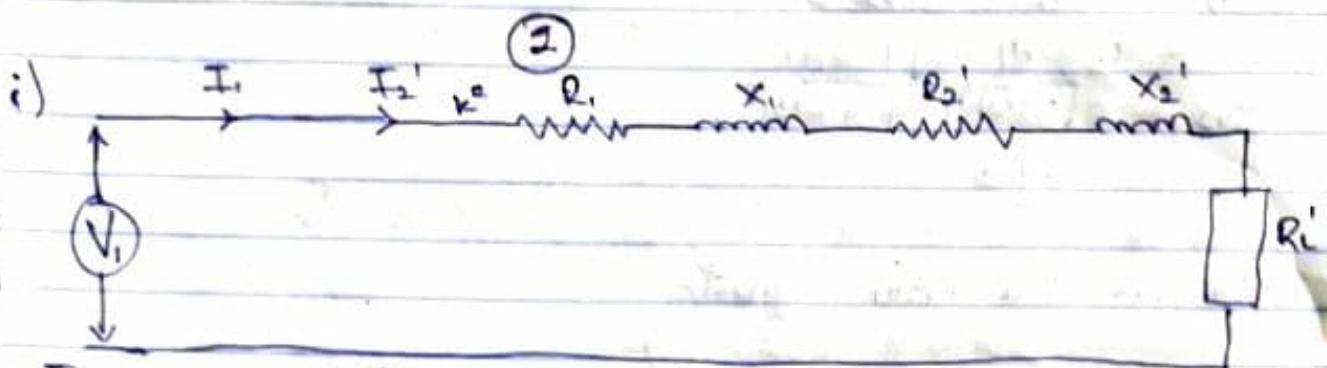

For version 2: You ignore the core, $\therefore I_1 = I_2'$

$$V_{line} = 415V$$

$$\text{No of Poles} = 6\text{-poles}$$

$$k = 6/5 = 1.2$$

$$R_1 = 0.25\Omega$$

$$X_1 = 0.75\Omega$$

$$R_2' = 1.173\Omega$$

$$X_2' = 0.52\Omega$$

$$\text{Frequency} = 50\text{Hz}$$

$$Z_1 = 0.25 + j0.75$$

$$Z_2 = 1.173 + j0.52$$

$$Cl.p = \frac{N_s - N_1}{N_s}$$

$$N_s = \frac{120f}{P} = \frac{120 \times 50}{6}$$

$$N_s = 1000\text{ rpm}$$

$$\text{Supply Voltage per phase}, V = \frac{415}{\sqrt{3}} = 239.50V$$

Referring to rotor,

$$R_{D2}' = (R_2 + k^2 R_1)$$

$$= 1.173 + (5/6)^2 \times 0.25$$

$$R_{D2}' = 1.347\Omega$$

$$X_{D2}' = (X_2 + k^2 X_1)$$

17/ENIAC06/0002

(2) control

$$\approx j (0.52 + \left(\frac{s}{b}\right)^2 \times 0.75)$$
$$= 1.041$$

$$Z_{02} = R_{02} + jX_{02}$$

$$= 1.347 + j1.041$$

$$Z_{02} = \sqrt{1.347^2 + 1.041^2}$$
$$= 1.7\Omega$$

To get the rotor current

$$I_2 = \frac{E_2}{Z_{02}}$$

Recall that $E_2 = kN\phi$

$$= 239.6 \times 0.83$$

$$= 199.67$$

$$\therefore I_2 = \frac{199.67}{1.7}$$

$$= 117.45A$$

(3)


17/EN/AD6/002

$$f = 50 \text{ Hz}, \text{Power} = 1 \text{ kW}, N = 2000 \text{ rpm}$$

$$V = 220 \text{ V}, R_L = 15 \Omega, X_L = 0.25 \Omega$$

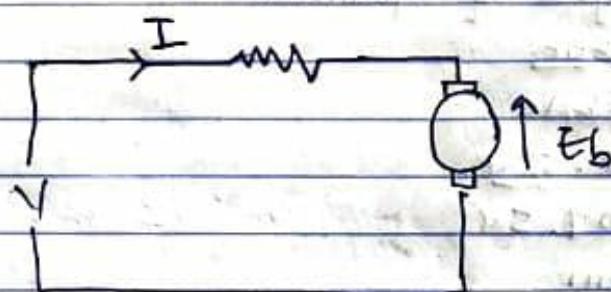i) On DC supply

Supply voltage = 220 V
currents, $I = 0.7 \text{ A}$



$$V - E_b = I_L \times R$$

$$V - (I_L R) = E_b$$

$$E_b = 220 - (0.7 \times 15)$$

$$= 209.5 \text{ V}$$

Speed for DC, $N = 2000 \text{ rpm}$


On AC supply, supply voltage = 220 V

Current, $I_c = 0.7 \text{ A}$

$$\text{Reactance drop} = 0.7 \times 15 = 10.5 \text{ V}$$

$$\text{Reactance voltage drop} = 0.7 \times 2 \times 50 \times 0.25$$

$$= 54.98$$

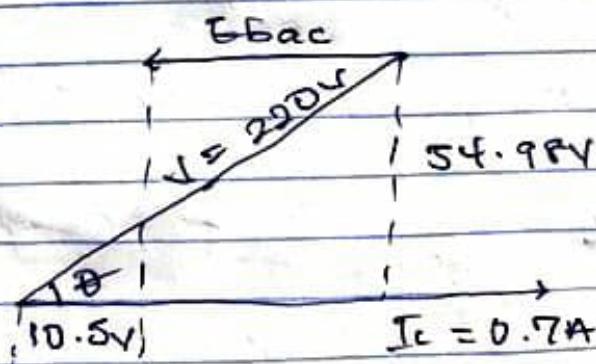

$$E_{bac} = \sqrt{V^2 - (X_L)^2} - IR$$

$$= \sqrt{220^2 - (54.98)^2} - 10.5$$

③ contd

17 | ENGD6 | 002

$$= 202.52V$$

Recall, $\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}$

$$\therefore \frac{E_{bac}}{E_{bdc}} = \frac{N_{ac}}{N_{dc}}$$

Noting N_{ac} the subject of formula

$$N_{ac} = N_{dc} \times \frac{E_{bac}}{E_{bdc}}$$

$$= 2000 \times \frac{202.52V}{209.54}$$

$$= 19.33.37 \text{ rpm}$$

$$P.F = \cos \phi = \frac{E_{bac} + IR}{V}$$

$$= \frac{202.52 + 10.5}{220}$$

$$= 0.968 \text{ (Lagging)}$$

The torque developed,

$$T_w = E_{bac} \times I$$

$$T_{ac} = \frac{E_{bac} \times I}{\omega}$$

where ω is speed in rad/s

$$\omega = 2\pi N$$

where N is speed in rev/min

$$T_{ac} = \frac{E_{bac} \times I_c}{2\pi \times N_{ac}}$$

$$= \frac{202.52 \times 0.7 \times 60}{2\pi \times 1933.37}$$

$$= 0.700 \text{ Nm}$$