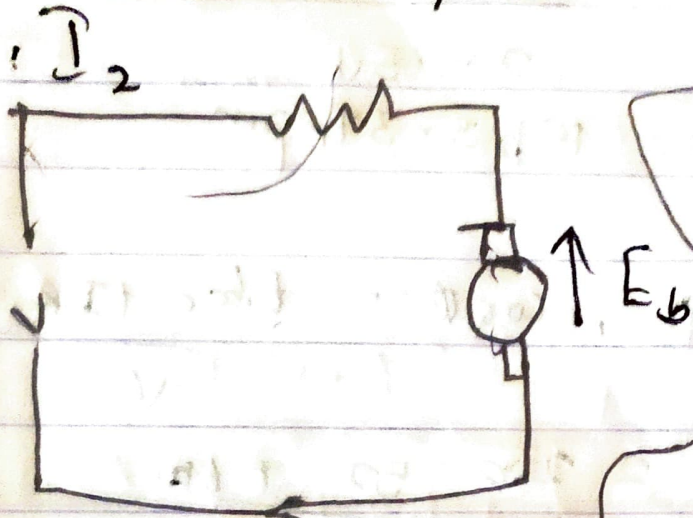


Adepoju Adeshina Adejusun  
1711EN606/003 Mechanical

3. On DC supply, Supply voltage = 220V  
Current draws,  $I = 0.7A$



On AC supply, supply voltage = 220V  
 $I = 0.7A$   
Reactance =  $0.7 \times 15 = 10.5V$

Reactance voltage =  $I \times X_L$   
 $= 0.7 \times 28$   
where  $X_L = \omega L = 2\pi fL$   
 $= 0.7 \times 28 \times 50 \times 0.25$   
 $= 54.98V$

$$V - E_b = I_2 \times R$$

$$V - [I_2 \times R] = E_b$$

$$E_b = 220 - [0.7 \times 15]$$

$$= 209.5V$$

Speed on DC

$$N_{dc} = 2000 \text{ rpm}$$

Recall Speed - Constants equation

$$\frac{N_2}{N_1} = \frac{E_b}{E_{b1}}$$

$$\therefore \frac{E_{bac}}{E_{bdc}} = \frac{N_{ac}}{N_{dc}}$$

$$E_{bac} = \sqrt{V^2 - (I \times R)^2}$$

$$= \sqrt{220^2 - (10.5)^2}$$

$$= 202.52V$$



3 (i) making  $N_{ac}$  subject of the formula

$$N_{ac} = \frac{E_{bac}}{E_{dc}}$$

$$= 2000 \times \frac{202.52V}{209.5V}$$

$$N_{ac} = 1933.37 \text{ rpm}$$

(ii) Power factor,  $\cos \phi = \frac{E_{bac}}{E_{dc}}$

$$= \frac{202.52}{209.5}$$

$$= 0.966$$

(iii) Torque developed

17/ENG006/003

Question 2

$$V_{line} = 415V$$

No of poles = 6

$$f = 50Hz$$

$$k = \frac{5}{6} = 0.83$$

$$Z_1 = 0.25 + j0.75 \quad \text{--- stator}$$

$$Z_2 = 1.173 + j0.52 \quad \text{--- rotor}$$

Supply voltage per phase  $\therefore V = \frac{415}{\sqrt{3}}$

$$= 239.604$$

Referring to rotor

$$R_{02} = (R_2 + k^2 R_1)$$



WINDING LOSS

$$(1.173 + \left(\frac{5}{6}\right)^2 \times 0.25)$$

$$R_{02} = 1.347 \Omega$$

$$X_{02} = (X_2 + K^2 X_1)$$

$$= j(0.52 + \left(\frac{5}{6}\right) \times 0.78)$$

$$= 1.041 \Omega$$

$$Z_{02} = R_{02} + jX_{02}$$

$$= 1.347 + j1.041$$

$$Z_{02} = \sqrt{1.347^2 + 1.041^2}$$

$$= 1.7 \Omega$$

To find rotor current


$$I_2 = \frac{E_2}{Z_{02}}$$

Recall that  $E_2 = K V_1$

$$2239.6 \times 0.85$$

$$I_2 = \frac{199.67}{1.7} = 117.45 \text{ A}$$

2. Equivalent circuit diagram

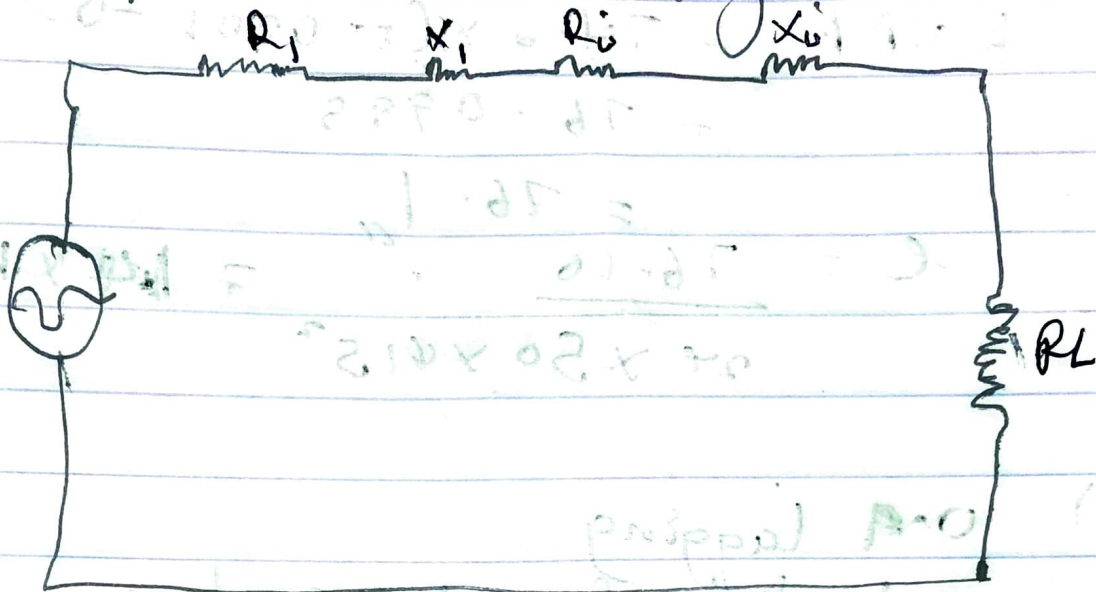

Question 1:

$$\text{unity} = 1$$

$$C = \frac{Q}{2\pi f V^2}$$

$$kVAR = P \times C$$

$$\text{actual P.F.} = \cos \theta = 0.7$$

$$\theta = \cos^{-1} 0.7$$

$$= 45.57^\circ$$

$$\tan (45.57^\circ) = 1.0201$$

$$\text{tangent P.F.} = \cos \theta = 1$$

$$\theta = \cos^{-1} 1 = 0$$

$$\tan 0 = 0$$



$$KVAR = 74.6 \times (1.0201 - 1)$$

$$= 76.0995$$

$$\approx 76.1 \text{ "}$$

$$e = \frac{76.10}{2\pi \times 50 \times 415^2} = 1.44 \times 10^{-6} \text{ "}$$

(A)

0.9 lagging

actual p.f = 1.0201

target p.f =  $\cos \theta = 0.9$

$$\theta = \cos^{-1}(0.9)$$

$$\theta = 154.16$$

$$\tan \theta = \tan (154.16)$$

$$= -0.48$$

$$KVAR = 74.6 \times (1.0201 - (0.948))$$

$$= 111.90$$

$$\approx 112 \text{ "}$$

$$e = \frac{KVAR}{2\pi f V^2} = \frac{112}{2\pi \times 50 \times 415^2}$$

$$= 2.068 \times 10^{-6} \text{ "}$$