

1) Unity = 1

$$C = \frac{KVAR}{2\pi f v^2}$$

$$KVAR = P \times (\tan \text{ actual pf} - \tan \text{ target pf})$$

$$\text{actual pf} = \cos \phi = 0.7$$

$$\phi = \cos^{-1} 0.7 = 45.57 \Rightarrow \tan(45.57) = 1.0201$$

$$\text{target pf} = \cos \phi = 1 \Rightarrow \phi = \cos^{-1}(1) = 0$$

$$\tan 0 = 0$$

$$KVAR = 74.6 \times (1.0201 - 0)$$

$$= 76.0995 \approx 76.1$$

$$C = \frac{76.10}{2 \times \pi \times 50 \times \left(\frac{415^2}{\sqrt{3}}\right)} = 4.22 \times 10^{-6} \text{ F}$$

$$= 4.22 \times 10^{-6} \text{ F}$$

ii) 0.9 lagging

$$\text{actual pf} = 1.0201$$

$$\text{target pf} = \cos \phi = 0.9$$

$$\phi = \cos^{-1}(0.9) = 26.64 \Rightarrow \tan \phi = 0.48$$

$$KVAR = 74.6 \times (1.0201 - 0.48) = 111.90 \approx 112$$


$$C = \frac{KVAR}{2\pi f v^2} = \frac{112}{2 \times \pi \times 50 \times \left(\frac{415^2}{\sqrt{3}}\right)}$$

$$= 6.21 \times 10^{-5} \text{ F}$$

$$= 6.21 \times 10^{-5} \text{ F}$$

drive motor: Three phase induction motor

3)

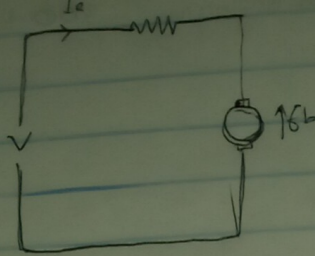

$$V = E_b + I_a \times R$$

$$V - [I_a \times R] = E_b$$

$$E_b = 220 - [0.7 \times 15]$$

$$= 209.5 \text{ V}$$

Speed on DC, $N_{DC} = 2000 \text{ rpm}$

recall speed

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} \quad \therefore \frac{E_{bAC}}{E_{bDC}} = \frac{N_{AC}}{N_{DC}}$$

$$N_{AC} = \frac{2000 \times 202.52 \text{ V}}{209.5 \text{ V}} = 1933.37 \text{ rpm}$$


On AC supply

$$V = 220 \text{ V}, I_a = 0.7 \text{ A}$$

$$\text{Resistance drop} = I_a \times R = 0.7 \times 15 = 10.5 \text{ V}$$

$$\text{Reactance voltage drop} = I_a \times X_L = 0.7 \times 2\pi f l$$
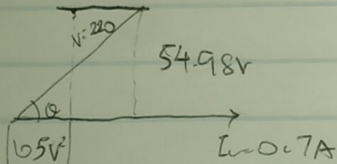
$$= 0.7 \times 2\pi \times 50 \times 0.25 = 54.98 \text{ V}$$



$$E_{bAC} = \sqrt{V^2 - [X_L]^2} - IR = \sqrt{(220)^2 - (54.98)^2} - 10.5 \text{ V}$$

$$= 202.52 \text{ V}$$

(i) Power factor, $\cos \phi = \frac{E_{bAC} + IR}{V} = \frac{202.52 + 10.5}{220} = 0.968$ lagging

(ii) Torque developed,

$$T_{ac} = \frac{E_{bAC} \times I_a}{\omega}$$


(iii) Universal motor

$$\omega = 2\pi n$$

$$T_{ac} = \frac{E_{bAC} \times I_a}{2\pi \times \frac{N_{AC}}{60}} = \frac{202.52 \times 0.7 \times 60}{2\pi \times 1933.37}$$

$$= 0.700 \text{ Nm}$$

2)

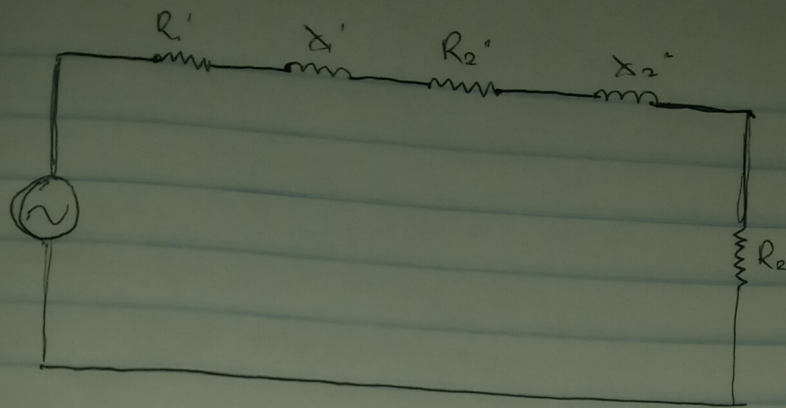

supply voltage per phase, $V = \frac{415}{\sqrt{3}} = 239.50V$

rotor;

$$R_{02} = (R_2 + k^2 R_1) = (1.173 + (5/6)^2 \times 0.25) = 1.347 \Omega$$

$$X_{02} = (X_2 + k^2 X_1) = j(0.52 + (5/6)^2 \times 0.75) = j1.041$$

$$Z_{02} = R_{02} + jX_{02} = 1.347 + j1.041$$

$$= \sqrt{1.347^2 + 1.041^2}$$

$$= 1.7 \Omega$$

rotor current;

$$I_2 = \frac{E_2}{Z_{02}}$$

$$E_2 = kV_1 = 239.6 \times 0.83 = 199.67V$$

$$I_2 = \frac{199.67}{1.7} = 117.45A$$