

Badsheraje of heritege paul
18/engoblozu

1)

ii) $V = 415V$

$f = 50Hz$

$P = 74.6kW$

$PF = 0.7$

$eff = 85\%$

Unity = 1

$\therefore C = \frac{kVAR}{2\pi fV^2}$

$kVAR = P \times C$ (from actual $\times \tan \theta$)
actual $P \cdot f = \cos \theta = 0.7$

$\theta = \cos^{-1}(0.7)$

$= 45.57$

$\tan(45.57) = 1.0201$

target $P \cdot f \Rightarrow \cos \theta = 1$

$\theta = \cos^{-1}(1) = 0$

$\tan \theta = 0$

$kVAR = 74.6 \times (1.0201 - 0)$
 $= 76.0995$
 $= 76.1$

$C = \frac{76.10}{2\pi \times 50 \times 415^2}$
 $= 1.4 \times 10^{-6} C$

ii) 0.9 lagging

actual p.f = 1.0201

target p.f = $\cos \theta = -0.9$

$\theta = \cos^{-1}(-0.9)$

$\theta = 154.10$

$\tan \theta = \tan(154.16)$

$= -0.48$

$KVAR = 74.6 \times (1.0201 - (-0.48))$

$= 111.90$

≈ 112

$C = \frac{KVAR}{2\pi f V^2} = \frac{112}{2\pi \times 50 \times 418^2}$

$= 2.068 \times 10^{-6} \text{ farad}$

$= 2.068 \mu\text{F}$

Bodovanje Ophodnega Paul



18/10/2006/074

$$2) k = \frac{5}{6} = 0.83$$

$$Z_1 = 0.28 + j0.75 \rightarrow \text{stator}$$

$$Z_2 = 1.173 + j0.52 \rightarrow \text{rotor}$$

$$V = 415V$$

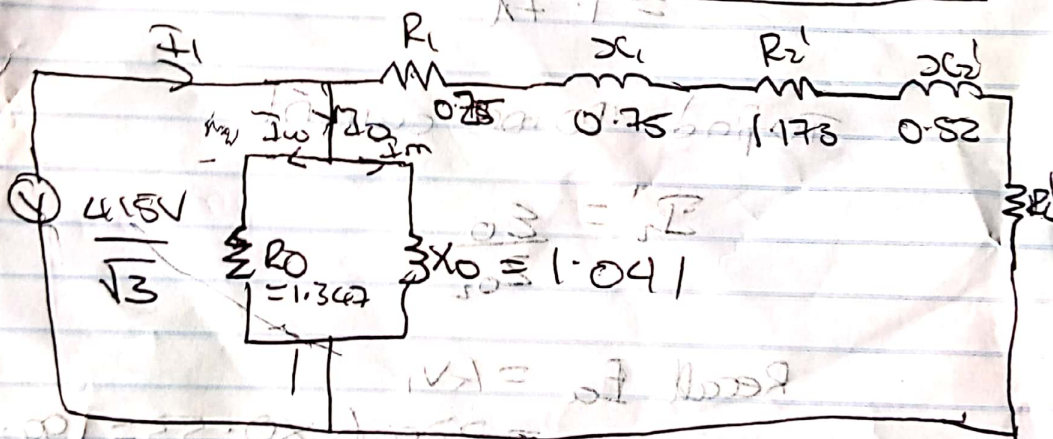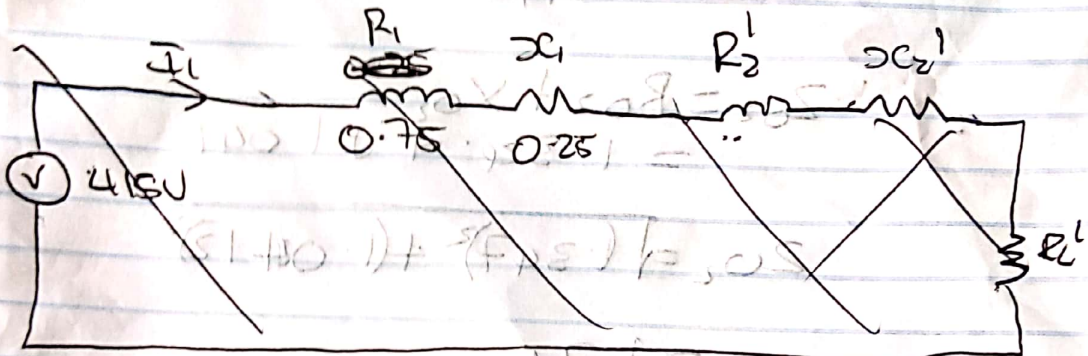

supply voltage for phase, V_L
for star connected

$$V_L = \sqrt{3} V_{\text{phase}}$$

$$415V = \sqrt{3} V_{\text{phase}}$$

$$V_{\text{phase}} = \frac{415}{\sqrt{3}}$$

$$= 239.6 V$$

Referring to rotor

$$R_{02} = (R_2 + k^2 R_1)$$

$$= (1.173 + \left(\frac{5}{6}\right)^2 \times 0.28)$$

$$= 1.347 \Omega$$

Balasan ya epheneretega awal
 is lengas 0.74

$$X_{02} = (X_2 + R_2^2 X_1)$$

$$X_{02} = (X_2 + k^2 R_1)$$

$$= j(0.82 + (\frac{8}{6})^2 \cdot 0.75) = 1.5$$

$$= 1.041$$

$$Z_{02} = R_{02} + jX_{02}$$

$$= 1.347 + j1.041$$

$$Z_{02} = \sqrt{(1.347)^2 + (1.041)^2}$$

$$= 1.71$$

to find rotor current

$$I_2' = \frac{E_0}{Z_{02}}$$


Recall $E_a = kV$

$$= 239.6 \times 0.53 = 126.178$$

$$I_2' = \frac{126.178}{1.71} = 73.8$$

Barabaraýe eýhenetegja Paul
18/engoblova

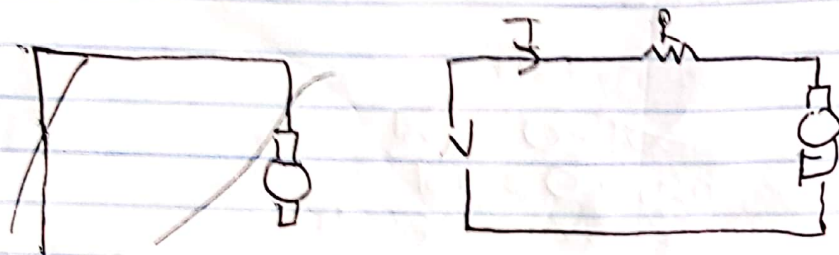3) $f = 50 \text{ Hz}$
 $N_{DC} = 2000$
 $\Sigma = 0.7 \text{ A}$
 $V = 220 \text{ V}$
 $R = 15 \Omega$
 $\omega L = 0.25 \text{ H}$



for DC Power supply

$$V - E_b = I_L \times R$$

$$220 - E_b = 0.7 \times 15$$

$$220 - E_b = 10.5$$

$$220 - 10.5 = E_b$$

$$209.5 = E_b$$

for AC supply

$$E_{bac} = \sqrt{V^2 - (I \omega L)^2} - IR$$

$$E_{bac} = \sqrt{220^2 - (0.7 \times 0.25)^2} - 0.7 \times 15 \Omega$$

$$= 219.9999 - 10.5$$

$$\omega L = 2\pi fL$$

$$= 2\pi \times 50 \times 0.25$$

$$= 78.5$$

$$\therefore E_{bac} = \sqrt{220^2 - (0.7 \times 78.5)^2} - 0.7 \times 15 \Omega$$

$$= 213 - 10.5$$

$$E_{bac} = 202.5$$

Back EMF of the motor is 202.5 V

Recall, speed control equation

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} = \frac{202.5}{209.5}$$

$$\therefore \frac{N_{ac}}{N_{bc}} = \frac{E_{bac}}{E_{bdc}}$$

$$N_{ac} = \frac{E_{bac} \times N_{bc}}{E_{bdc}}$$

$$\text{where } N_{bc} = 2000 \text{ rpm}$$

$$E_{bac} = 202.5$$

$$\text{where } E_{dc} = 209.5$$

$$\therefore N_{ac} = \frac{202.5}{209.5} \times 2000$$

$$N_{ac} = 1933 \text{ rpm}$$

$$\text{power factor } \cos \theta = \frac{IR + E_{bac}}{V}$$

$$= \frac{10.5 + 202.5}{220}$$

$$\cos \theta = 0.968 \text{ lagging}$$

$$\text{Torque developed } T_w = E_{bac} \times I$$

$$T_{ac} = \frac{E_{bac} \times I}{\omega}$$

Badaseraje oghonetege Paul
1st engob 1074

where $\omega = 2\pi n$

$$n = \frac{N_{ac}}{60} = \frac{1933}{60} = 32.2$$

$$\therefore T_{ac} = \frac{202.5 \times 10.7}{2\pi \times 32.2}$$

$$T_{ac} = 0.7 \text{ Nm}$$

31) The motor used is a universal motor