

Lumumba Ebikpo Emmanuel

17ENG061052

Mechanical Eng. Question 1

$$V = 415\text{V}, 3-\phi, 4\text{ wire } f = 50\text{Hz}$$

$$P = 74.6, \text{ P.f.} = 0.7 \text{ eff. } 85\%$$

Vary: \perp

$$C = \frac{kVAR}{2\pi fV^2}$$

$$kVAR = P \times \left(\tan \theta_{\text{actual}} - \tan \theta \right)$$
$$\theta = \cos^{-1} 0.7$$
$$= 45.57$$
$$\tan(45.57) = 1.0201$$

$$\text{Target P.f.} \Rightarrow \cos \theta = 1$$
$$\theta = \cos^{-1} 1 = 0$$
$$\tan 0 = 0$$

$$kVAR = 74.6 \times (1.0201 - 0)$$
$$= 76.0995$$
$$\underline{\underline{76.1}}$$

$$C = \frac{76.10}{2\pi \times 50 \times 415^2} = 1.4 \times 10^{-6} \text{ F}$$

(ii) 0.9 lagging
actual p.f. = 1.0201

$$\text{Target p.f.} = \cos \theta = 0.9$$
$$\theta = \cos^{-1}(0.9)$$
$$\theta = 26.10^\circ$$
$$\tan \theta = \tan(26.10^\circ)$$
$$= 0.48$$

$$kVAR = 74.6 \times (1.0201 - (-0.48))$$
$$= 44.90$$
$$\underline{\underline{44.9}}$$

Name Lumumba Ebinif Emmanuel
17/ENG06/052
Mechanical Engineering

4. Question 3

On Ac Supply


Supply Voltage = 220V

Current drawn, $I_c = 0.7A$

$$\text{Resistance drop} = I_c \times R = 0.7 \times 15 = 10.5V$$

$$\text{Reactance Voltage Drop} = I_c \times X_c = 0.7 \times 2\pi fL$$
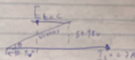
$$\begin{aligned}\text{Where } X_c &= j\omega L = 2\pi fL \\ &= 0.7 \times 2\pi \times 50 \times 0.25 \\ &= \underline{54.98V}\end{aligned}$$



$$\begin{aligned}E_{bac} &= \sqrt{V^2 - (X_c)^2} - IR \\ &= \sqrt{(220)^2 - (54.98)^2} - 10.5V \\ &= \underline{202.52V}\end{aligned}$$

Recall Speed Constant equation

$$\frac{N_b}{N_i} = \frac{E_{bi}}{E_{bi}}$$

$$\frac{E_{bac}}{E_{bdc}} = \frac{N_{dc}}{N_{dc}}$$

$$\begin{aligned}\text{Lang } N_{dc} &= N_{dc} \times \frac{E_{bac}}{E_{bdc}} \\ &= 2000 \times \frac{202.52V}{207.5V}\end{aligned}$$

$$N_{dc} = \underline{1933.37 \text{ rpm}}$$

Lumumba Ebrokpa Emmanuel
17/EN0061052
Mechanical Engineering.

Question 2

$$V_s = 415\text{V}$$


No of Poles = 6

$$f = 50\text{Hz}$$

$$k_s \approx 0.83$$

$$Z_s = 0.25 + j0.75 \text{ ~ Stator}$$

$$Z_r = 1.173 + j0.52 \text{ ~ Rotor}$$

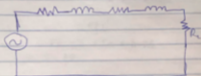

Supply Voltage per phase, $V_s \frac{415}{\sqrt{3}} = 239.50\text{V}$

Referring to rotor

$$R_{02} = (R_s + k_s^2 R_r)$$
$$= (0.25 + (0.83)^2 \times 1.173)$$
$$R_{02} = 1.347\Omega$$

$$X_{01} = (X_s + k_s^2 X_r)$$
$$= j(0.75 + (0.83)^2 \times 0.52)$$
$$= 1.041$$

$$Z_{01} = R_{02} + X_{01}$$
$$= 1.347 + j1.041$$

$$Z_{02} = \sqrt{1.347^2 + 1.041^2}$$
$$= 1.7\Omega$$

Lumumba Ebimpo Emmanuel

17/ENG06/052

Mechanical Engineering

$$\text{Power factor, } \cos \alpha = \frac{E_{bc} + I R}{\omega}$$
$$= \frac{202.52 + 10.5}{220}$$

~~Watt Speed in rad/s~~

$$= 0.968 \text{ lagging}$$

$$\text{Torque developed } T_w = \frac{E_{bc} \times I}{\omega}$$
$$T_{ac} = \frac{E_{bc} \times I}{\omega}$$

$\omega = 2\pi n$, where n is speed

$$T_{ac} = \frac{E_{bc} \times I_c}{2\pi \times \frac{N_{ac}}{60}}$$
$$= \frac{202.52 \times 0.7 \times 60}{2\pi \times 1933.37}$$
$$= 0.700 \text{ Nm}$$

To find rotor current

$$I_r = \frac{E_r}{Z_r}$$

Recall that $E_r = kv$,

$$= 239.6 \times 0.85$$
$$= 199.67 \text{ V}$$

$$\therefore I_r = \frac{199.67}{1.75} = 117.45 \text{ A}$$