

Name: Inegbedion Andrew Odigie

Department: Electrical/Electronics Engineering.

Matric no: 17/EN004/033

300 Level

Question 1

ABUAD mango juice factory is serviced by a 415V, 3-Phase, 4-wire, 50 Hz. This supply powers the main drive motor having an output of 74.6 kW and running on full load at a power factor of 0.7 lagging with an efficiency of 85%.

Identify the drive motor type and sketch the motor-supply circuit with a direct-online starter [5 marks]

Determine the capacitance per phase of a mech-connected capacitor necessary to raise the power factor to

(i) Unity

(ii) 0.9 lagging

[10 marks]

Sketch the phasor diagram using an appropriate scale showing the compound values of currents [5 marks].

Solution

$V = 415V$, 3- ϕ , 4-wire, $f = 50Hz$, $P = 74.6$
 $p.f = 0.7$, $\eta = 85\%$

(b)

(i) Unity = 1

$$C = \frac{kVAR}{2\pi f V^2}$$

$$\rightarrow kVAR = P \left(\tan \text{ actual } p.f \bar{x} \tan \text{ target } p.f \right)$$

$$\text{actual } p.f \Rightarrow \cos \theta = 0.7$$

$$\theta = \cos^{-1} 0.7$$

$$= 45.57$$

$$\tan (45.57) = 1.0201$$

$$\text{target } p.f \Rightarrow \cos \theta = 1$$

$$\theta = \cos^{-1} 1 = 0$$

Ingebedron Andrew Odjore
K11EN604/033

$$\tan \theta = 0$$

$$\begin{aligned} \text{KVAR} &= 74.6 \times (1.0201 - 0) \\ &= 76.0995 \\ &\approx 76.10 \end{aligned}$$

$$\begin{aligned} C &= \frac{76.10}{2\pi \times 50 \times 4 \times 10^{-6}} \\ &= 0.0000014 \\ &\approx 1.4 \times 10^{-6} \text{ C,} \\ &\text{(1)} \end{aligned}$$

0.9 lagging

$$\text{actual p.f.} = 1.0201$$

$$\begin{aligned} \text{target p.f.} &= \cos \theta = 0.9 \\ \theta &= \cos^{-1}(0.9) \\ &= 26.64^\circ \\ \tan \theta &= 0.48 \end{aligned}$$

$$\begin{aligned} \text{KVAR} &= 74.6 \times (1.0201 - 0.48) \\ &= 111.90 \\ &\approx 112 \end{aligned}$$

$$\begin{aligned} C &= \frac{\text{KVAR}}{2\pi fV} \\ &= \frac{112}{2\pi \times 50 \times 4 \times 10^{-6}} \\ &= 0.00086 \\ &\approx 8.6 \times 10^{-4} \text{ C} \end{aligned}$$

Name: Inegbedion Andrew Ojigie.

Department: Electrical/Electronics Engineering. 300 level.

Matric no: 17/ENH04/033.

Question 1

A 25 hp, 415V (Line-Line), 6-pole, 50Hz, star-star connected, 3-phase induction motor has used in the production factory of PZ Cussens. Stator/rotor phase voltage ratio of 6/5. The stator and rotor impedances per phase are $(0.25 + j0.75)$ ohms and $(1.173 + j0.52)$ ohms respectively using the approximate circuit version 2 referred to the rotor side ~~at~~ at a slip of unity. Find the following.

(a) Draw the equivalent circuit diagram referred to the rotor side (version 2) [2 marks]

(b) Rotor (secondary) current i_2 [8 marks]

solution

$$V_{\text{line}} = 415 \text{ V}$$

$$\text{No of poles} = 6$$


$$f = 50 \text{ Hz}$$

$$k = \frac{6}{6} = 0.83$$

$$Z_1 = 0.25 + j0.75 \text{ - stator}$$

$$Z_2 = 1.173 + j0.52 \text{ - rotor}$$

(1)

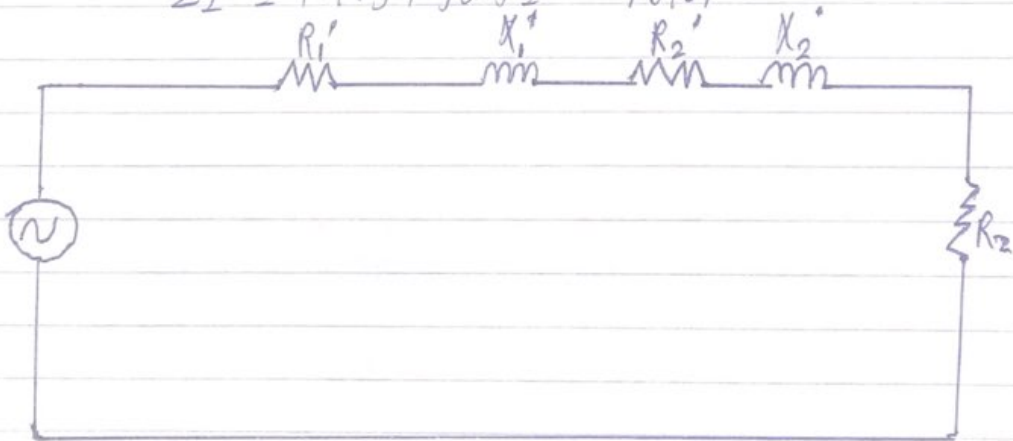

$$\text{supply voltage per phase, } V = \frac{415}{\sqrt{3}} = 239.60 \text{ v}$$

Referring to rotor

(11) Inegbedron Andrew Otrigle.
171EN041083

$$R_{02} = (R_2 + K^2 R_1) \\ = (1.173 + (5/6)^2 \times 0.25) \\ R_{02} = 1.347 \Omega$$

$$X_{02} = (X_2 + K^2 X_1) \\ = j(0.52 + (5/6)^2 \times 0.75) \\ = j1.041$$

$$Z_{02} = R_{02} + X_{02}$$

$$= 1.347 + j1.041$$

$$Z_{02} = \sqrt{1.347^2 + 1.041^2} \\ = 1.7 \Omega$$

To find Motor Current


$$I_2 = \frac{E_2}{Z_{02}}$$

Recall that $E_2 = KV_1$

$$= 239.6 \times 0.83$$

$$= 199.67 \text{ V}$$
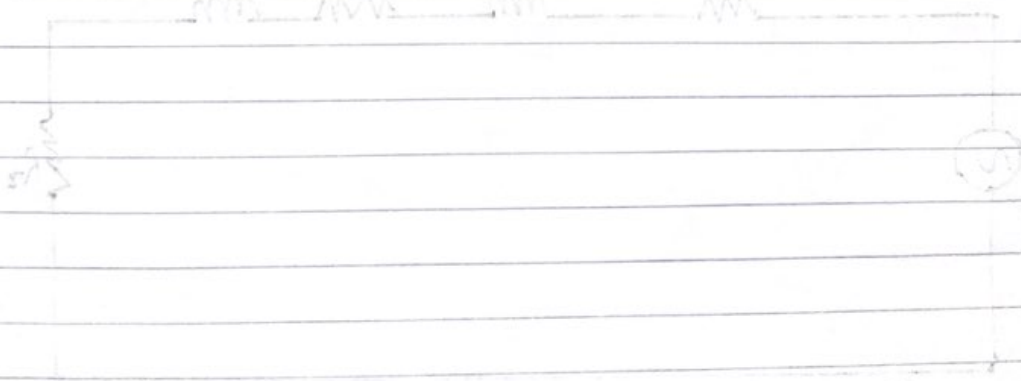
$$\therefore I_2 = \frac{199.67}{1.7} = 117.45 \text{ A}$$



Name: Inegbedion Andrew Odegre.

Department: Electrical/Electronics Engineering.

Matric no: 17/ENK04/033.

300 LEVEL

Question 3.

A 50 Hz, 1/4 hp motor runs at 2000 rpm and takes 0.7 A when connected to a 220 V DC source. If the resistance and inductance of the machine are given as respectively, determine the following when the motor is connected to a 220 V, 50 Hz AC supply and is loaded to take 0.7 A of current;

- (i) speed of the motor.
- (ii) the power factor of the motor.
- (iii) Torque developed by the motor.
- (iv) What type of motor could be used for this application?


Solution.

$f = 50 \text{ Hz}$, ~~1/4 hp~~ $1/4 \text{ hp}$, $N_s = 2000 \text{ rpm}$, $V = 220$
 15Ω and 0.25 H

On DC supply:

Supply voltage = 220 V

Current drawn, $I = 0.7 \text{ A}$

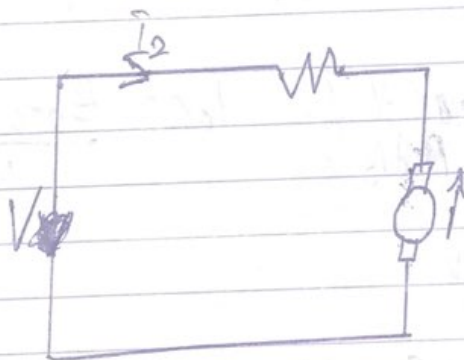

$$V - E_b = I_2 * R$$

$$V - [I_2 * R] = E_b$$

$$E_b = 220 - [0.7 * 15] = 209.5 \text{ V}$$

Speed on DC, $N_b = 2000 \text{ rpm}$

Integration Andrew Odighe

17/ENR04/033

(3I)

Recall ~~the~~ Speed - constants equation

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}$$

So

$$\frac{E_{bac}}{E_{bc}} = \frac{N_{ac}}{N_{dc}}$$

Making N_{ac} subject of the formula

$$N_{ac} = N_{dc} \times \frac{E_{bac}}{E_{bc}}$$
$$= 2000 \times \frac{202.52 \text{ V}}{209.5 \text{ V}}$$

$$N_{ac} = 1933.37 \text{ rpm}$$

(3II)

Power factor, $\cos \theta = \frac{E_{bac} + IR}{V}$

$$= \frac{202.52 + 10}{220}$$

$$= 0.968 \text{ ~~lagging~~ lagging}$$

(3III)

Torque developed $T_w = E_{bac} \times I$ $T_{ac} = \frac{E_{bac} \times I}{\omega}$

∴ where ω is speed in rad/s

On AC supply

Supply voltage = 220V

Current drain, $I_2 = 0.7 \text{ A}$

Resistance ~~drop~~ drop = $I_2 \times R = 0.7 \times 15 =$


$$= 10.5 \text{ V}$$

where $R_L = j\omega L \times 2\pi fL$

$$= 0.7 \times 2\pi \times 50 \times 0.25$$

Ingbedron Andrew Odrgr
1711EN004/033

$$= 54.98 \text{ V}$$

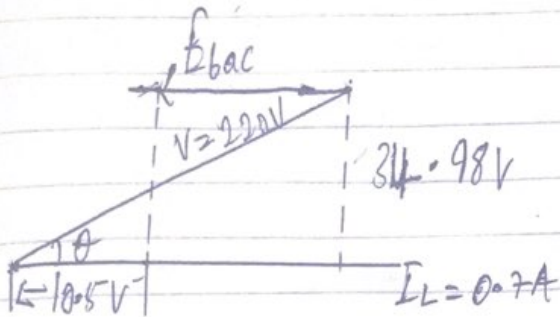

$$\begin{aligned} E_{bac} &= \sqrt{V^2 - [I_L R]^2} \\ &= \sqrt{(220)^2 - (54.98)^2} - 10.5 \text{ V} \\ &= 202.52 \text{ V} \end{aligned}$$