

Wednesday 17th June 2020.

Oru kavayen Eruten.

17/2/2024/053

Elect/Elect.

Electrical Machines. (EEE 326)

Test

Question 1

$V = 415V$, 3- ϕ , $f = 50Hz$, $P = 74.6$
 $\cos \phi = 0.7$, $\text{eff} = 85\%$

① Unity = 1

$$C = \frac{\text{KVAR}}{2\pi f V^2}$$

$\Rightarrow \text{KVAR} = P (\tan \text{actual } \phi - \tan \text{target } \phi)$

actual $\phi \Rightarrow \cos \theta = 0.7$

$$\theta = \cos^{-1} 0.7$$

$$\approx 45.57$$

$$\tan(45.57) = 1.0201$$

target $\phi \Rightarrow \cos \theta = 1$

$$\theta = \cos^{-1} 1 = 0$$

$$\tan 0 = 0$$

$$\text{KVAR} = 74.6 \times (1.0201 - 0)$$

$$= 76.0995$$

$$\approx 76.10$$

$\cdot 0.01$

$\times 10$

$$C = \frac{76.10}{2\pi \times 50 \times 415^2}$$

$$= 0.0000014$$

$$= 1.4 \times 10^{-6}$$

$$= 1.4 \times 10^{-6} \text{ F}$$

① 0.9 lagging

$$\text{actual pf} = 1.0201$$

$$\text{power pf} = \cos \theta = 0.9$$

$$\theta = \cos^{-1}(0.9)$$

$$= 26.16^\circ$$

$$\tan \theta = 0.48$$

$$\text{KVAR} = 74.6 \times (1.0201 - 0.48)$$

$$= 111.90$$

$$\approx 112$$

$$C = \frac{\text{KVAR}}{2\pi f}$$

$$= 112$$

$$\frac{112}{2\pi \times 50 \times 415^2}$$

$$= 0.00086$$

$$\approx 8.6 \times 10^{-4} \text{ F}$$

17/12/2024
Elect/Elect.

Question 2

$$V_{ph} = 415V$$


$$k = \frac{5}{6} = 0.83$$

NO. of poles = 6

$$Z_1 = 0.25 + j0.75 \text{ - Stator}$$

$$f = 50Hz$$

$$Z_2 = 1.173 + j0.52 \text{ - rotor}$$

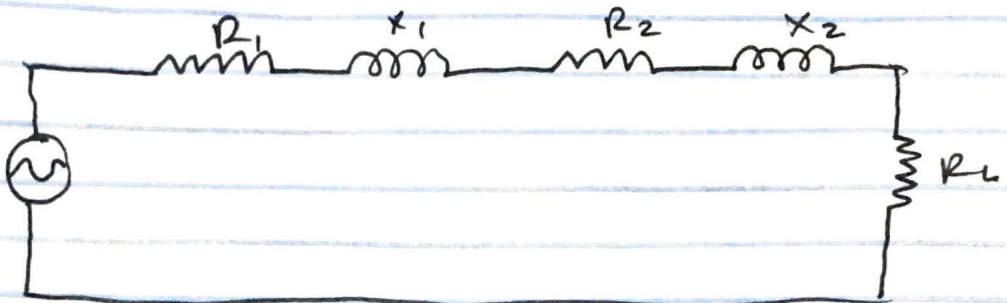

Supply voltage per phase, $V = \frac{415}{\sqrt{3}} = 239.80V$

Refering to rotor

$$R_{02} = R_2 + k^2 R_1$$

$$= 1.173 + \left(\frac{5}{6}\right)^2 \times 0.25$$

$$R_{02} = 1.347 \Omega$$

$$X_{02} = X_2 + k^2 X_1$$

$$= j(0.52 + \left(\frac{5}{6}\right)^2 \times 0.75)$$

$$= 1.041$$

$$Z_{02} = R_{02} + jX_{02}$$

$$= 1.347 + j1.041$$

$$Z_{02} = \sqrt{1.347^2 + 1.041^2}$$

$$= 1.7 \Omega$$

Rotor current

$$I_2 = \frac{E_2}{Z_{02}} \quad \left[\text{Reem } E_2 = s V_1 \right]$$

$$= \frac{239.6 \times 0.83}{1.7}$$

$$= 117.45A$$

$$\therefore I_2 = \frac{117.45}{1.7} = 69.09A$$


$$= 117.45A$$

Question 3

$f = 50\text{Hz}$, $1/4\text{hp}$, $N = 2000\text{rpm}$, $V = 220$
 15Ω and 0.25H

On DC supply
supply voltage 220V
 δ

current drawn, $I_2 = 0.7\text{A}$

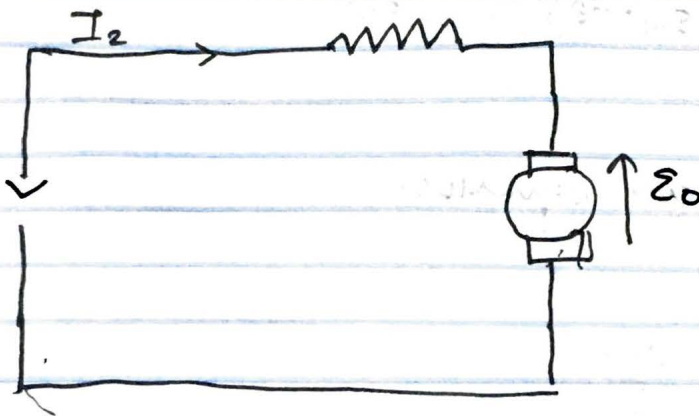

$$V - E_b = I_2 \cdot R$$

$$V - [I_2 \cdot R] = E_b$$

$$E_b = 220 - [0.7 \cdot 15]$$

$$= \underline{209.5\text{V}}$$

Speed on DC
 $N_w = 2000\text{rpm}$

On AC supply

supply voltage $= 220\text{V}$

current drawn $= I_L = 0.7\text{A}$

$$\text{Resistance drop} = I_L \cdot R = 0.7 \times 15$$

$$= \underline{10.5\text{V}}$$

$$\text{Reactance voltage drop} = I_L \cdot X_L$$


$$= 0.7 \times 2\pi f L$$

$$\text{where } X_L = j\omega L = 2\pi f L$$

$$= 0.7 \times 2\pi \times 50 \times 0.25$$

$$= \underline{54.98\text{V}}$$

17/ENG041053
 Elect/Elect.

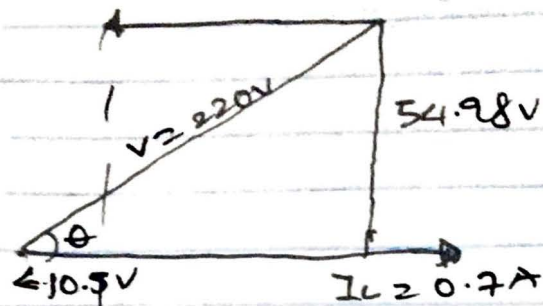

$$E_{bac} = \sqrt{V^2 - [X_L]^2} - IR$$

$$= \sqrt{(220)^2 - (54.98)^2} - 10.5V$$

$$= \underline{\underline{202.52V}}$$

For constant speed constant equation

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}$$

$$80 = \frac{E_{bae}}{E_{b80}} = \frac{N_{ae}}{N_{80}}$$

$$N_{ae} = \frac{N_{80} \times E_{bae}}{E_{b80}}, \quad 2000 \times \frac{202.52V}{209.5V}$$

$$N_{ae} = 1933.37 \text{ rpm}$$

Power factor, $\cos \phi = \frac{E_{bae} + IR^2}{V}$

$$= \frac{202.52 + 10.5}{220} = 0.968 \text{ lagging}$$

Torque developed $[W = E_{bae} \times I]$

$$I_{ae} = \frac{E_{bae} \times I}{\omega} \quad [\text{where } \omega \text{ is rad/s for speed}]$$

$$\omega = 2\pi n, \text{ where } n \text{ is}$$

$$I_{ae} = \frac{E_{bae} \times I_L}{2\pi \times \frac{N_{ae}}{60}} = \frac{202.52 \times 0.7 \times 60}{2\pi \times 1933.37}$$

$$= \underline{\underline{0.700 \text{ Nm}}}$$