

IKON SAMUEL OSCAR

17/ENG06/045

MECHANICAL ENGINEERING

EEE 326 TEST

QUESTION 1

UV $V = 415V$ 3- ϕ , 4-wire

$$f = 50 \text{ Hz}$$

$$P = 74.6$$

$$p.f = 0.7$$

$$\% \text{ eff} = 85\%$$

(i) Unity = 1

$$C = \frac{\text{KVAR}}{2\pi f V^2}$$

$$P_f = \cos \theta = 0.7$$

$$\theta = \cos^{-1}(0.7)$$

$$\theta = 45.57^\circ$$

$$\text{actual } p.f = \tan(45.57) = 1.02$$

$$\text{KVAR} = P \times (\tan \text{ actual } p.f - \tan \text{ target } p.f)$$

$$= \cos \theta = 1$$

$$\cos^{-1}(1) = 0$$

$$\tan 0 = 0$$

$$\therefore \text{KVAR} = 74.6 \times (1.02 - 0)$$

$$= 76.092$$

$$C = \frac{76.092}{2\pi \times 50 \times 415^2} = 1.4 \times 10^{-6} \text{ C}$$

$$2\pi \times 50 \times 415^2$$

(ii) 0.9 lagging

$$\text{actual } p.f = 1.02$$

$$T.p.f = \cos \theta = -0.9$$

$$\theta = \cos^{-1}(-0.9) = 154.158^\circ$$

$$\tan(154.158) = -0.48$$

$$\text{KVAR} = 74.6 \times (1.02 - (-0.48)) = 111.9$$

$$C = \text{KVAR}$$

$$2IFV$$

$$= 111.9$$

$$2 \times \pi \times 50 \times 415^2$$

$$= 2.068 \text{ AW}^{-6} \text{ C} //$$

17/ENG06/045

MECHANICAL ENGINEERING

EEE 326 TEST

QUESTION 2

$= 4.5v$

No. of poles = 6

$f = 50Hz$


$K = \frac{5}{6} = 0.23$

$Z_1 = 0.25 + j0.75$

— stator

$Z_2 = 1.175 + j0.52$

— rotor

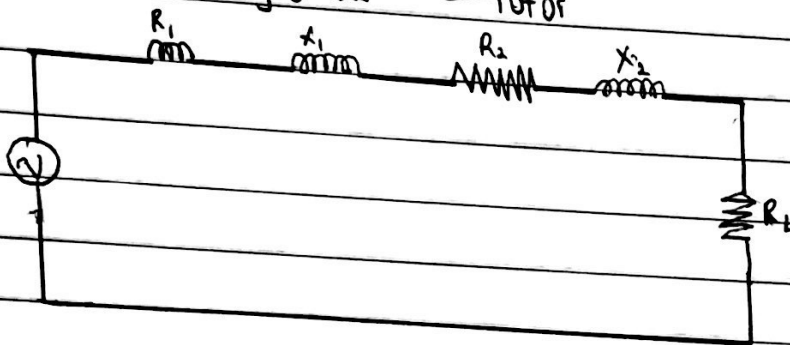

Supply voltage per phase, $v = \frac{415}{\sqrt{3}} = 239.50v$

Referring to rotor

$R_{02} = (R_2 + K^2 R_1)$

$= (1.173 + (\frac{5}{6})^2 \times 0.25)$

$R_{02} = 1.347\Omega$

$X_{02} = (X_2 + K^2 X_1)$

$= j(0.52 + (\frac{5}{6})^2 \times 0.75)$

$= 1.041$

$Z_{02} = R_{02} + X_{02}$

$= 1.347 + j1.041$

$Z_{02} = \sqrt{1.347^2 + 1.041^2}$


$= 1.7\Omega //$

(ii) to find rotor current

$$I_2 = \frac{E_2}{Z_{02}}$$

Recall that $E_2 = kV_1$
 $= 239.6 \times 0.83$
 $= 199.67V$
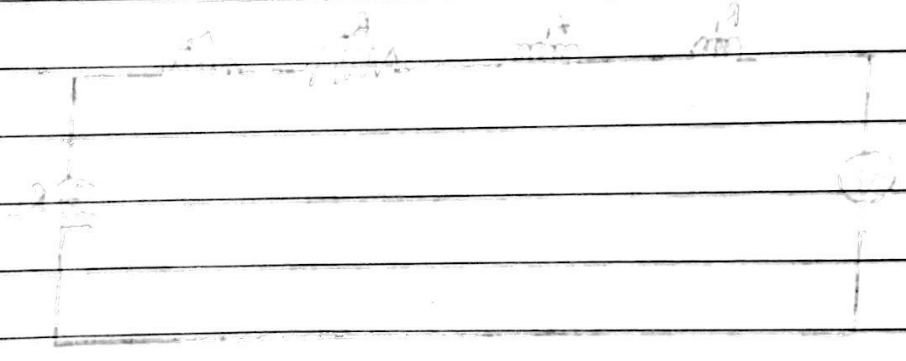
$$\therefore I_2 = \frac{199.67}{1.7} = 117.45A //$$



IKON SAMUEL OSCAR

MECHANICAL ENGINEERING

QUESTION 3

$$P = 50\text{Hz}$$

$$R = 15\Omega$$

$$N = 2000\text{rpm (dc)}$$

$$L = 0.25\text{H}$$

$$I = 0.7\text{A}$$

$$V = 220\text{V}$$

$$E = V - IR$$

$$= 220 - (0.7 \times 15)$$

$$= 209.5\text{V}$$

$$E_{ac} = \sqrt{V^2 - (I \times L)^2} - IR$$

$$I \times L = 0.7 \times 2 \times \pi \times 50 \times 0.25$$

$$= 54.98\text{V}$$

$$IR = 0.7 \times 15$$

$$= 10.5\text{V}$$

$$\therefore E_{ac} = \sqrt{220^2 - 54.98^2} - 10.5$$

$$= 213.02 - 10.5$$

$$= 202.52\text{V}$$

(i) Speed of motor

$$\text{Recall } N_{ac} = E_{ac}$$

$$N_{dc} \quad E_{dc}$$

$$N_{ac} = \frac{202.52}{209.5}$$

$$2000 \quad 209.5$$

$$N_{ac} = \frac{2000 \times 202.52}{209.5}$$

$$209.5$$

$$\therefore N_{ac} = 1933.37\text{rpm} //$$

IKON SAMUEL OSCAR
17/ENG06/045

PAGE 6

(ii) Power factor

$$pf = \frac{E + IR}{V} = \frac{202.52 + 10.5}{220} = 0.97 //$$

(iii) Torque developed

$$T = \frac{EI}{2\pi N/60} = \frac{202.52 + 0.7}{2\pi \times 1933.37/60} = 0.7 \text{ Nm} //$$

iv) Universal motor