

Name: Esaduwa Aina Robert

Dept: Mechanical

Subj: Electrical Machines

Matric: 11/ENG06/032

- i) $V = 415\text{V}$, 3 ϕ 4 wire of 50Hz $P = 74.6$
 $\text{p.f} = 0.7$, $\% \text{ eff} = 85\%$

① unity 1.

$$C = \frac{k\text{VAR}}{2\pi f v^2}$$

$\text{kVAR} = P \times (\tan \text{actual p.f} \times \text{katange p.f})$

actual p.f $\Rightarrow \cos \theta = 0.7$

$$\theta = \cos^{-1} 0.7$$

$$= 45.57$$

$$\tan (45.57) = 1.0201$$

target p.f $\Rightarrow \cos \theta = 1$

$$\theta = \cos^{-1} 1 = 0$$

$$\tan \theta = 0$$

$$\text{kVAR}_s = 74.6 \times (1.0201 - 0)$$

$$= 76.10$$

$$\approx 76.10$$

$$C = \frac{76.10}{2 \times \pi \times 50 \times 415^2}$$

$$= 0.0000014$$

$$\approx 1.4 \times 10^{-6} \text{C}$$

ii) 0.9 lagging.

Actual p.f = ~~0.7~~ 0.920

target p.f = $\cos \theta = 0.9$

$$\theta = \cos^{-1} (0.9)$$

$$= 26.16$$

$$\tan \theta = 0.48$$

2 17/ENG 06/032

Esaduwa Afaite Robert

$$E_{var} = 74.6 \times 11.0201 = (-0.78)$$

$$= 111.90$$

$$\approx 112$$

$$C = k VAR.$$

$$\approx 2\pi fV$$

$$= 112$$

$$2 \times \pi \times 50 \times 415^2$$

$$= 0.00086$$

$$= 8.6 \times 10^{-4} \text{ C/V}$$

~~2) $V_s = 415V$~~

~~*~~

2) $V_s = 415V$


$$\text{No of poles} = 6$$

$$f = 50 \text{ Hz}$$

$$k = 5/6 = 0.83$$

$$Z_1 = 0.25 + j10.75 \text{ --- stator}$$
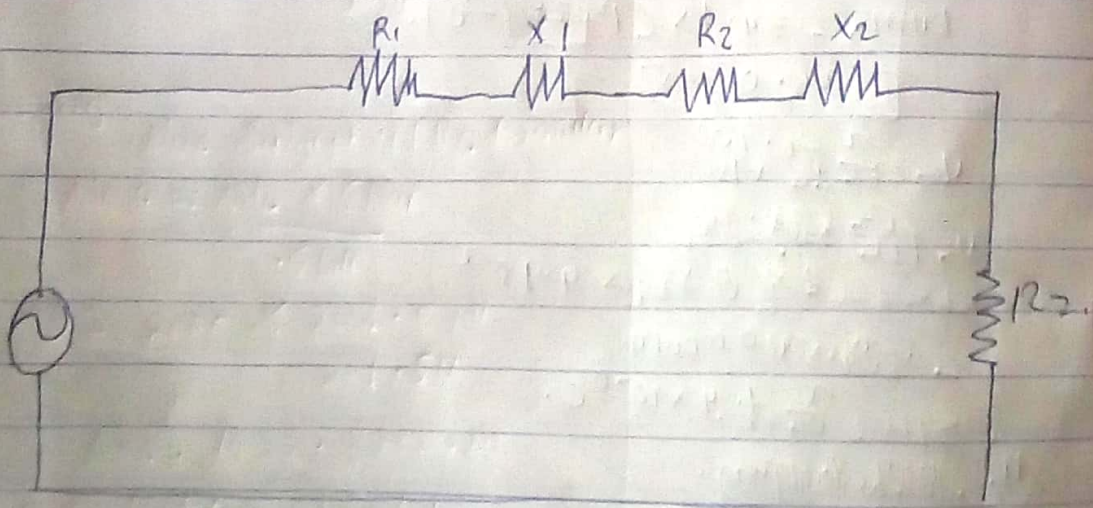
$$Z_2 = 1.93 + j10.52 \text{ --- rotor}$$



$$\text{Supply Voltage per phase } V = \frac{415}{\sqrt{3}} = 239.50 \text{ V}$$

Referring to rotor

$$R_{02} = (R_2 + k^2 R_1)$$

$$= (1.93 + (5/6)^2 \times 0.25)$$

8 17/Eno 06/032

Sadiwa Alain Robert

$$= 1.041$$

$$Z_{02} = R_{02} + jX_{02}$$

$$= 1.547 + j1.041$$

$$Z_{02} = R_{02} + jX_{02}$$

$$2.154 = 7 + j1.041$$

$$Z_{02} = \sqrt{1.547^2 + 1.041^2}$$

$$= 1.7 \Omega$$


3) $P = 50 \text{ hp}$, $1/4 \text{ hp}$ $N/2 = 2000 \text{ rpm}$ $V = 220$

150Ω and 0.254

on DC supply

Supply voltage = 220 V

Current drawn $I = 0.7 \text{ A}$

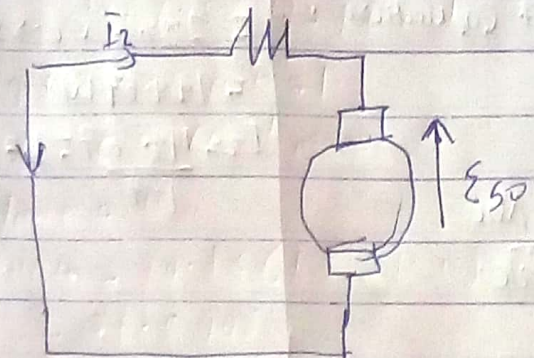

$$V - E_b = I_L \times R$$

$$V = (I_L \times R) + E_b$$

$$E_b = 220 - (0.7 \times 15)$$

$$= 209.5 \text{ V}$$

Speed on DC

$$= 2000 \text{ rpm}$$

on AC supply

Supply Voltage = 220 V


Current drawn = $I = 0.7 \text{ A}$

$$\text{Reactance drop } I_L \times R = 0.7 \times 15 = 10.5 \text{ V}$$

Reactance Voltage Drop $I_L \times X_c$

Graduate Albert Robert

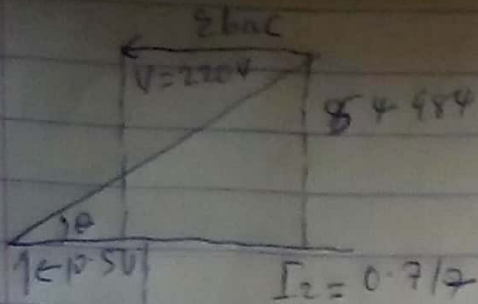where $X_L = j\omega L = 2\pi fL$
 $= 0.7 \times 2\pi \times 60 \times 0.25$
 $= 54.98V$



$$\begin{aligned} E_{bac} &= \sqrt{V^2 - (X_L)^2} - I_r \\ &= \sqrt{(220)^2 - (54.98)^2} - 10.54 \\ &= \underline{\underline{202.52V}} \end{aligned}$$

Recall speed constant equation

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}$$

$$\text{So } \frac{E_{bac}}{E_{bdc}} = \frac{N_{ac}}{N_{dc}}$$

making N_{ac} subject of the formula

$$N_{ac} = \frac{N_{dc} \times E_{bac}}{E_{bdc}}$$

$$= \frac{2000 \times 202.52V}{209.5V}$$

$$N_{ac} = 1933.37582m$$

(i) Power factor = $\frac{S_{real} + I_r}{V}$
 $= \frac{202.52 + 10}{220}$

50.988 lags
 Torque developed $T = \frac{E_{bac} \times I_a}{\omega}$
 $\omega = 2\pi n / 60$

$$\begin{aligned} T_{KO} &= \frac{E_{bac} \times I_a}{2\pi \times N_{ac}} \\ &= \frac{202.52 \times 0.7 \times 60}{2\pi \times 1933.37} \\ &= 0.700 Nm \end{aligned}$$

To find total current

$$I_r = \frac{E_2}{20^2}$$

Recall that $E_2 = k_1 \omega_1$

$$\begin{aligned} &= 239.6 \times 6.55 \\ &= 199.67W \end{aligned}$$

$$I_2 = \frac{199.67}{1.9} = 112.45A$$