

Name: Mmezi Victor

Dept: Mechanical

Matric: 17/ENG 06/054

2-) $V_{17} = 415V$


No of poles = 6

$f = 50 \text{ Hz}$

$k = \frac{5}{6} = 0.83$

$Z_1 = 0.25 + j0.75$ --- Stator

$Z_2 = 1.173 + j0.52$ --- rotor

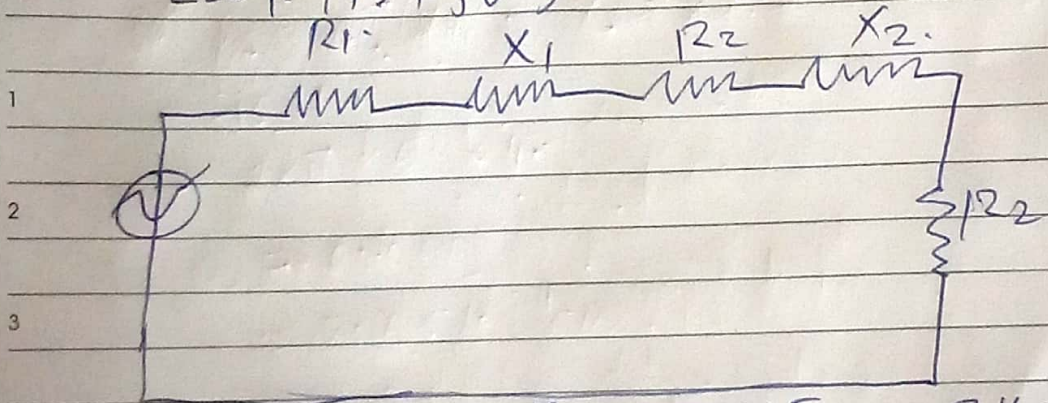

Supply voltage per phase $V = \frac{415}{\sqrt{3}} = 239.50V$

Referring to rotor

$R_{02} = (R_2 + k^2 R_1)$
 $= (1.173 + (\frac{5}{6})^2 \times 0.25)$

$R_{02} = 1.347 \Omega$

$X_{02} = (X_2 + k^2 X_1)$
 $= j(0.52 + (\frac{5}{6})^2 \times 0.75)$
 $= j1.041$ @

$Z_{02} = R_{02} + X_{02}$
 $= 1.347 + j1.041$

JUNE

M	T	W	T	F	S	S
					1	2
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

Mmezi Vichor
17/6/2019

19

Wednesday

Week 25

2019

170-196

$$Z_{02} = R_{02} \times X_{02}$$

$$= 1.547 + j 1.041$$

$$Z_{02} = \sqrt{1.547^2 + 1.041^2}$$

$$= \underline{\underline{1.92}}$$

10

11

12

1

2

3

4

5

6

7

JUNE



@

M	T	W	T	F	S	S
					1	2
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

Mmezi Victor 17/ENG 06/054
3


$$\text{Reactance drop} = I_c \times R = 0.7 \times 15 = 10.5 \text{ V}$$

$$\text{Reactance voltage drop} = I_c \times X_c$$

$$\text{where } X_c = j\omega L = 2\pi fL$$

$$= 0.7 \times 2\pi \times 50 \times 0.25$$

$$= 54.98 \text{ V}$$

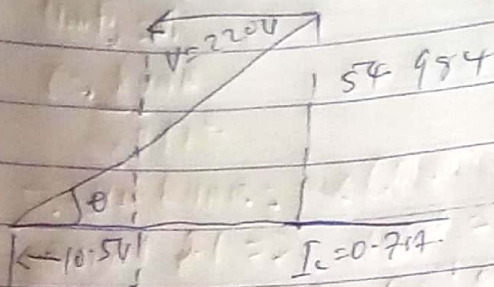

$$E_{bac} = \sqrt{V^2 - (X_c)^2} - IR$$

$$= \sqrt{(220)^2 - (54.98)^2} - 10.54$$

$$= 202.524$$

Recall speed constant equation:

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}$$

$$\text{So } \frac{E_{bac}}{E_{bdc}} = \frac{N_{ac}}{N_{dc}}$$

Making N_{ac} subject of the formula:

$$N_{ac} = N_{dc} \times \frac{E_{bac}}{E_{bdc}}$$

$$= 2000 \times \frac{202.524}{209.50}$$

$$N_{ac} = 1933.37 \text{ rpm}$$

$$(ii) \text{ Power factor} = \frac{E_{bac} + IR}{V}$$

$$= \frac{202.52 + 10}{220}$$

17/ENG 66/057
4

~~T~~ = 0.965 lags.

Torque developed $T_w = \Sigma b a c$.

$\omega = 2\pi n$, where n is speed in rpm

$$T_{ao} = \Sigma b a c \times T_c$$

$$\frac{2\pi \times 1933 \cdot 37}{60}$$

$$= \frac{202.57 \times 0.7 \times 60}{2\pi \times 1933.37}$$

$$= 0.700 \text{ Nm}$$

$$= 0.700 \text{ Nm}$$

To find rotor current.

$$I_r = \frac{\Sigma_2}{202}$$

Recall that $\Sigma_2 = k_r I_r$

$$= 239.6 \times 0.85$$

$$= 199.67 \text{ W}$$

$$I_r = \frac{199.67}{1.7} = 117.45 \text{ A}$$

17/5/2006/054 Mmazi Victor

Name: Mmazi Victor

Dept: Mechanical Engineering

Matric: 17/5/2006/054

Subj: Electrical Machines

(i) ~~Given~~ $V = 415V$, 3- ϕ ϕ -wire of = 50 Hz, $P = 74.6$
 $p.f = 0.7$, % eff = 85%

(i) Unity = 1

$$C = \frac{kVAR}{2\pi f u^2}$$

$$\rightarrow \text{KVAR} = P \times (\tan \text{ actual } p.f - \tan \text{ target } p.f)$$

$$\text{Actual } p.f \Rightarrow \cos \theta = 0.7$$

$$\theta = \cos^{-1} 0.7$$

$$= 45.57^\circ$$

$$\tan (45.57^\circ) = 1.0201$$

$$\text{target } p.f \Rightarrow \cos \theta = 1$$

$$\theta = \cos^{-1} 1 = 0$$

$$\tan \theta = 0$$

$$KVAR = 74.6 \times (1.0201 - 0)$$

$$= 76.0995$$

$$\approx 76.10$$

$$C = \frac{76.10}{2 \times \pi \times 50 \times 415^2}$$

$$= 0.0000014$$

$$\approx 1.4 \times 10^{-6} F$$

(ii) 0.9 lagging.

$$\text{Actual } p.f = 1.0201$$

$$\text{target } p.f = \cos \theta = 0.9$$

$$\theta = \cos^{-1} (0.9)$$

$$= 26.6^\circ$$

$$\tan \theta = -0.48$$

Mmari Victor 11/5na 06/054 2

$$KVAR = 90.6 \times [(1.0281) - (0.948)]$$

$$= 111.90$$

$$\approx 112$$

$$C = \frac{KVAR}{2\pi fV}$$

$$= \frac{112}{2\pi \times 50 \times 4.15^2}$$

$$= 0.00086$$


$$= 8.6 \times 10^{-4} C //$$

Q) $P = 50 \text{ Hz}$, $P = 4 \text{ hp}$, $N = 2000 \text{ RPM}$, $V = 220$
 150Ω and 0.25 H

on DC supply.

Supply Voltage = 220V.

Current draws, $I = 0.7 \text{ A}$.

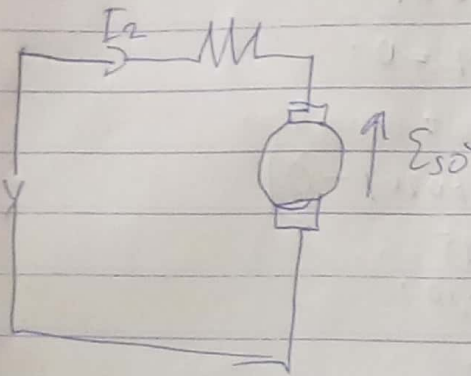

$$V - E_b = I_c * R$$

$$V = (I_c * R) + E_b$$

$$E_b = 220 - (0.7 * 15)$$

$$= 209.5 \text{ V}$$

Speed on DC.

$N_{dc} = 2000 \text{ RPM}$.

on AC supply.

Supply Voltage = 220V.

Current draw $I = 0.7 \text{ A}$.