

Amoo Oluwaferanmi Mark

18/eng04/077

Test

1)

AMOO OLUWAFERANMI MARK

18/ENG104/077

ELECTRICAL/ELECTRONICS ENGINEERING



ELECTRICAL MACHINES EEE 326

TEST

7 The equivalent

(i) Power factor raised to unity = 1

$$C = \frac{KVAR}{2\pi f V^2}$$

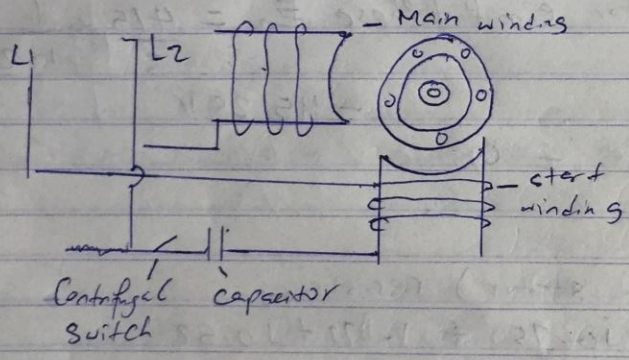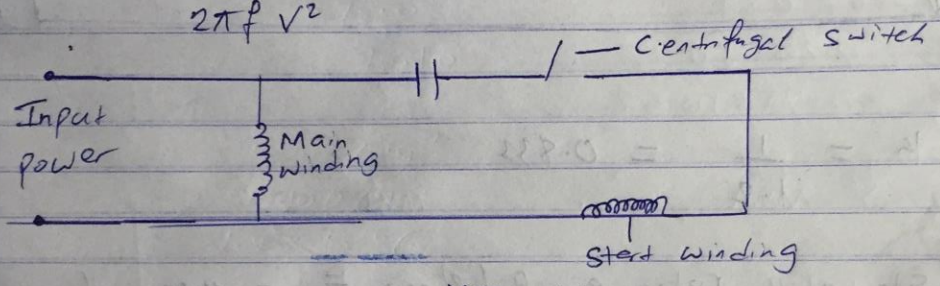

The drive motor type is a capacitor-start single phase Induction Motor

$$\text{Unity} = 1$$

$$C = \frac{KVAR}{2\pi f V^2}$$

$$KVAR = P \times (\tan \text{ actual P.f} - \tan \text{ target P.f})$$

$$\text{actual P.f} \Rightarrow \cos \theta = 0.7$$

$$\theta = \cos^{-1} 0.7$$

$$= 45.57$$

$$\tan (45.57) = 1.0201$$

2

18: AMOO OLUWAFERANMI MARIC

18/ENG04/077

$$\text{target power factor} \Rightarrow \cos \theta = 1$$

$$\theta = \cos^{-1} 1 = 0$$

$$\tan \theta = 0$$

$$\text{KVAR} = 74.6 \times (1.0201 - 0)$$

$$= 76.0955$$

$$\approx 76.10$$

$$C = \frac{76.10}{2\pi \times 50 \times 415^2}$$

$$= 0.0000014$$

$$\approx 1.4 \times 10^{-6} \text{ C}$$

ii 0.9 Lagging

actual P.F = 1.0201

$$\text{target power factor} = \cos \theta = -0.9$$

$$\theta = \cos^{-1} (-0.9)$$

$$= 154.16$$

$$\tan \theta = -0.48$$

$$\text{KVAR} = 74.6 \times (1.0201 - (-0.48))$$

$$= 111.90$$

$$\approx 112$$

$$C = \frac{\text{KVAR}}{2\pi fV}$$

$$= \frac{112}{2\pi \times 50 \times 415^2}$$

$$= 0.00086$$


$$\approx 8.6 \times 10^{-4} \text{ C}$$

$$= 0.00086$$

$$\approx 8.6 \times 10^{-4} \text{ C}$$

3

ASADU OLUNAFERANMI
181EN0041077

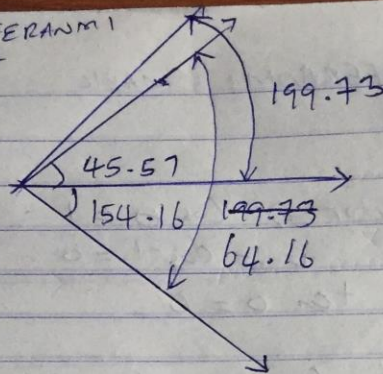


2 $V = 415 \text{ V}$

$$k = 5/6 = 0.83$$

$$Z_1 = 0.25 + j0.75$$

$$Z_2 = 1.173 + j0.52$$

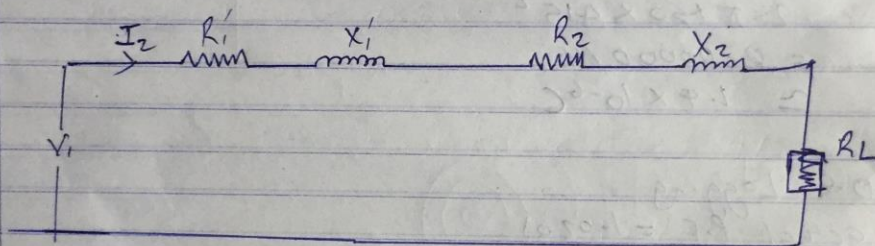

Supply Voltage per phase $V = \frac{415}{\sqrt{3}} = 239.60 \text{ V}$

Referring to rotor

$$R_{02} = (R_2 + k^2 R_1)$$

$$= (1.173 + (5/6)^2 \times 0.25)$$

$$R_{02} = 1.347 \Omega$$

$$X_{02} = (X_2 + k^2 X_1)$$

$$= j(0.52 + (5/6)^2 \times 0.75)$$

$$= 1.041$$

$$Z_{02} = R_{02} + X_{02}$$

$$= 1.347 + j1.041$$

$$Z_{02} = \sqrt{1.347^2 + 1.041^2}$$

$$= 1.7 \Omega$$

To find Rotor Current

$$I_2 = \frac{E_2}{Z_{02}}$$

4


AMOO OLUWAFERANMI MARIC

18/ENR04/077

$$\begin{aligned} \text{Recall that } E_b &= K\omega \\ &= 239.6 \times 0.83 \\ &= 199.67 \end{aligned}$$

$$\begin{aligned} \therefore I_r &= \frac{199.67}{1.7} \\ &= 117.45 \text{ A} // \end{aligned}$$
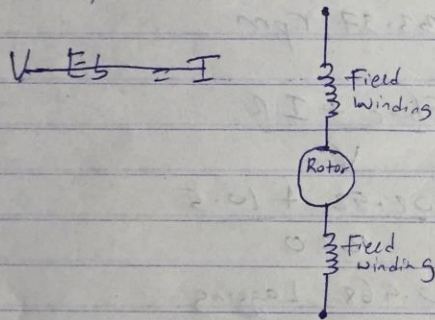
$$\begin{aligned} 3 \quad f &= 50 \text{ Hz} & V &= 220 \text{ V} \\ \frac{1}{4} \text{ hp} & & R &= 15 \\ N_s &= 2000 \text{ rpm} & L &= 0.25 \end{aligned}$$



$$V - E_b = I_r \times R$$

$$V - [I_r \times R] = E_b$$

$$E_b = 220 - [0.7 \times 15]$$

$$E_b = 209.5 \text{ V}$$

For AC supply

$$\text{Supply Voltage} = 220 \text{ V}$$

$$\text{Current drawn} = I_r = 0.7 \text{ A}$$

$$\begin{aligned} \text{Resistance drop} &= I_r \times R = 0.7 \times 15 \\ &= 10.5 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{Reactance Voltage drop} &= I_r \times X_L \\ &= 0.7 \times 2\pi fL \end{aligned}$$

$$\text{Where } X_L = j\omega L = 2\pi fL$$

$$= 0.7 \times 2 \times \pi \times 50 \times 0.25$$

$$= 54.98 \text{ V}$$

5) AM00 OLUWAFERANMI
181ENG04/077 -

$$\begin{aligned} E_{bac} &= \sqrt{V^2 - [X_L]^2} - IR \\ &= \sqrt{220^2 - (54.5)^2} - 10.5 \\ &= 202.52 \text{ V} \end{aligned}$$

(i) Recall Speed Equation

$$\frac{N_2}{N_1} = \frac{E_{bac}}{E_{dc}}$$

$$N_1 = \frac{E_{bac} \times N_2}{E_{dc}}$$

$$N_1 = \frac{202.52 \times 2000}{209.5}$$

$$= 2000 \times \frac{202.52}{209.5}$$

$$N_1 = 1933.37 \text{ rpm}$$

(ii) Power factor, $\cos \phi = \frac{E_{bac} + IR}{V}$

$$= \frac{202.52 + 10.5}{220}$$

$$= 0.968 \text{ Lagging}$$

(iii) Torque developed $T_{ac} = \frac{E_{bac} \times I}{\omega}$

$$= \frac{202.52 \times 0.7}{2 \times 50 \times \pi}$$

$$= 0.45 \text{ Nm}$$

iv A Universal Motor could be used for the Application