

Mechanical - Engineering

Question 1

$f = 50 \text{ Hz}$; efficiency = 85%; power factor = 0.7; $V = 415 \text{ V}$; 3 ϕ ; 4-wire.
 $P = 74.6$

a) unity = 1

$$C = \frac{kVAR}{2\pi fV^2}$$

$$= 7.618 = P \times \left(\frac{\tan \theta_{actual} \text{ p.f.} - \tan \theta_{target} \text{ p.f.}}{\cos^2 \theta_{target} \text{ p.f.}} \right)$$

actual p.f. $\Rightarrow \cos \theta = 0.7$

$$\theta = \cos^{-1} 0.7 = 45.57$$

$$\tan(45.59) = 1.0201$$

target p.f. $\Rightarrow \cos \theta = 1$

$$\theta = \cos^{-1} 1 = 0$$

$$\tan 0 = 0$$

$$kVAR = 74.6 \times (1.0201 - 0)$$

$$= 76.18$$

$$C = 76.18$$

$$\frac{76.18}{2 \times \pi \times 50 \times 415^2} = 0.0000014$$

$$\approx 1.4 \times 10^{-6} \text{ F}$$

b) 0.9 Lagging

actual p.f. = 1.0201

target p.f. = $\cos \theta = 0.9$

$$\theta = \cos^{-1}(0.9)$$

$$= 26.16$$

$$\tan \theta = 0.48$$

17/EN6061005

~~Question 1~~ Question 1 (cont. d)

$$K_{VAR} = 74.6 \times (1.021 - C - 0.48)$$

$$\approx 11.90$$

$$\approx 12$$

$$C = \frac{K_{VAR}}{2\pi fV}$$

$$\approx \frac{12}{2 \times \pi \times 50 \times 415^2}$$

$$\approx 0.00086$$

$$\approx 8.6 \times 10^{-4} C$$

17/10/2020

Arjun Chakrabarti
17EN60605
Mechanical Engineering


Electrical Machines
EE6326

Question 2

$$V = 4150, \text{ No of poles} = 6; \text{ } p = 50 \text{ Hz}; \text{ } 5/6 = 0.83$$

$$Z_1 = 0.25 + j0.75 \quad \text{--- stator}$$
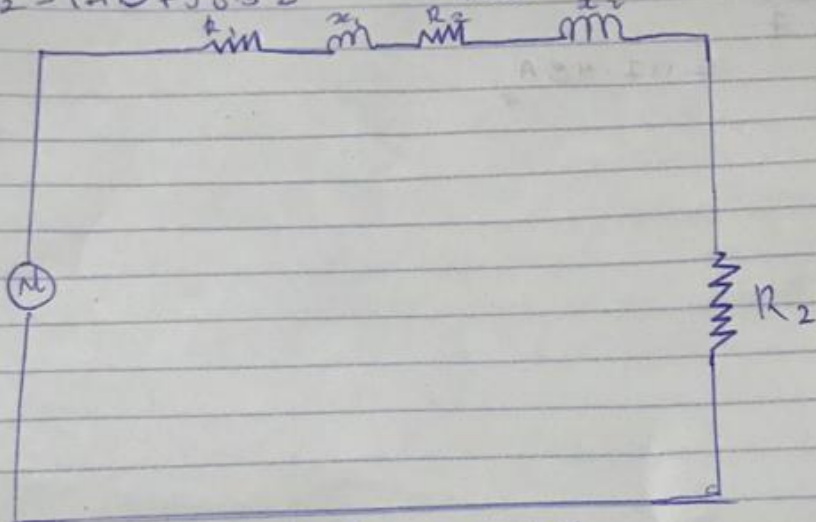
$$Z_2 = 1.173 + j0.52 \quad \text{--- rotor}$$



Supply voltage per phase $V = \frac{415}{\sqrt{3}} = 239.50 \text{ V}$

Referring to rotor

$$R_{02} = (R_2 + k^2 R_1)$$

$$= (1.173 + (5/6)^2 \times 0.25)$$

$$R_{02} = 1.347 \Omega$$

$$X_{02} = (X_2 + k^2 X_1)$$

$$= j(0.52 + (5/6)^2 \times 0.75)$$

$$= j1.041$$

$$Z_{02} = R_{02} + jX_{02}$$

$$= 1.347 + j1.041$$

$$= Z_{02} \sqrt{1.347^2 + 1.041^2}$$

$$= 1.7 \Omega$$

17/16/16 04/005

an estion ②

$$I_2 = \frac{E_2}{202}$$

Recall that $E_2 = k i_1$
 $= 239.6 \times 0.85$
 $= 199.67 \text{ A}$

$$\therefore I_2 = \frac{199.67}{1.7}$$

$$= 117.45 \text{ A}$$

B

*


QUESTION 3

$f = 50\text{ Hz}$, $1/4\text{ hp}$, $N_2 = 2000\text{ rpm}$; $V = 220\text{ V}$ $150\text{ L and } 0.25$

On DC Supply

Supply Voltage = 220 V

Current drawn $I = 0.7\text{ A}$

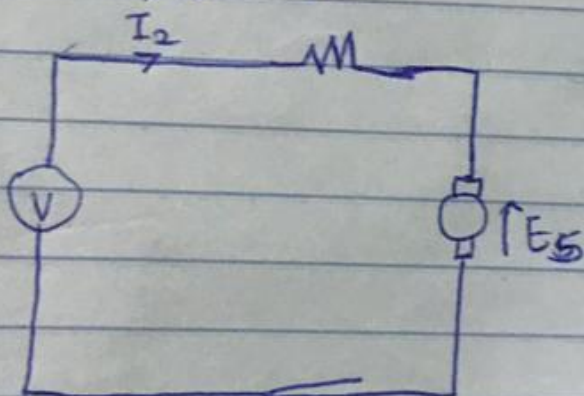

$$V = E_b + I_L R$$

$$V = [I_L R] + E_b$$

$$E_b = 220 - [0.7 \times 5]$$

$$= 209.5\text{ V}$$

Speed on DC

$$N_{DC} = 2000\text{ rpm}$$

on estun 2

17/6/06/005

Question 3


on AC supply

Supply voltage = 220V

Current drawn $I_L = 0.7A$

Reactance drop = $I_L \times R = 0.7 \times 15 = 10.5V$

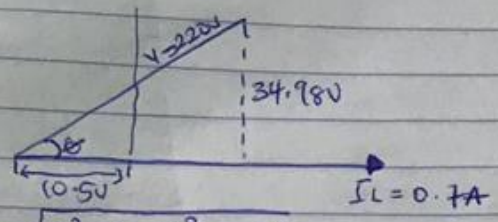Reactance voltage drop = $I_L \times X_L = 0.7 \times 2\pi fL$
where $X_L = 2\pi fL$
 $= 0.7 \times 2\pi \times 80 \times 0.25 = 54.98V$



$$E_{bac} = \sqrt{V^2 - [X_L I]^2} - IR$$

$$= \sqrt{(220)^2 - (54.98)^2} - 10.5V$$

$$= 202.52V$$

Recall speed constant equation

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}$$

$$\text{so } \frac{E_{bac}}{E_{bae}} = \frac{2n_{ac}}{n_{dc}}$$

making n_{ac} subject of the formula

$$n_{ac} = n_{dc} \times \frac{E_{bac}}{E_{bae}}$$

$$= 2000 \times \frac{202.52V}{209.5V}$$

$$= 1933.37 \text{ rpm}$$

Power factor, $\cos \phi = \frac{E_{bac} + IR}{V}$

$$= \frac{202.52 + 10.5}{220}$$

17/11/2015

question 3

$$= 0.968 \text{ Lagging}$$

$$\text{Torque developed } T_w = \frac{E_b a_e \times I}{\omega}$$
$$T_{ac} = \frac{E_b a_e \times I}{\omega}$$

~~at speed~~ Constant equation. where ω is speed in rad/sec

$$\omega = 2\pi n$$

where n is speed in revolution

$$T_{ac} = \frac{E_b a_e \times I}{2\pi \times \frac{N a_e}{60}}$$

$$= \frac{202.52 \times 0.7 \times 60}{2\pi \times 1933.37}$$

$$= 0.700 \text{ Nm}$$